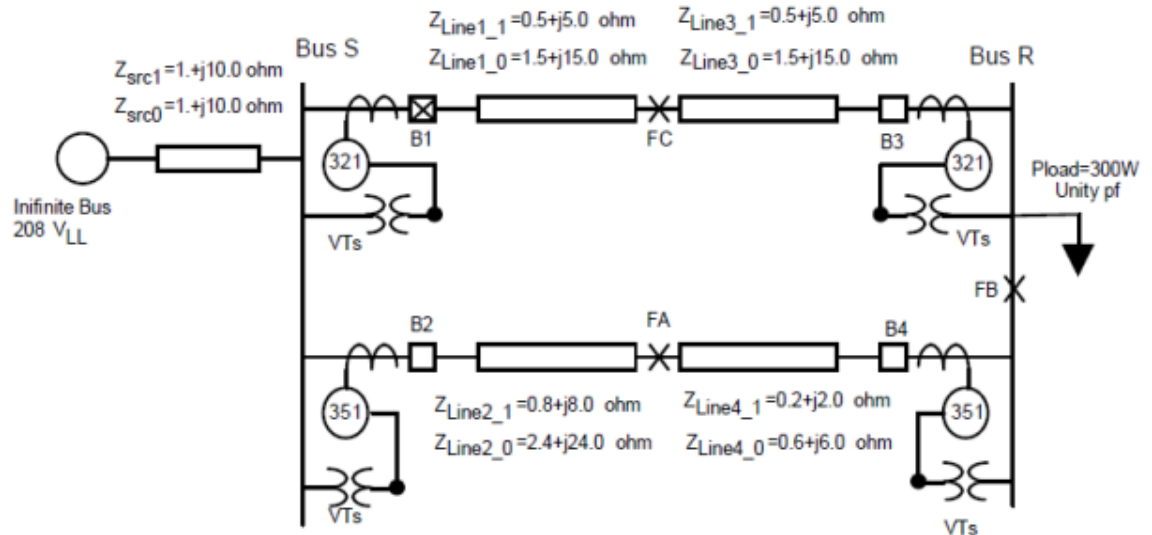


# Joe Stanley

## Lab 1 ECE525



### Before the Lab

1. Calculate load current and potential fault currents and voltages seen at the relay at B2 for faults placed at the boundaries of zone 1 (80% of the way from BusS to BusR) and zone 2 (150% of the impedance of Line2 + Line4) to determine the relay settings.

- FA ia at 80% of the line.
- FB ia at 100% of the line.
- FC ia at 150% of the line.

*Note:* For our purposes, all electrical characteristics related to the protective relays and breakers will be ignored.

In [49]:

```
1 # Import the Necessary Libraries
2 #####
3 import numpy as np
4 from scipy.optimize import fsolve
5 import cmath as c
6 import eepower as eep
7 from eepower import u, m, k, M
```

In [50]:

```
1  # Define ALL System Components
2  #####
3  Vsrc_l1 = 208 #V angle 0
4  Zsrc1 = 1+10j
5  Zsrc0 = 1+10j
6  Zline1_1 = 0.5+5j
7  Zline1_0 = 1.5+15j
8  Zline2_1 = 0.8+8j
9  Zline2_0 = 2.4+24j
10 Zline3_1 = 0.5+5j
11 Zline3_0 = 1.5+15j
12 Zline4_1 = 0.2+2j
13 Zline4_0 = 0.6+6j
14 Pload_3phs = 300
15 PF = 1.0
```

In [96]:

```
1  # Calculate (pre-fault) Load Current
2  #####
3
4  # Find total Positive-Sequence Impedance
5  Zp_eq = Zsrc1 + Zline2_1 + Zline4_1
6  print("Total Pos-Seq Z:",Zp_eq,"ohms")
7
8  # Constant Power Load will vary current draw to meet voltage characteristics
9  # Luckily, we can model it as a resistor since it's unity PF.
10 Vsrc_ln = eep.phaseline(VLL = Vsrc_ll)
11 eep.cprint(Vsrc_ln,"Volts","Line-Neutral Source Voltage")
12
13 # Define Functions
14 I1 = lambda VL: abs((Vsrc_ln - VL) / Zp_eq)
15 I2 = lambda VL: Pload_3phs / (3*VL)
16 loadvolt = lambda VL: I1(VL) - I2(VL)
17
18 # Use Numerical Solver to Calculate Load Voltage
19 VL = fsolve(loadvolt, 50)
20 print("Load Voltage Magnitude (L-N):",VL[0],"Volts")
21
22 # Use Function to determine the pre-fault Load current
23 Iload = I1(VL)[0]
24 print("Load Current Magnitude:",Iload,"Amps")
25
26 # Since no reference angle given on Vsrc, and Load declared as unity-PF,
27 # we can "set" the Load voltage and current to angle-0-degrees
28
29 # Find Load Current from Source
30 Vz = Iload * Zp_eq
31 IL = Iload * eep.phasor(1,-np.degrees(c.phase(Vz)))
32 Iload = [IL, IL * eep.a**2, IL * eep.a]
33 eep.cprint(Iload,"Amps","Load Current:")
34
35 # Find Pre-Fault Voltage at Relay and Breaker 2
36 Vpre = abs(Vsrc_ln) - IL * Zsrc1
37 eep.cprint(Vpre,"Volts","Pre-Fault Voltage at Bus S:")
38
39 # Find Pre-Fault Approximate Load Impedance
40 Zload = VL/I1(VL)[0]
41 print("Load Resistance:",Zload[0],"ohms")
```

Total Pos-Seq Z: (2+20j) ohms  
Line-Neutral Source Voltage 120.089  $\angle$  0.0° Volts  
Load Voltage Magnitude (L-N): 99.98636346596534 Volts  
Load Current Magnitude: 1.0001363839383888 Amps  
[['Load Current: 1.0  $\angle$  -84.289° Amps']  
 ['Load Current: 1.0  $\angle$  155.711° Amps']  
 ['Load Current: 1.0  $\angle$  35.711° Amps']]  
Pre-Fault Voltage at Bus S: 110.038  $\angle$  0.0° Volts  
Load Resistance: 99.97272879148129 ohms

In [60]:

```
1  # Calculate the Sequence Impedances
2  #####
3
4  # Pos/Neg and Zero Sequence for FA
5  Zseq1_A = Zsrc1 + Zline2_1
6  Zseq0_A = Zsrc0 + Zline2_0
7  ZFA = [Zseq0_A, Zseq1_A, Zseq1_A]
8
9  # Pos/Neg and Zero Sequence for FB
10 Zseq1_B = Zp_eq
11 Zseq0_B = Zsrc0 + Zline2_0 + Zline4_0
12 ZFB = [Zseq0_B, Zseq1_B, Zseq1_B]
13
14 # Pos/Neg and Zero Sequence for FC
15 Zseq1_C = Zsrc1 + Zline2_1 + Zline4_1 + Zline3_1
16 Zseq0_C = Zsrc0 + Zline2_0 + Zline4_0 + Zline3_0
17 ZFC = [Zseq0_C, Zseq1_C, Zseq1_C]
```

In [90]:

```
1  # Calculate the Total Currents
2  #####
3  # Total = Fault + Load
4
5  # Single Line to Ground
6  print("SLG Results:")
7  IFA_slg = eep.fault.phs1g(Vsrc_ln,ZFA,sequence=False)
8  eep.cprint(IFA_slg + Iload,"Amps","IFA-SLG")
9  IFB_slg = eep.fault.phs1g(Vsrc_ln,ZFB,sequence=False)
10 eep.cprint(IFB_slg + Iload,"Amps","IFB-SLG")
11 IFC_slg = eep.fault.phs1g(Vsrc_ln,ZFC,sequence=False)
12 eep.cprint(IFC_slg + Iload,"Amps","IFC-SLG")
13 print()
14
15 # Double Line to Ground
16 print("DLG Results:")
17 IFA_dlg = eep.fault.phs2g(Vsrc_ln,ZFA,sequence=False)
18 eep.cprint(IFA_dlg + Iload,"Amps","IFA-DLG")
19 IFB_dlg = eep.fault.phs2g(Vsrc_ln,ZFB,sequence=False)
20 eep.cprint(IFB_dlg + Iload,"Amps","IFB-DLG")
21 IFC_dlg = eep.fault.phs2g(Vsrc_ln,ZFC,sequence=False)
22 eep.cprint(IFC_dlg + Iload,"Amps","IFC-DLG")
23 print()
24
25 # Double Line
26 print("Line-to-Line Results:")
27 IFA_dl = eep.fault.phs2(Vsrc_ln,ZFA,sequence=False)
28 eep.cprint(IFA_dl + Iload,"Amps","IFA-DL")
29 IFB_dl = eep.fault.phs2(Vsrc_ln,ZFB,sequence=False)
30 eep.cprint(IFB_dl + Iload,"Amps","IFB-DL")
31 IFC_dl = eep.fault.phs2(Vsrc_ln,ZFC,sequence=False)
32 eep.cprint(IFC_dl + Iload,"Amps","IFC-DL")
33 print()
34
35 # Double Line
36 print("Bolted (3-Phase) Results:")
37 IFA_3 = eep.fault.phs3(Vsrc_ln,ZFA,sequence=False)
38 eep.cprint(IFA_3 + Iload,"Amps","IFA-Bolted")
39 IFB_3 = eep.fault.phs3(Vsrc_ln,ZFB,sequence=False)
40 eep.cprint(IFB_3 + Iload,"Amps","IFB-Bolted")
41 IFC_3 = eep.fault.phs3(Vsrc_ln,ZFC,sequence=False)
42 eep.cprint(IFC_3 + Iload,"Amps","IFC-Bolted")
```

SLG Results:

```
[['IFA-SLG 6.121 ∠ -84.289° Amps']
 ['IFA-SLG 1.0 ∠ 155.711° Amps']
 ['IFA-SLG 1.0 ∠ 35.711° Amps']]
[['IFB-SLG 5.481 ∠ -84.289° Amps']
 ['IFB-SLG 1.0 ∠ 155.711° Amps']
 ['IFB-SLG 1.0 ∠ 35.711° Amps']]
[['IFC-SLG 4.414 ∠ -84.289° Amps']
 ['IFC-SLG 1.0 ∠ 155.711° Amps']
 ['IFC-SLG 1.0 ∠ 35.711° Amps']]
```

DLG Results:

```
[['IFA-DLG 1.0 ∠ -84.289° Amps']
 ['IFA-DLG 7.102 ∠ 164.372° Amps']]
```

```
['IFA-DLG 7.102 ∠ 27.049° Amps']]  
[['IFB-DLG 1.0 ∠ -84.289° Amps']  
['IFB-DLG 6.461 ∠ 164.928° Amps']  
['IFB-DLG 6.461 ∠ 26.494° Amps']]  
[['IFC-DLG 1.0 ∠ -84.289° Amps']  
['IFC-DLG 5.329 ∠ 165.651° Amps']  
['IFC-DLG 5.329 ∠ 25.77° Amps']]
```

Line-to-Line Results:

```
['IFA-DL 1.0 ∠ -84.289° Amps']  
['IFA-DL 6.634 ∠ -178.612° Amps']  
['IFA-DL 6.634 ∠ 10.034° Amps']]  
[['IFB-DL 1.0 ∠ -84.289° Amps']  
['IFB-DL 6.061 ∠ -179.022° Amps']  
['IFB-DL 6.061 ∠ 10.443° Amps']]  
[['IFC-DL 1.0 ∠ -84.289° Amps']  
['IFC-DL 5.03 ∠ -179.995° Amps']  
['IFC-DL 5.03 ∠ 11.416° Amps']]
```

Bolted (3-Phase) Results:

```
['IFA-Bolted 7.639 ∠ -84.289° Amps']  
['IFA-Bolted 7.639 ∠ 155.711° Amps']  
['IFA-Bolted 7.639 ∠ 35.711° Amps']]  
[['IFB-Bolted 6.975 ∠ -84.289° Amps']  
['IFB-Bolted 6.975 ∠ 155.711° Amps']  
['IFB-Bolted 6.975 ∠ 35.711° Amps']]  
[['IFC-Bolted 5.78 ∠ -84.289° Amps']  
['IFC-Bolted 5.78 ∠ 155.711° Amps']  
['IFC-Bolted 5.78 ∠ 35.711° Amps']]
```

In [121]:

```
1 # Calculate the Voltage at Bus S
2 #####
3
4 # Make Vsrc Matrix
5 Vsrc = [Vsrc_ln, Vsrc_ln*eeep.a**2, Vsrc_ln*eeep.a]
6
7 # Single Line to Ground Fault
8 print("SLG Results:")
9 eeep.cprint(Vsrc - ((IFA_slg + Iload) * Zsrc1), "Volts", "VFA-SLG:")
10 eeep.cprint(Vsrc - ((IFB_slg + Iload) * Zsrc1), "Volts", "VFB-SLG:")
11 eeep.cprint(Vsrc - ((IFC_slg + Iload) * Zsrc1), "Volts", "VFC-SLG:")
12 print()
13
14 # Double Line to Ground Fault
15 print("DLG Results:")
16 eeep.cprint(Vsrc - ((IFA_dlg + Iload) * Zsrc1), "Volts", "VFA-DLG:")
17 eeep.cprint(Vsrc - ((IFB_dlg + Iload) * Zsrc1), "Volts", "VFB-DLG:")
18 eeep.cprint(Vsrc - ((IFC_dlg + Iload) * Zsrc1), "Volts", "VFC-DLG:")
19 print()
20
21 # Double Line Fault
22 print("Line-to-Line Results:")
23 eeep.cprint(Vsrc - ((IFA_dl + Iload) * Zsrc1), "Volts", "VFA-DL:")
24 eeep.cprint(Vsrc - ((IFB_dl + Iload) * Zsrc1), "Volts", "VFB-DL:")
25 eeep.cprint(Vsrc - ((IFC_dl + Iload) * Zsrc1), "Volts", "VFC-DL:")
26 print()
27
28 # Bolted Fault
29 print("Bolted (3-Phase) Results:")
30 eeep.cprint(Vsrc - ((IFA_3 + Iload) * Zsrc1), "Volts", "VFA-Bolted:")
31 eeep.cprint(Vsrc - ((IFB_3 + Iload) * Zsrc1), "Volts", "VFB-Bolted:")
32 eeep.cprint(Vsrc - ((IFC_3 + Iload) * Zsrc1), "Volts", "VFC-Bolted:")
```

SLG Results:

```
['VFA-SLG: 58.571 ∠ 0.0° Volts']
['VFA-SLG: 110.038 ∠ -120.0° Volts']
['VFA-SLG: 110.038 ∠ 120.0° Volts']
['VFB-SLG: 65.004 ∠ 0.0° Volts']
['VFB-SLG: 110.038 ∠ -120.0° Volts']
['VFB-SLG: 110.038 ∠ 120.0° Volts']
['VFC-SLG: 75.727 ∠ 0.0° Volts']
['VFC-SLG: 110.038 ∠ -120.0° Volts']
['VFC-SLG: 110.038 ∠ 120.0° Volts']
```

DLG Results:

```
['VFA-DLG: 110.038 ∠ 0.0° Volts']
['VFA-DLG: 50.681 ∠ -132.245° Volts']
['VFA-DLG: 50.681 ∠ 132.245° Volts']
['VFB-DLG: 110.038 ∠ 0.0° Volts']
['VFB-DLG: 56.955 ∠ -130.521° Volts']
['VFB-DLG: 56.955 ∠ 130.521° Volts']
['VFC-DLG: 110.038 ∠ 0.0° Volts']
['VFC-DLG: 67.971 ∠ -127.817° Volts']
['VFC-DLG: 67.971 ∠ 127.817° Volts']
```

Line-to-Line Results:

```
['VFA-DL: 110.038 ∠ 0.0° Volts']
```

```
['VFA-DL: 66.593 ∠ -145.71° Volts']  
['VFA-DL: 66.593 ∠ 145.71° Volts']]  
[['VFB-DL: 110.038 ∠ 0.0° Volts']  
['VFB-DL: 70.011 ∠ -141.8° Volts']  
['VFB-DL: 70.011 ∠ 141.8° Volts']]  
[['VFC-DL: 110.038 ∠ 0.0° Volts']  
['VFC-DL: 76.878 ∠ -135.697° Volts']  
['VFC-DL: 76.878 ∠ 135.697° Volts']]
```

Bolted (3-Phase) Results:

```
[['VFA-Bolted: 43.322 ∠ 0.0° Volts']  
['VFA-Bolted: 43.322 ∠ -120.0° Volts']  
['VFA-Bolted: 43.322 ∠ 120.0° Volts']]  
[['VFB-Bolted: 49.993 ∠ 0.0° Volts']  
['VFB-Bolted: 49.993 ∠ -120.0° Volts']  
['VFB-Bolted: 49.993 ∠ 120.0° Volts']]  
[['VFC-Bolted: 62.002 ∠ 0.0° Volts']  
['VFC-Bolted: 62.002 ∠ -120.0° Volts']  
['VFC-Bolted: 62.002 ∠ 120.0° Volts']]
```

In [ ]:

1

In [ ]:

1