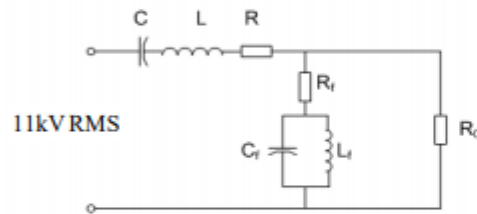


# Joe Stanley

## ECE 525 - Homework 3

I. For the capacitively coupled voltage transformer (CCVT, also known as a capacitive voltage transformer or CVT) circuit below do the following:

- Determine a Laplace domain transfer function for the relay voltage (the voltage across the load resistance  $R_0$ ) in response to a change in the input voltage. You might find the references linked with the CCVT lectures on the web page very useful.
- Plot the frequency response of the magnitude of the output voltage from 20Hz to 25th harmonic of 60Hz.
- Plot the responses for the output voltage versus time for the two sets of CCVT parameters listed below using a circuit simulation program when the primary voltage goes to zero due a fault occurring at a voltage peak with an ideal source. Determine analytical result for extra credit. You are encouraged to use a transient circuit simulation tool
- Plot the responses for the output voltage versus time for the two sets of CCVT parameters listed below using a circuit simulation program when the primary voltage goes to zero due a fault occurring at a voltage zero (again, ideal source). Determine analytical result for extra credit.



CCVT 1 (medium C (energy) CCVT )

$R_0 = 1.03997 \cdot 10^5$	— load resistance, $\Omega$
$L_f = 315.3$	— suppression inductance, H
$C_f = 0.0285 \cdot 10^{-6}$	— suppression capacitance, F
$R_f = 77379$	— suppression resistance, $\Omega$
$R = 3289$	— resistance, $\Omega$
$C = 9.1605 \cdot 10^{-6}$	— sum of dividing capacitances, F
$L = 76.136$	— inductance, H

CCVT 2 (high C (energy) CCVT )

$R_0 = 2.08584 \cdot 10^5$	— load resistance, $\Omega$
$L_f = 616.35$	— suppression inductance, H
$C_f = 0.01134 \cdot 10^{-6}$	— suppression capacitance, F
$R_f = 148519$	— suppression resistance, $\Omega$
$R = 1536$	— resistance, $\Omega$
$C = 0.162442 \cdot 10^{-6}$	— sum of dividing capacitances, F
$L = 48.136$	— inductance, H

```
In [1]: 1 # Import Supporting Libraries
        2 import numpy as np
        3 import matplotlib.pyplot as plt
        4 import eepower as eep
        5 import eesignal as ees
        6 from eepower import u,m,k,M # Unit scaling
```

A)

From the GE paper written by B. Kasztenny, D. Sharples, V. Asara and M. Pozzuli, we can see that the transfer function is:

$$H(s) = \frac{A_3 s^3 + A_2 s^2 + A_1 s}{B_4 s^4 + B_3 s^3 + B_2 s^2 + B_1 s + B_0}$$

where the terms are defined as:

$$A_3 = L_f C_f R_f R_0 C$$

$$A_2 = L_f R_0 C$$

$$A_1 = R_f R_0 C$$

$$B_4 = L_f C_f (R_f + R_0) L C$$

$$B_3 = L C L_f + R C L_f C_f (R_f + R_0) + L_f C_f R_f R_0 C$$

$$B_2 = L C (R_f + R_0) + R C L_f + L_f C_f (R_f + R_0) + L_f R_0 C$$

$$B_1 = R C (R_f + R_0) + L_f + R_f R_0 C$$


$$B_0 = R_f + R_0$$


In [2]:

```
1  # Define Function to Generate Transfer Function Terms
2  # Transfer function should be returned as:
3  # ([NUMERATOR],[DENOMINATOR])
4  # ie a tuple of lists describing each s-order term
5  def ccvtterms(Ro,Lf,Cf,Rf,R,C,L):
6      """
7      ccvtterms Function:
8
9      A simple function that accepts the specifying values that
10     define a capacitively coupled voltage transformer, and will
11     use the arguments to develop a transfer function set (numerator,
12     denominator) for use in Bode plot functions and other systems.
13
14     Returns
15     -----
16     num:      list of float
17              List of the numerator terms in traditional polynomial order.
18     den:      list of float
19              List of the denominator terms in traditional polynomial order.
20     """
21     # Define Each Term
22     A3 = Lf*Cf*Rf*Ro*C
23     A2 = Lf*Ro*C
24     A1 = Rf*Ro*C
25     A0 = 0
26     B4 = Lf*Cf*(Rf+Ro)*L*C
27     B3 = L*C*Lf+R*C*Lf*Cf*(Rf+Ro)+Lf*Cf*Rf*Ro*C
28     B2 = L*C*(Rf+Ro)+R*C*Lf+Lf*Cf*(Rf+Ro)+Lf*Ro*C
29     B1 = R*C*(Rf+Ro)+Lf+Rf*Ro*C
30     B0 = Rf+Ro
31     # Generate Term Lists for Transfer Function
32     num = [A3,A2,A1,A0]
33     den = [B4,B3,B2,B1,B0]
34     return(num,den)
```

In [3]:

```
1  # B) Plot Frequency Response
2
3  # Define Givens for CCVT 1
4  Ro = 1.03997e5 #  $\Omega$ 
5  Lf = 315.3     # H
6  Cf = 0.0285e-6 # F
7  Rf = 77379     #  $\Omega$ 
8  R = 3289       #  $\Omega$ 
9  C = 9.1605e-8  # F
10 L = 76.136     # H
11
12 # Generate Transfer Function
13 system = ccvttransterms(Ro,Lf,Cf,Rf,R,C,L)
14 # Use Function to generate Bode Plot
15 ees.bode(system,20,25*60,angle=False,freqaxis='DEG',title="Medium C")
16
17 # Define Givens for CCVT 2
18 Ro = 2.08584e5 #  $\Omega$ 
19 Lf = 616.35    # H
20 Cf = 0.01134e-6 # F
21 Rf = 148519    #  $\Omega$ 
22 R = 1536       #  $\Omega$ 
23 C = 0.162442e-6 # F
24 L = 48.136     # H
25
26 # Generate Transfer Function
27 system = ccvttransterms(Ro,Lf,Cf,Rf,R,C,L)
28 # Use Function to generate Bode Plot
29 ees.bode(system,20,25*60,angle=False,freqaxis='deg',title="High C")
```

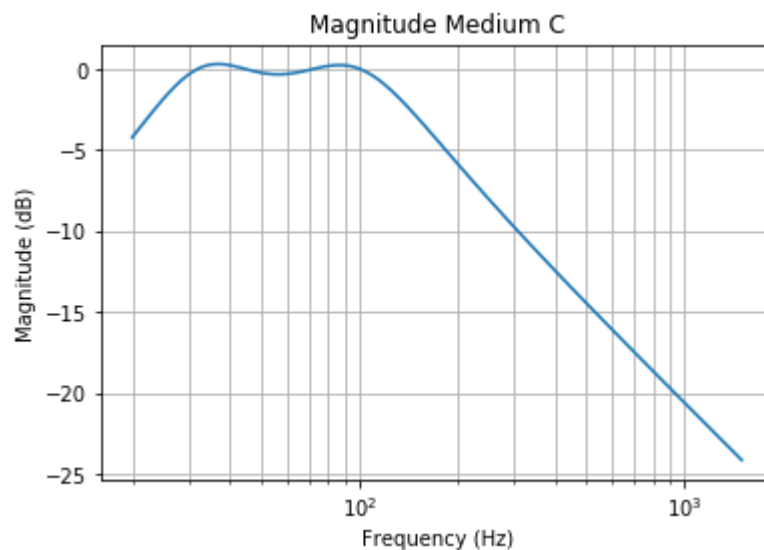

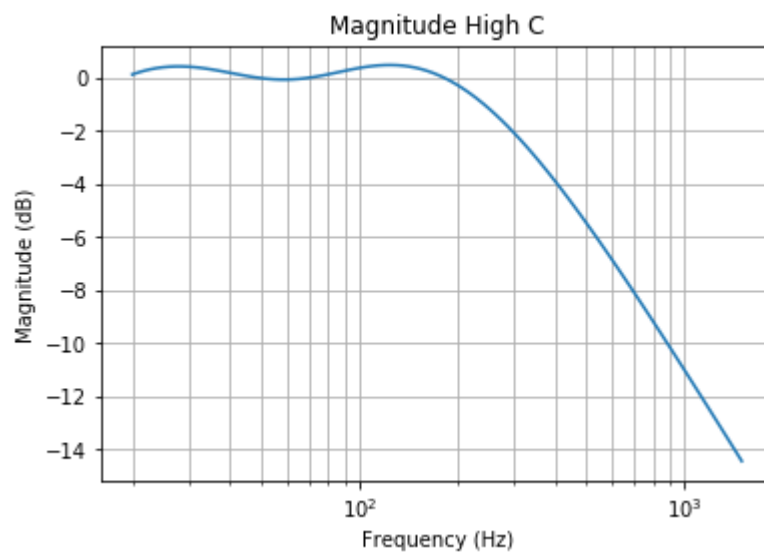


In [ ]:


1


In [ ]:

1

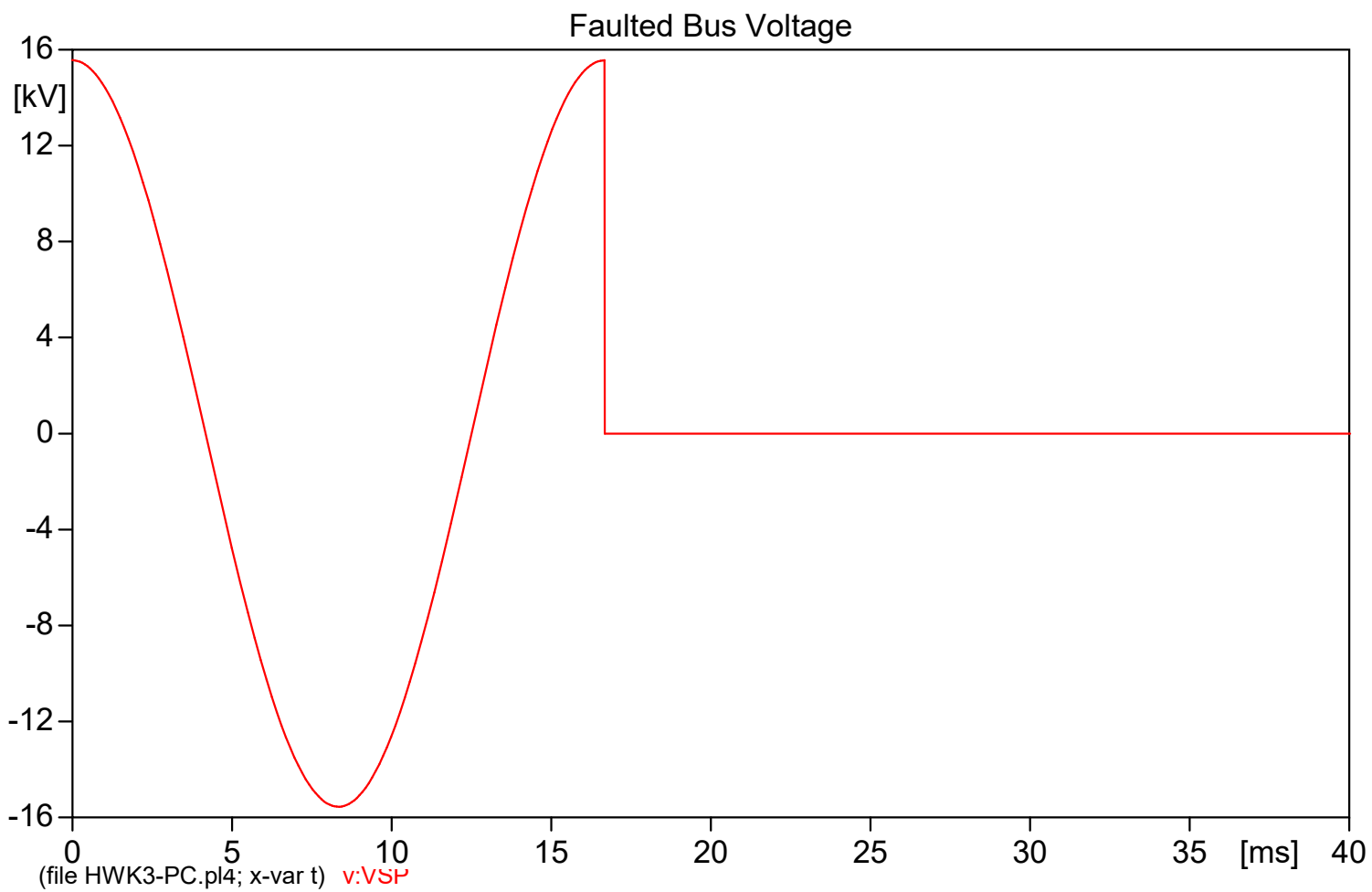

CCVT Output Voltages

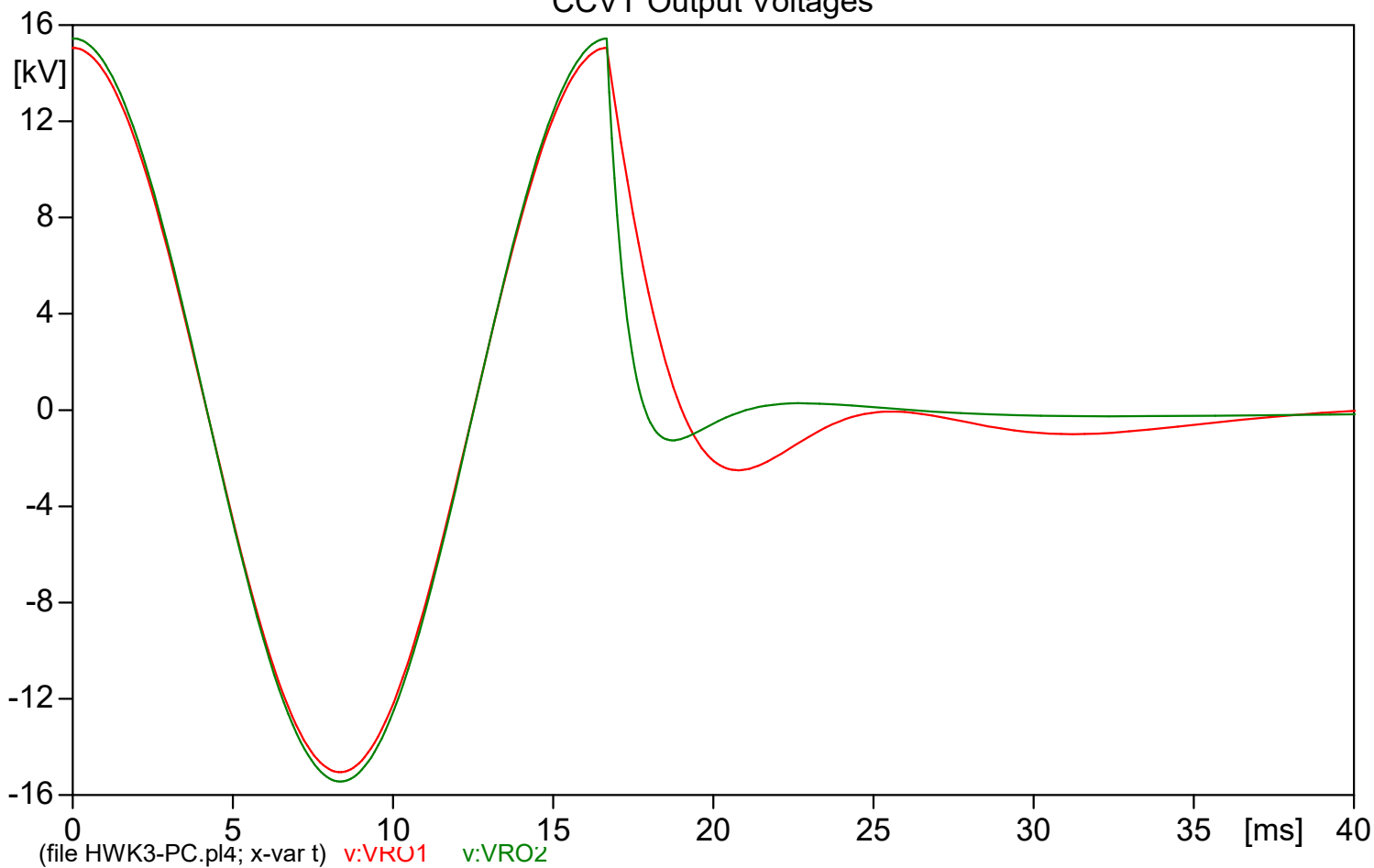

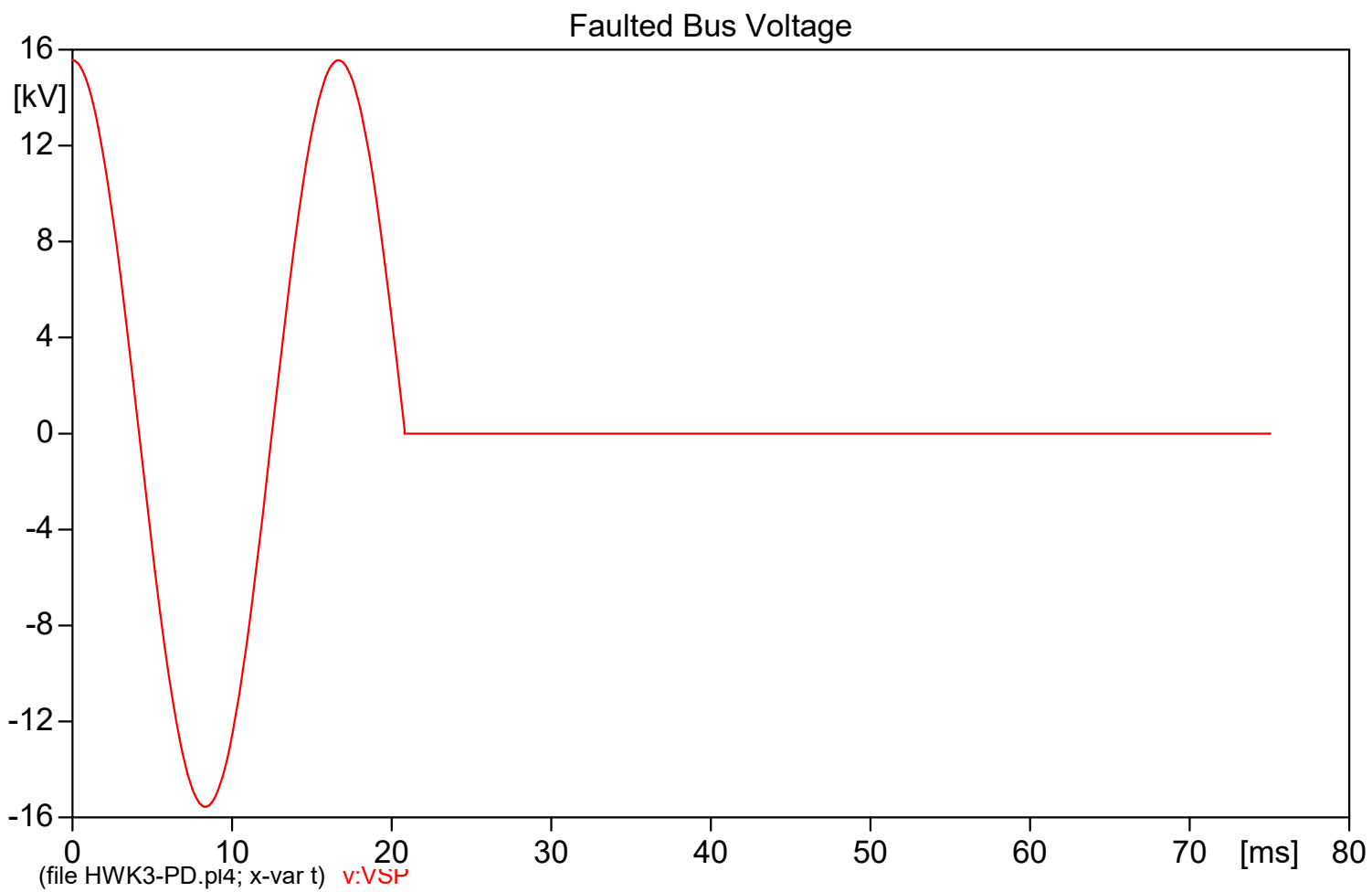

CCVT Output Voltages

