

Joe Stanley

ECE523 - HWK2

```
In [1]: 1 # Import Libraries
        2 import numpy as np
        3 import matplotlib.pyplot as plt
        4 import electricpy as ep
        5 from electricpy.constants import *
```

Problem 1:


Determine the symmetrical components for the following currents and sketch a phasor diagram, based on

- a) Phase "a" referenced components
- b) Phase "b" referenced components
- c) Phase "c" referenced components


In [8]:

```
1 # Define and Display Currents
2 currents = [[0,0],
3             [0,-120],
4             [2500,30]]
5 phs = ep.phasorlist(currents)
6 ep.cprint(phs,label=["IA","IB","IC"])
7
8 # a) "A"-Reference
9 symA = ep.abc_to_seq(phs)
10 ep.phasorplot(symA,legend=["I0","I1","I2"],title="A-Reference",
11               colors=["#0000FF","#00FF00","#FF0000"])
12 ep.cprint(symA,label=["I0","I1","I2"])
13 print()
14
15 # b) "B"-Reference
16 symB = ep.abc_to_seq(phs,"B")
17 ep.phasorplot(symB,legend=["I0","I1","I2"],title="B-Reference",
18               colors=["#0000FF","#00FF00","#FF0000"])
19 ep.cprint(symB,label=["I0","I1","I2"])
20 print()
21
22 # c) "C"-Reference
23 symC = ep.abc_to_seq(phs,"C")
24 ep.phasorplot(symC,legend=["I0","I1","I2"],title="C-Reference",
25               colors=["#0000FF","#00FF00","#FF0000"])
26 ep.cprint(symC,label=["I0","I1","I2"])
27 print()
```

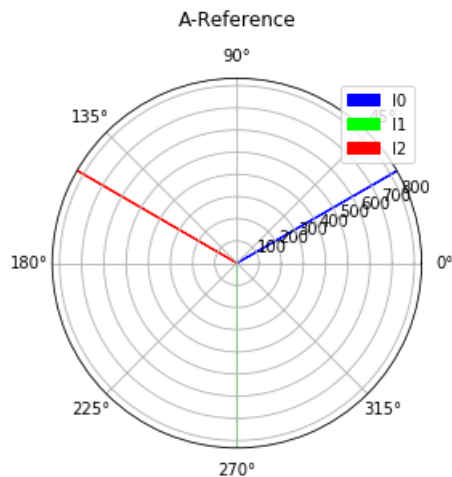
```
[['IA 0.0 ∠ 0.0°']
 ['IB 0.0 ∠ -180.0°']
 ['IC 2500.0 ∠ 30.0°']]
```


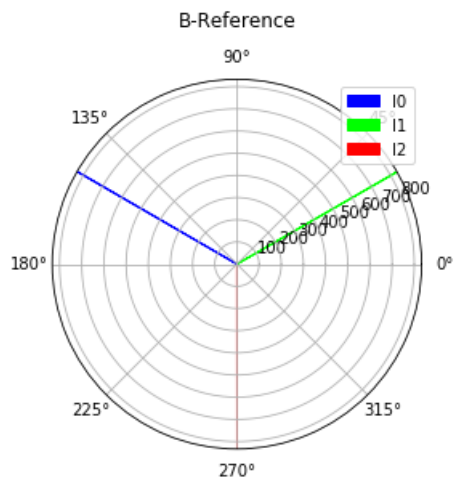
```
[['I0 833.333 ∠ 30.0°']
 ['I1 833.333 ∠ -90.0°']
 ['I2 833.333 ∠ 150.0°']]
```


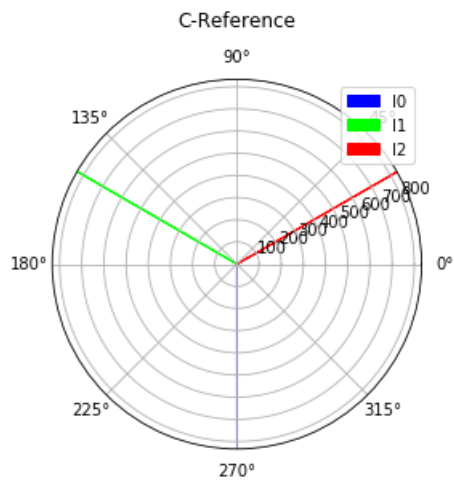
```
[['I0 833.333 ∠ 150.0°']
['I1 833.333 ∠ 30.0°']
['I2 833.333 ∠ -90.0°']]
```



```
[['I0 833.333 ∠ -90.0°']
['I1 833.333 ∠ 150.0°']
['I2 833.333 ∠ 30.0°']]
```


Problem 2:

Repeat problem 1. with the following currents:


In [9]:

```
1 # Define and Display Currents
2 currents = [[4500,-25.84],
3             [8503,-229.5],
4             [4500,94.16]]
5 phs = ep.phasorlist(currents)
6 ep.cprint(phs,label=["IA","IB","IC"])
7
8 # a) "A"-Reference
9 symA = ep.abc_to_seq(phs)
10 ep.phasorplot(symA,legend=["I0","I1","I2"],title="A-Reference",
11               colors=["#0000FF","#00FF00","#FF0000"])
12 ep.cprint(symA,label=["I0","I1","I2"])
13 print()
14
15 # b) "B"-Reference
16 symB = ep.abc_to_seq(phs,"B")
17 ep.phasorplot(symB,legend=["I0","I1","I2"],title="B-Reference",
18               colors=["#0000FF","#00FF00","#FF0000"])
19 ep.cprint(symB,label=["I0","I1","I2"])
20 print()
21
22 # c) "C"-Reference
23 symC = ep.abc_to_seq(phs,"C")
24 ep.phasorplot(symC,legend=["I0","I1","I2"],title="C-Reference",
25               colors=["#0000FF","#00FF00","#FF0000"])
26 ep.cprint(symC,label=["I0","I1","I2"])
27 print()
```

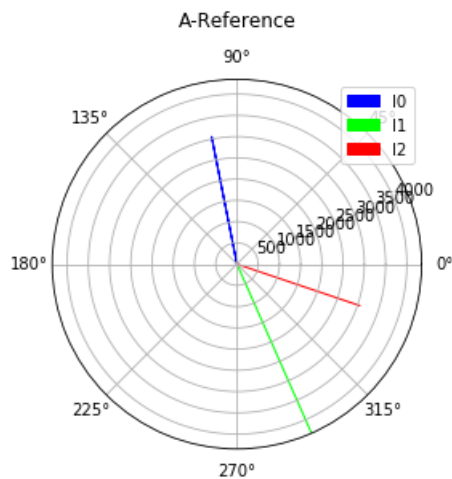
```
[['IA 4500.0 ∠ -25.84°']
 ['IB 8503.0 ∠ 130.5°']
 ['IC 4500.0 ∠ 94.16°']]
```


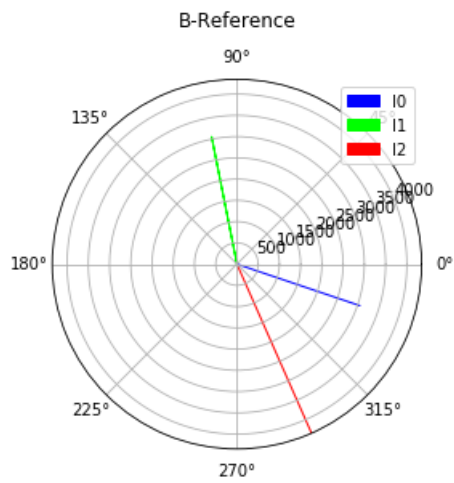
```
[['I0 3056.873 ∠ 101.311°']
 ['I1 4348.723 ∠ -66.214°']
 ['I2 3056.873 ∠ -18.689°']]
```


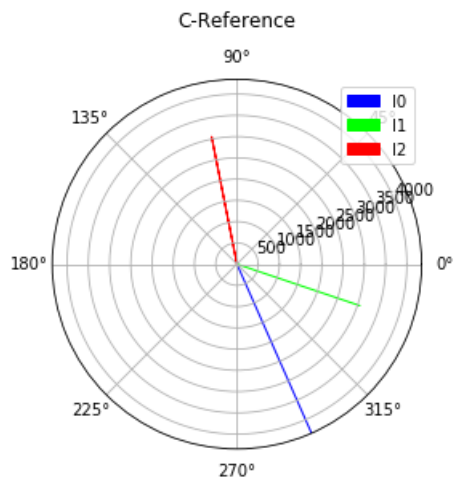
```
[['I0 3056.873 ∠ -18.689°']
['I1 3056.873 ∠ 101.311°']
['I2 4348.723 ∠ -66.214°']]
```



```
[['I0 4348.723 ∠ -66.214°']
['I1 3056.873 ∠ -18.689°']
['I2 3056.873 ∠ 101.311°']]
```

Problem 3:

Determine the phase voltage given the following phase "a" referenced symmetrical components. Repeat assuming they are instead phase "b" and then phase "c" referenced symmetrical components.

```


In [10]: 1 # Define Symmetrical Voltages
2 volt = [[0.274,-90],
3         [0.709,90],
4         [0.299,-90]]
5 seq = ep.phasorlist(volt)
6 ep.cprint(seq,label=["I0","I1","I2"])
7
8 # a) "A"-Reference
9 phsA = ep.seq_to_abc(seq)
10 ep.phasorplot(phsA,legend=["IA","IB","IC"],title="A-Reference",
11              colors=["#0000FF","#00FF00","#FF0000"])
12 ep.cprint(phsA,label=["IA","IB","IC"])
13 print()
14
15 # b) "B"-Reference
16 phsB = ep.seq_to_abc(seq,"B")
17 ep.phasorplot(phsB,legend=["IA","IB","IC"],title="B-Reference",
18              colors=["#0000FF","#00FF00","#FF0000"])
19 ep.cprint(phsB,label=["IA","IB","IC"])
20 print()
21
22 # c) "C"-Reference
23 phsC = ep.seq_to_abc(seq,"C")
24 ep.phasorplot(phsC,legend=["IA","IB","IC"],title="C-Reference",
25              colors=["#0000FF","#00FF00","#FF0000"])
26 ep.cprint(phsC,label=["IA","IB","IC"])
27 print()

```

```

[['I0 0.274 ∠ -90.0°']
 ['I1 0.709 ∠ 90.0°']
 ['I2 0.299 ∠ -90.0°']]


```

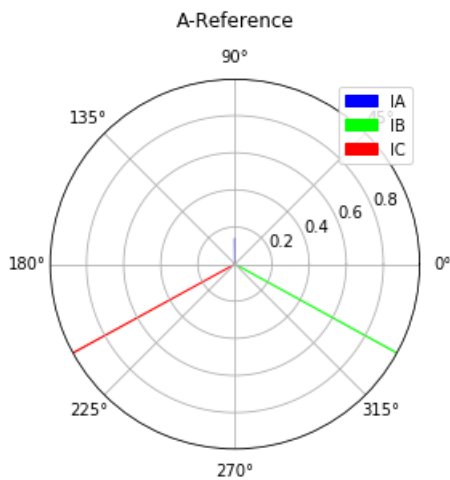


```

[['IA 0.136 ∠ 90.0°']
 ['IB 0.996 ∠ -28.754°']
 ['IC 0.996 ∠ -151.246°']]

```

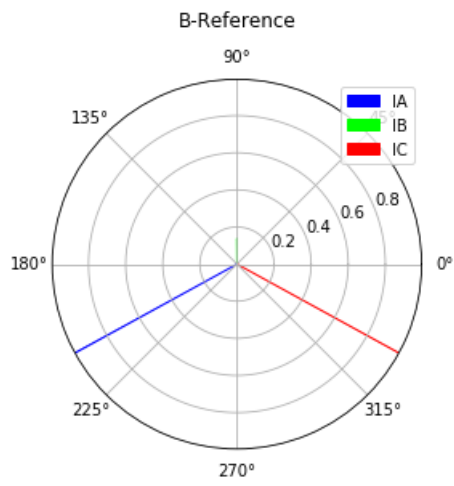
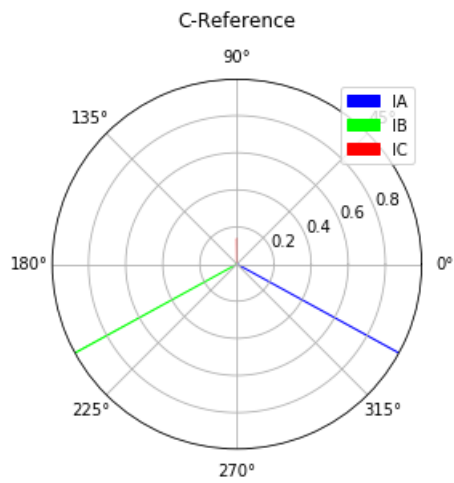
```
[['IA' 0.996 ∠ -151.246°']
['IB' 0.136 ∠ 90.0°']
['IC' 0.996 ∠ -28.754°']]
```



```
[['IA' 0.996 ∠ -28.754°']
['IB' 0.996 ∠ -151.246°']
['IC' 0.136 ∠ 90.0°']]
```

Problem 4: (text 2.10)

In [5]:

```
1 # Create Arbitrary Impedance (Load)
2 Zaa = 0.5+0.1j
3 Zbb = 0.74+0.15j
4 Zcc = 0.89+0.11j
5 Zab = 0.1+0.6j
6 Zbc = 0.11+0.58j
7 Zca = 0.12+0.56j
8 Zabc = np.array([[Zaa,Zab,Zca],
9                  [Zab,Zbb,Zbc],
10                 [Zca,Zbc,Zcc]])
11
12 # Evaluate Sequence Impedance
13 Z012 = ep.sequencez(Zabc)
14 print("Sequence Impedance:\n",Z012)
15
16 # Create Balanced Voltage Source
17 Vsrc = ep.phasorlist([[1,0],
18                      [1,-120],
19                      [1,120]])
20 V012 = ep.abc_to_seq(Vsrc)
21 print("\nSequence Voltages of Balanced Voltage Source:")
22 ep.cprint(V012,label=["V0","V1","V2"])
23
24 # Evaluate Sequence Currents
25 I012 = np.linalg.inv(Z012).dot(V012)
26 print("\nSequence Currents:")
27 ep.cprint(I012,label=["I0","I1","I2"])
28
29 # Evaluate Phase Currents
30 Iabc = ep.seq_to_abc(I012)
31 print("\nPhase Currents:")
32 ep.cprint(Iabc,label=["IA","IB","IC"])
33
34 # Determine Neutral Current
35 In = np.sum(Iabc)
36 print("\nNeutral Current:")
37 ep.cprint(In,label="In:")
38
39 # Determine 3*I0
40 I0_3 = 3*I012[0]
41 print("\nZero-Sequence Current:")
42 ep.cprint(I0_3,label="3*I0:")
43
44 # Demonstrate that Currents are Equal
45 ion = r"$$I_{0}-I_{n}="+ep.clatex(I0_3-In,double=True,predollar=False)
```

Sequence Impedance:

```
[[ 0.930+1.28j -0.082+0.039j -0.128-0.059j]
 [-0.128-0.059j  0.600-0.46j -0.117+0.022j]
 [-0.082+0.039j -0.093-0.042j  0.600-0.46j ]]
```

Sequence Voltages of Balanced Voltage Source:

```
['V0 0.0 ∠ 0.0°']
['V1 1.0 ∠ -0.0°']
['V2 0.0 ∠ 90.0°']]
```

Sequence Currents:

```
['I0 0.073 ∠ -29.092°']
['I1 1.338 ∠ 38.622°']
['I2 0.177 ∠ 97.877°']]
```

Phase Currents:

```
['IA 1.458 ∠ 41.934°']
['IB 1.472 ∠ -85.131°']
['IC 1.089 ∠ 159.259°']]
```

Neutral Current:

In: 0.219 ∠ -29.092°

Zero-Sequence Current:

3*I0: 0.219 ∠ -29.092°

This demonstrates that $I_n = I_0$ as shown below by their subtracted total:

$$I_0 - I_n = 0.0 \angle -17.103^\circ$$

Problem 5: (text 2.13)

```
In [6]: 1 # Define Givens
2 Vab = ep.phasor(1,30)
3 Vac = ep.phasor(1,-30)
4 Vbc = ep.phasor(1,-90)
5 Vca = Vac * 1j**2
6
7 # Determine Line-to-Neutral Voltages
8 Van = ep.phaseline(VLL=Vab,complex=True)
9 Vbn = ep.phaseline(VLL=Vbc,complex=True)
10 Vcn = ep.phaseline(VLL=Vca,complex=True)
11
12 # Generate Sequence Voltages
13 V012 = ep.abc_to_seq([Van,Vbn,Vcn])
14 ep.cprint(V012,label=["V0", "V1", "V2"])
15
16 # Create LaTeX String
17 Vtex = r'$$V_{012}='+ep.clatex(V012,predollar=False,double=True)

[['V0 0.0 ∠ -104.036°']
 ['V1 0.577 ∠ -0.0°']
 ['V2 0.0 ∠ 15.945°']]
```

Line-to-Neutral Voltages:

$$V_{012} = \begin{bmatrix} 0.0 \angle -104.036^\circ \\ 0.577 \angle -0.0^\circ \\ 0.0 \angle 15.945^\circ \end{bmatrix}$$

Problem 6:

```

In [7]: 1 # Define Givens
2 CTR_H = 500
3 CTR_L = 5
4 CTR = CTR_H/CTR_L
5 PHS_L = [[12,-87],
6          [4,-120],
7          [4,120]]
8 PHS_L = ep.phasorlist(PHS_L)
9
10 # a) Primary Currents
11 print("a) Primary Currents:")
12 PHS_H = ep.primary(PHS_L,CTR)
13 ep.cprint(PHS_H)
14
15 # b) Secondary Sequence Currents
16 print("\nb) Sequence Components:")
17 PHS_L_012 = ep.abc_to_seq(PHS_L)
18 ep.cprint(PHS_L_012,label=["I0","I1","I2"])
19
20 # c) Residual Current
21 print("\nc) Neutral Current:")
22 I_r = np.sum(PHS_L)
23 ep.cprint(I_r,label="Residual:")
24 ep.cprint(3*PHS_L_012[0],label="3*I0:\t ")
25
26 # d) Delta Currents
27 PHS_L_D = ep.phaseline(Iline=ep.secondary(PHS_L,CTR),complex=True)
28 PHS_L_D_012 = ep.abc_to_seq(PHS_L_D)
29 PHS_L_D_012[0] = 0 # Force Zero-Sequence to Zero
30 print("\nd) Sequence Currents:")
31 ep.cprint(PHS_L_D_012,label=["I0","I1","I2"])

```

a) Primary Currents:

```

[['1200.0 ∠ -87.0°']
 ['400.0 ∠ -120.0°']
 ['400.0 ∠ 120.0°']]

```

b) Sequence Components:

```

[['I0 4.15 ∠ -105.716°']
 ['I1 4.922 ∠ -54.247°']
 ['I2 4.15 ∠ -105.716°']]

```

c) Neutral Current:

```

Residual: 12.449 ∠ -105.716°
3*I0:      12.449 ∠ -105.716°

```

d) Sequence Currents:

```

[['I0 0.0 ∠ 0.0°']
 ['I1 0.028 ∠ -24.247°']
 ['I2 0.024 ∠ -75.716°']]

```

In []: 1