


Joe Stanley

HWK3 - ECE523

```
In [1]: 1 # Import Modules
2 import numpy as np
3 import matplotlib.pyplot as plt
4 from tabulate import tabulate
5 import electricpy as ep
6 from electricpy import fault as flt
7 from electricpy.constants import *
```

Problem 1:

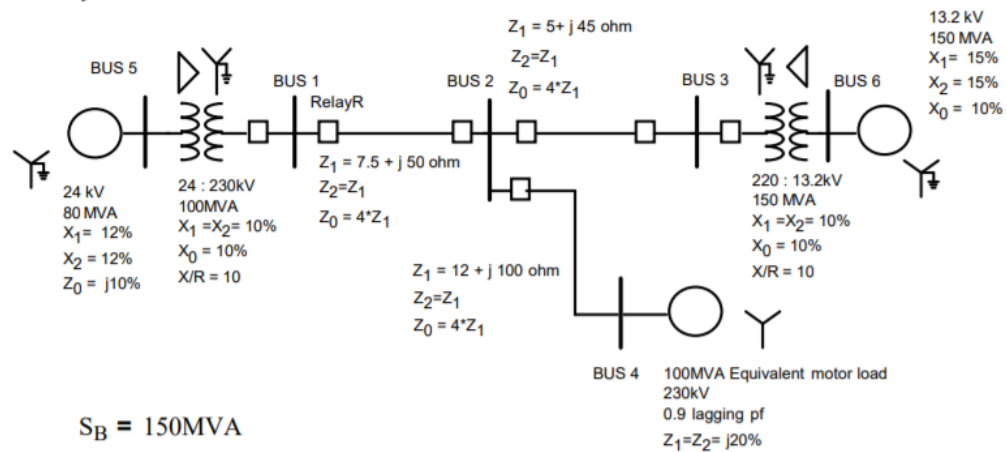1. Create positive, negative and zero sequence Ybus and Zbus matrices for the system below to study faults on the line between BUS 1 and BUS 2. Use $M=0.6$



$$S_B = 150\text{MVA}$$

Start voltage bases using rated voltage for the generator at BUS 5

In [2]:

```
1 # Define Per-Unit Bases
2 Sbase = 150*M
3 Vbase5 = 24*k
4 Vbase1234 = 230*k
5 Vbase6 = Vbase1234 *13.2/220
6 Zbase1234 = ep.zpu(Sbase,Vbase1234)
7
8 # Evaluate Per-Unit Line Impedances
9 Z12_1 = (7.5 + 50j)/Zbase1234
10 Z12_0 = 4*Z12_1
11 Z23_1 = (5 + 45j) /Zbase1234
12 Z23_0 = 4*Z23_1
13 Z24_1 = (12 + 100j)/Zbase1234
14 Z24_0 = 4*Z24_1
15 print("Z12:", np.around(Z12_1,3),
16       "\nZ23:", np.around(Z23_1,3),
17       "\nZ24:", np.around(Z24_1,3))
18
19 # Define System Terms
20 percent = 1/100
21 g5_x1 = 12j*percent
22 g5_x2 = g5_x1
23 g5_x0 = 10j*percent
24 t15_1 = ep.puchgbase(ep.rxrecompose(10*percent,10), ep.zpu(100*M, 230*k), Zbase1234)
25 t15_2 = t15_1
26 t15_0 = t15_1
27 g6_x1 = 15j*percent
28 g6_x2 = g6_x1
29 g6_x0 = 10j*percent
30 t36_1 = ep.puchgbase(ep.rxrecompose(10*percent,10), ep.zpu(150*M, 220*k), Zbase1234)
31 t36_2 = t36_1
32 t36_0 = t36_1
33 m4_x1 = 20j*percent
34 m4_x2 = m4_x1
35
36 # Since we're considering a fault at location M, we must create a
37 # fictitious bus for the location M. Let's Define two "new Lines"
38 Mdist = 0.6
39 Z1M_1 = Z12_1 * Mdist
40 Z1M_0 = Z12_0 * Mdist
41 ZM2_1 = Z12_1 * (1-Mdist)
42 ZM2_0 = Z12_0 * (1-Mdist)
43
44 # Define the Positive-Sequence Y-Bus Matrix, Will be 7x7 (include M bus)
45 ybus1 = np.array([
46     [1/(t15_1)+1/(Z1M_1), 0, 0, 0, -en30/(t15_1), 0, -1/(Z1M_1)],
47     [0, 1/(ZM2_1)+1/(Z23_1)+1/(Z24_1), -1/(Z23_1), -1/(Z24_1), 0, 0, -1/(ZM2_1)],
48     [0, -1/(Z23_1), 1/(Z23_1)+1/(t36_1), 0, 0, -en30/(t36_1), 0],
49     [0, -1/(Z24_1), 0, 1/(Z24_1)+1/(m4_x1), 0, 0, 0],
50     [-en30/(t15_1), 0, 0, 0, 1/(t15_1)+1/(g5_x1), 0, 0],
51     [0, 0, -en30/(t36_1), 0, 0, 1/(t36_1)+1/(g6_x1), 0],
52     [-1/(Z1M_1), -1/(ZM2_1), 0, 0, 0, 0, 1/(Z1M_1)+1/(ZM2_1)]
53 ])
54 zbus1 = np.linalg.inv(ybus1)
55 LATEXybus1 = ep.clatex(ybus1,round=1,polar=False,double=True)
56 LATEXzbus1 = ep.clatex(zbus1,polar=False,double=True)
57
58 # Define the Negative-Sequence Y-Bus Matrix
59 ybus2 = np.array([
60     [1/(t15_2)+1/(Z1M_1), 0, 0, 0, -en30/(t15_2), 0, -1/(Z1M_1)],
61     [0, 1/(ZM2_1)+1/(Z23_1)+1/(Z24_1), -1/(Z23_1), -1/(Z24_1), 0, 0, -1/(ZM2_1)],
62     [0, -1/(Z23_1), 1/(Z23_1)+1/(t36_2), 0, 0, -en30/(t36_2), 0],
63     [0, -1/(Z24_1), 0, 1/(Z24_1)+1/(m4_x2), 0, 0, 0],
64     [-en30/(t15_2), 0, 0, 0, 1/(t15_2)+1/(g5_x2), 0, 0],
65     [0, 0, -en30/(t36_2), 0, 0, 1/(t36_2)+1/(g6_x2), 0],
66     [-1/(Z1M_1), -1/(ZM2_1), 0, 0, 0, 0, 1/(Z1M_1)+1/(ZM2_1)]
67 ])
68 zbus2 = np.linalg.inv(ybus2)
69 LATEXybus2 = ep.clatex(ybus2,round=1,polar=False,double=True)
70 LATEXzbus2 = ep.clatex(zbus2,polar=False,double=True)
71
72 # Define the Zero-Sequence Y-Bus Matrix
73 ybus0 = np.array([
74     [1/(t15_0)+1/(Z1M_0), 0, 0, 0, 0, 0, -1/(Z1M_0)],
75     [0, 1/(ZM2_0)+1/(Z23_0)+1/(Z24_0), -1/(Z23_0), -1/(Z24_0), 0, 0, -1/(ZM2_0)],
76     [0, -1/(Z23_0), 1/(Z23_0)+1/(t36_0), 0, 0, 0, 0],
77     [0, -1/(Z24_0), 0, 1/(Z24_0), 0, 0, 0],
78     [0, 0, 0, 0, 1/(t15_0)+1/(g5_x0), 0, 0],
79     [0, 0, 0, 0, 0, 1/(t36_0)+1/(g6_x0), 0],
80     [-1/(Z1M_0), -1/(ZM2_0), 0, 0, 0, 0, 1/(Z1M_0)+1/(ZM2_0)]
81 ])
82 zbus0 = np.linalg.inv(ybus0)
83 LATEXybus0 = ep.clatex(ybus0,round=1,polar=False,double=True)
84 LATEXzbus0 = ep.clatex(zbus0,polar=False,double=True)
```

Z12: (0.021+0.142j)

Z23: (0.014+0.128j)

Positive Sequence:**Y-Bus Matrix:**

$$\begin{bmatrix} 2.4 - j18.1 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 2.7 + j6.0 & 0.0 - j0.0 & -1.7 + j11.5 \\ 0.0 - j0.0 & 3.9 - j28.5 & -0.9 + j7.7 & -0.4 + j3.5 & 0.0 - j0.0 & 0.0 - j0.0 & -2.6 + j17.2 \\ 0.0 - j0.0 & -0.9 + j7.7 & 1.9 - j18.6 & 0.0 - j0.0 & 0.0 - j0.0 & 4.5 + j9.9 & 0.0 - j0.0 \\ 0.0 - j0.0 & -0.4 + j3.5 & 0.0 - j0.0 & 0.4 - j8.5 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 \\ -3.9 + j5.4 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.7 - j14.9 & 0.0 - j0.0 & 0.0 - j0.0 \\ 0.0 - j0.0 & 0.0 - j0.0 & -6.3 + j8.8 & 0.0 - j0.0 & 0.0 - j0.0 & 1.1 - j17.5 & 0.0 - j0.0 \\ -1.7 + j11.5 & -2.6 + j17.2 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 4.3 - j28.7 \end{bmatrix}$$

Z-Bus Matrix:

$$\begin{bmatrix} 0.011 + j0.153 & 0.004 + j0.091 & 0.001 + j0.059 & -0.001 + j0.038 & 0.035 + j0.058 & 0.018 + j0.032 & 0.007 + j0.116 \\ 0.004 + j0.091 & 0.01 + j0.139 & 0.004 + j0.091 & 0.0 + j0.057 & 0.02 + j0.035 & 0.029 + j0.049 & 0.008 + j0.12 \\ 0.001 + j0.059 & 0.004 + j0.091 & 0.009 + j0.143 & -0.001 + j0.038 & 0.012 + j0.023 & 0.046 + j0.076 & 0.003 + j0.078 \\ -0.001 + j0.038 & 0.0 + j0.057 & -0.001 + j0.038 & 0.004 + j0.141 & 0.007 + j0.015 & 0.01 + j0.021 & -0.0 + j0.049 \\ -0.033 + j0.059 & -0.021 + j0.035 & -0.014 + j0.022 & -0.01 + j0.014 & 0.002 + j0.097 & -0.001 + j0.016 & -0.026 + j0.045 \\ -0.019 + j0.032 & -0.028 + j0.049 & -0.043 + j0.078 & -0.013 + j0.019 & -0.001 + j0.016 & 0.003 + j0.112 & -0.024 + j0.042 \\ 0.007 + j0.116 & 0.008 + j0.12 & 0.003 + j0.078 & -0.0 + j0.049 & 0.026 + j0.044 & 0.024 + j0.042 & 0.012 + j0.152 \end{bmatrix}$$

Negative Sequence:**Y-Bus Matrix:**

$$\begin{bmatrix} 2.4 - j18.1 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & -3.9 + j5.4 & 0.0 - j0.0 & -1.7 + j11.5 \\ 0.0 - j0.0 & 3.9 - j28.5 & -0.9 + j7.7 & -0.4 + j3.5 & 0.0 - j0.0 & 0.0 - j0.0 & -2.6 + j17.2 \\ 0.0 - j0.0 & -0.9 + j7.7 & 1.9 - j18.6 & 0.0 - j0.0 & 0.0 - j0.0 & -6.3 + j8.8 & 0.0 - j0.0 \\ 0.0 - j0.0 & -0.4 + j3.5 & 0.0 - j0.0 & 0.4 - j8.5 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 \\ 2.7 + j6.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.7 - j14.9 & 0.0 - j0.0 & 0.0 - j0.0 \\ 0.0 - j0.0 & 0.0 - j0.0 & 4.5 + j9.9 & 0.0 - j0.0 & 0.0 - j0.0 & 1.1 - j17.5 & 0.0 - j0.0 \\ -1.7 + j11.5 & -2.6 + j17.2 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 4.3 - j28.7 \end{bmatrix}$$

Z-Bus Matrix:

$$\begin{bmatrix} 0.011 + j0.153 & 0.004 + j0.091 & 0.001 + j0.059 & -0.001 + j0.038 & -0.033 + j0.059 & -0.019 + j0.032 & 0.007 + j0.116 \\ 0.004 + j0.091 & 0.01 + j0.139 & 0.004 + j0.091 & 0.0 + j0.057 & -0.021 + j0.035 & -0.028 + j0.049 & 0.008 + j0.12 \\ 0.001 + j0.059 & 0.004 + j0.091 & 0.009 + j0.143 & -0.001 + j0.038 & -0.014 + j0.022 & -0.043 + j0.078 & 0.003 + j0.078 \\ -0.001 + j0.038 & 0.0 + j0.057 & -0.001 + j0.038 & 0.004 + j0.141 & -0.01 + j0.014 & -0.013 + j0.019 & -0.0 + j0.049 \\ 0.035 + j0.058 & 0.02 + j0.035 & 0.012 + j0.023 & 0.007 + j0.015 & 0.002 + j0.097 & -0.001 + j0.016 & 0.026 + j0.044 \\ 0.018 + j0.032 & 0.029 + j0.049 & 0.046 + j0.076 & 0.01 + j0.021 & -0.001 + j0.016 & 0.003 + j0.112 & 0.024 + j0.042 \\ 0.007 + j0.116 & 0.008 + j0.12 & 0.003 + j0.078 & -0.0 + j0.049 & -0.026 + j0.045 & -0.024 + j0.042 & 0.012 + j0.152 \end{bmatrix}$$

Zero Sequence:**Y-Bus Matrix:**


$$\begin{bmatrix} 1.1 - j9.5 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & -0.4 + j2.9 \\ 0.0 - j0.0 & 1.0 - j7.1 & -0.2 + j1.9 & -0.1 + j0.9 & 0.0 - j0.0 & 0.0 - j0.0 & -0.6 + j4.3 \\ 0.0 - j0.0 & -0.2 + j1.9 & 1.3 - j12.8 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 \\ 0.0 - j0.0 & -0.1 + j0.9 & 0.0 - j0.0 & 0.1 - j0.9 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 \\ 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.7 - j16.6 & 0.0 - j0.0 & 0.0 - j0.0 \\ 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 1.1 - j20.8 & 0.0 - j0.0 \\ -0.4 + j2.9 & -0.6 + j4.3 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 1.1 - j7.2 \end{bmatrix}$$

Z-Bus Matrix:

$$\begin{bmatrix} 0.014 + j0.133 & 0.006 + j0.068 & 0.001 + j0.01 & 0.006 + j0.068 & 0.0 - j0.0 & 0.0 - j0.0 & 0.009 + j0.094 \\ 0.006 + j0.068 & 0.04 + j0.327 & 0.006 + j0.05 & 0.04 + j0.327 & 0.0 - j0.0 & 0.0 - j0.0 & 0.026 + j0.224 \\ 0.001 + j0.01 & 0.006 + j0.05 & 0.009 + j0.085 & 0.006 + j0.05 & 0.0 - j0.0 & 0.0 - j0.0 & 0.004 + j0.034 \\ 0.006 + j0.068 & 0.04 + j0.327 & 0.006 + j0.05 & 0.176 + j1.462 & 0.0 - j0.0 & 0.0 - j0.0 & 0.026 + j0.224 \\ 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.002 + j0.06 & 0.0 - j0.0 & 0.0 - j0.0 \\ 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.0 - j0.0 & 0.002 + j0.048 & 0.0 - j0.0 \\ 0.009 + j0.094 & 0.026 + j0.224 & 0.004 + j0.034 & 0.026 + j0.224 & 0.0 - j0.0 & 0.0 - j0.0 & 0.04 + j0.308 \end{bmatrix}$$

Problem 2:

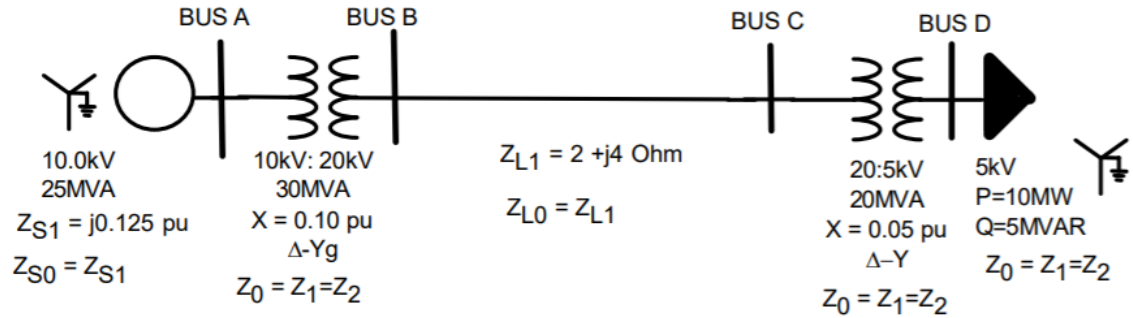2. Analyze the following faults. Use $S_{base}=25 \text{ MVA}$ and a voltage base of 5 kV at BUS D. You can neglect load current in your fault current calculations. Treat all buses as being at 1.0 pu magnitude prior to the fault.
- Three phase fault at Bus C. Find V and I at the fault location and at BUS A
 - SLG fault with $R_f=0$ at Bus C. Find V and I at the fault location and at BUS A
 - LL fault with $R_f=0$ at Bus C. Find V and I at the fault location and at BUS A
 - DLG fault with $R_f=R_g=0$ at Bus C, Find V and I at the fault location and at BUS A
 - Compare the fault current magnitudes and voltages between the different fault types, plus for faults at fault location at BUS B



```

In [3]: 1 # Define Per-Unit Bases
2 Sbase = 25*M
3 VbaseD = 5*k
4 VbaseBC = 20*k
5 VbaseA = 10*k
6 ZbaseBC = ep.zpu(Sbase,VbaseBC)
7
8 # Evaluate Load Impedance
9 Sload = 10*M + 5j*M
10 Zload = ep.powerimpedance(Sload,VbaseD)
11 print("Load Impedance:",np.around(Zload,3))
12
13 # Set Impedances in Appropriate Base
14 Zsrc = 0.125j
15 tab_1 = ep.puchgbase(0.10j,ep.zpu(30*M,20*k),ZbaseBC)
16 tcd_1 = ep.puchgbase(0.05j,ep.zpu(20*M,20*k),ZbaseBC)
17 Zline = (2+4j) / ZbaseBC
18 print("Transformer 1:",tab_1,
19       "\nTransformer 2:",tcd_1,
20       "\nZline:",Zline)
21
22 # Evaluate the Z-Bus Matricies
23 zbus1 = np.linalg.inv(np.array([
24     [1/Zsrc+1/tab_1, -e30/tab_1, 0, 0],
25     [-en30/tab_1, 1/tab_1+1/Zline, -1/Zline, 0],
26     [0, -1/Zline, 1/Zline+1/tcd_1, -e30/tcd_1],
27     [0, 0, -en30/tcd_1, 1/tcd_1+1/Zload]
28 ]))
29 zbus2 = np.linalg.inv(np.array([
30     [1/Zsrc+1/tab_1, -e30/tab_1, 0, 0],
31     [-e30/tab_1, 1/tab_1+1/Zline, -1/Zline, 0],
32     [0, -1/Zline, 1/Zline+1/tcd_1, -en30/tcd_1],
33     [0, 0, -e30/tcd_1, 1/tcd_1+1/Zload]
34 ]))
35 zbus0 = np.linalg.inv(np.array([
36     [1/Zsrc, 0, 0, 0],
37     [0, 1/tab_1+1/Zline, -1/Zline, 0],
38     [0, -1/Zline, 1/Zline+1/tcd_1, 0],
39     [0, 0, 0, 1/Zload]
40 ]))
41 print("\nPositive Sequence Z-Bus:")
42 print(tabulate(np.asarray(np.around(zbus1,3),dtype=str),tablefmt="fancy_grid"))
43 print("\nNegative Sequence Z-Bus:")
44 print(tabulate(np.asarray(np.around(zbus2,3),dtype=str),tablefmt="fancy_grid"))
45 print("\nZero Sequence Z-Bus:")
46 print(tabulate(np.asarray(np.around(zbus0,3),dtype=str),tablefmt="fancy_grid"))

```

Load Impedance: (2.5+5j)
Transformer 1: 0.08333333333333334j
Transformer 2: 0.0625j
Zline: (0.125+0.25j)

Positive Sequence Z-Bus:

(0.001+0.123j)	(-0.059+0.106j)	(-0.056+0.101j)	(-0.098+0.059j)
(0.062+0.104j)	(0.003+0.202j)	(0.003+0.192j)	(-0.092+0.167j)
(0.059+0.099j)	(0.003+0.192j)	(0.122+0.422j)	(-0.102+0.422j)
(0.1+0.055j)	(0.099+0.163j)	(0.315+0.3j)	(0.124+0.474j)

Negative Sequence Z-Bus:

(0.001+0.123j)	(0.062+0.104j)	(0.059+0.099j)	(0.1+0.055j)
(-0.059+0.106j)	(0.003+0.202j)	(0.003+0.192j)	(0.099+0.163j)
(-0.056+0.101j)	(0.003+0.192j)	(0.122+0.422j)	(0.315+0.3j)
(-0.098+0.059j)	(-0.092+0.167j)	(-0.102+0.422j)	(0.124+0.474j)

Zero Sequence Z-Bus:

0.125j	0j	0j	0j
0j	(0.005+0.067j)	(-0.004+0.012j)	0j
0j	(-0.004+0.012j)	(0.003+0.054j)	0j
0j	0j	0j	(2.5+5j)

```

In [4]: 1 # Evaluate The Thevenin Set For Fault Calculations
2 Zth = [zbus0[3,3],zbus1[3,3],zbus2[3,3]]
3 print("Sequence Impedances at Bus C:",np.around(Zth,3))
4
5 # A) Three-Phase
6 I012 = flt.phs3(1,Zth)
7 VA = flt.busvolt(1,3,1,zbus0,zbus1,zbus2,I012,sequence=False)
8 VC = flt.busvolt(3,3,1,zbus0,zbus1,zbus2,I012,sequence=False)
9 print("\nThree-Phase Fault")
10 ep.cprint(ep.seq_to_phs(I012),"A",label=["IA","IB","IC"])
11 ep.cprint(VA,"V",["A-VA","A-VB","A-VC"])
12 ep.cprint(VC,"V",["C-VA","C-VB","C-VC"])
13
14 # B) SLG Fault:
15 I012 = flt.phs1g(1,Zth)
16 VA = flt.busvolt(1,3,1,zbus0,zbus1,zbus2,I012,sequence=False)
17 VC = flt.busvolt(3,3,1,zbus0,zbus1,zbus2,I012,sequence=False)
18 print("\nSingle-Line-to-Ground Fault")
19 ep.cprint(ep.seq_to_phs(I012),"A",label=["IA","IB","IC"])
20 ep.cprint(VA,"V",["A-VA","A-VB","A-VC"])
21 ep.cprint(VC,"V",["C-VA","C-VB","C-VC"])
22
23 # C) LL Fault:
24 I012 = flt.phs2(1,Zth)
25 VA = flt.busvolt(1,3,1,zbus0,zbus1,zbus2,I012,sequence=False)
26 VC = flt.busvolt(3,3,1,zbus0,zbus1,zbus2,I012,sequence=False)
27 print("\nLine-to-Line Fault")
28 ep.cprint(ep.seq_to_phs(I012),"A",label=["IA","IB","IC"])
29 ep.cprint(VA,"V",["A-VA","A-VB","A-VC"])
30 ep.cprint(VC,"V",["C-VA","C-VB","C-VC"])
31
32 # D) DLG Fault:
33 I012 = flt.phs2g(1,Zth)
34 VA = flt.busvolt(1,3,1,zbus0,zbus1,zbus2,I012,sequence=False)
35 VC = flt.busvolt(3,3,1,zbus0,zbus1,zbus2,I012,sequence=False)
36 print("\nDouble-Line-to-Ground Fault")
37 ep.cprint(ep.seq_to_phs(I012),"A",label=["IA","IB","IC"])
38 ep.cprint(VA,"V",["A-VA","A-VB","A-VC"])
39 ep.cprint(VC,"V",["C-VA","C-VB","C-VC"])

```

Sequence Impedances at Bus C: [2.500+5.j 0.124+0.474j 0.124+0.474j]

Three-Phase Fault

```

[['IA 2.042 ∠ -75.369° A']
 ['IB 2.042 ∠ 164.631° A']
 ['IC 2.042 ∠ 44.631° A']]
[['A-VA 0.846 ∠ -11.119° V']
 ['A-VB 0.846 ∠ -131.119° V']
 ['A-VC 0.846 ∠ 108.881° V']]
[['C-VA 0.107 ∠ 12.454° V']
 ['C-VB 0.107 ∠ -107.546° V']
 ['C-VC 0.107 ∠ 132.454° V']]

```

Single-Line-to-Ground Fault

```

[['IA 0.458 ∠ -65.207° A']
 ['IB 0.0 ∠ 45.0° A']
 ['IC 0.0 ∠ 56.31° A']]
[['A-VA 0.972 ∠ -0.73° V']
 ['A-VB 1.0 ∠ -120.0° V']
 ['A-VC 0.997 ∠ 118.256° V']]
[['C-VA 0.86 ∠ -1.549° V']
 ['C-VB 0.966 ∠ -117.198° V']
 ['C-VC 0.978 ∠ 116.819° V']]

```

Line-to-Line Fault

```

[['IA 0.0 ∠ 0.0° A']
 ['IB 1.768 ∠ -165.369° A']
 ['IC 1.768 ∠ 14.631° A']]
[['A-VA 1.034 ∠ -6.353° V']
 ['A-VB 0.846 ∠ -131.119° V']
 ['A-VC 0.887 ∠ 122.126° V']]
[['C-VA 1.0 ∠ -0.0° V']
 ['C-VB 0.488 ∠ -169.327° V']
 ['C-VC 0.528 ∠ 170.13° V']]

```

Double-Line-to-Ground Fault

```

[['IA 0.0 ∠ -67.38° A']
 ['IB 1.798 ∠ -169.39° A']
 ['IC 1.747 ∠ 18.77° A']]
[['A-VA 1.027 ∠ -6.603° V']
 ['A-VB 0.846 ∠ -131.119° V']
 ['A-VC 0.886 ∠ 121.576° V']]
[['C-VA 0.967 ∠ -0.279° V']
 ['C-VB 0.465 ∠ -169.419° V']
 ['C-VC 0.506 ∠ 169.125° V']]

```

```

In [5]: 1 # Evaluate The Thevenin Set For Fault Calculations
2 Zth = [zbus0[2,2],zbus1[2,2],zbus2[2,2]]
3 print("Sequence Impedances at Bus B:",np.around(Zth,3))
4
5 # A) Three-Phase
6 I012 = flt.phs3(1,Zth)
7 VA = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
8 VC = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
9 print("\nThree-Phase Fault")
10 ep.cprint(ep.seq_to_phs(I012),"A",label=["IA","IB","IC"])
11 ep.cprint(VA,"V",["A-VA","A-VB","A-VC"])
12 ep.cprint(VC,"V",["C-VA","C-VB","C-VC"])
13
14 # B) SLG Fault:
15 I012 = flt.phs1g(1,Zth)
16 VA = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
17 VC = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
18 print("\nSingle-Line-to-Ground Fault")
19 ep.cprint(ep.seq_to_phs(I012),"A",label=["IA","IB","IC"])
20 ep.cprint(VA,"V",["A-VA","A-VB","A-VC"])
21 ep.cprint(VC,"V",["C-VA","C-VB","C-VC"])
22
23 # C) LL Fault:
24 I012 = flt.phs2(1,Zth)
25 VA = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
26 VC = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
27 print("\nLine-to-Line Fault")
28 ep.cprint(ep.seq_to_phs(I012),"A",label=["IA","IB","IC"])
29 ep.cprint(VA,"V",["A-VA","A-VB","A-VC"])
30 ep.cprint(VC,"V",["C-VA","C-VB","C-VC"])
31
32 # D) DLG Fault:
33 I012 = flt.phs2g(1,Zth)
34 VA = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
35 VC = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
36 print("\nDouble-Line-to-Ground Fault")
37 ep.cprint(ep.seq_to_phs(I012),"A",label=["IA","IB","IC"])
38 ep.cprint(VA,"V",["A-VA","A-VB","A-VC"])
39 ep.cprint(VC,"V",["C-VA","C-VB","C-VC"])

```

Sequence Impedances at Bus B: [0.003+0.054j 0.122+0.422j 0.122+0.422j]

Three-Phase Fault

```

[['IA 2.279 ∠ -73.893° A']
 ['IB 2.279 ∠ 166.107° A']
 ['IC 2.279 ∠ 46.107° A']]
[['A-VA 0.829 ∠ -13.68° V']
 ['A-VB 0.829 ∠ -133.68° V']
 ['A-VC 0.829 ∠ 106.32° V']]
[['C-VA 0.569 ∠ -12.278° V']
 ['C-VB 0.569 ∠ -132.278° V']
 ['C-VC 0.569 ∠ 107.722° V']]

```

Single-Line-to-Ground Fault

```

[['IA 3.226 ∠ -74.641° A']
 ['IB 0.0 ∠ 33.69° A']
 ['IC 0.0 ∠ 36.87° A']]
[['A-VA 0.784 ∠ -4.134° V']
 ['A-VB 1.0 ∠ -120.0° V']
 ['A-VC 0.965 ∠ 106.968° V']]
[['C-VA 0.523 ∠ -13.573° V']
 ['C-VB 0.901 ∠ -113.619° V']
 ['C-VC 0.976 ∠ 111.718° V']]

```

Line-to-Line Fault

```

[['IA 0.0 ∠ 0.0° A']
 ['IB 1.974 ∠ -163.893° A']
 ['IC 1.974 ∠ 16.107° A']]
[['A-VA 1.045 ∠ -7.325° V']
 ['A-VB 0.829 ∠ -133.68° V']
 ['A-VC 0.867 ∠ 122.324° V']]
[['C-VA 1.0 ∠ -0.0° V']
 ['C-VB 0.773 ∠ -141.477° V']
 ['C-VC 0.623 ∠ 129.381° V']]

```

Double-Line-to-Ground Fault


```

[['IA 0.0 ∠ 75.964° A']
 ['IB 3.32 ∠ 139.989° A']
 ['IC 3.463 ∠ 68.842° A']]
[['A-VA 0.866 ∠ -11.698° V']
 ['A-VB 0.829 ∠ -133.68° V']
 ['A-VC 0.823 ∠ 109.561° V']]
[['C-VA 0.763 ∠ -4.627° V']
 ['C-VB 0.517 ∠ -125.583° V']
 ['C-VC 0.55 ∠ 99.569° V']]

```

Problem 3:

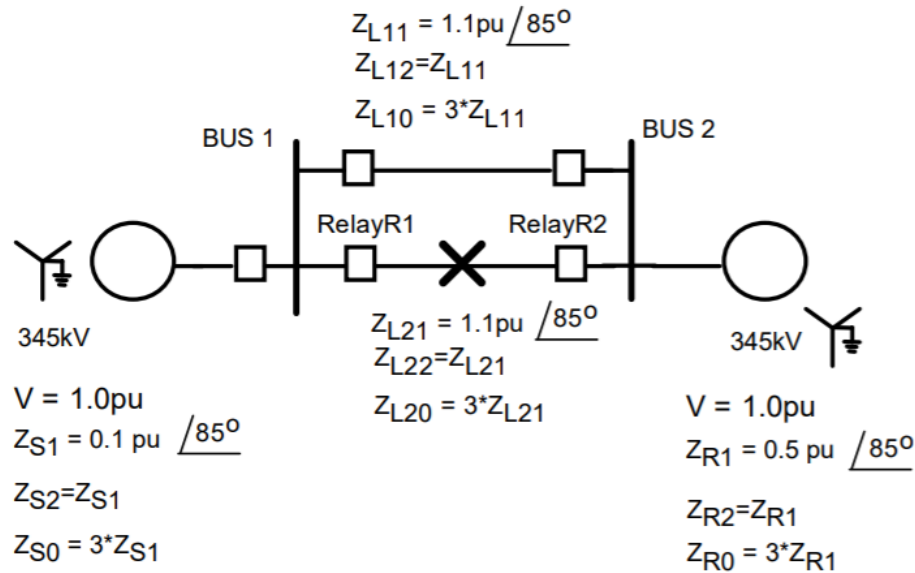3. Do the following for the circuit below. **Also check your results with a commercial fault program and show comparison in tables.**
- Calculate and sketch the positive, negative and zero sequence equivalent circuits based on a fault 40% of the way down line 2 (the lower of the two lines).
 - Calculate the voltages and currents at RelayR1 and RelayR2, for SLG, LL, and DLG faults with $R_f = 0$. I recommend using Zbus matrix methods.
 - Repeat the part (b) for a SLG fault, LL, and DLG with $R_f = 0.75$ pu. For the DLG put the fault resistance in the neutral to ground path.




```

In [16]: 1 # Define Impedances
2 zs1 = ep.phasor(0.1,85)
3 z11 = ep.phasor(1.1,85)
4 z113 = ep.phasor(1.1,85)*0.4
5 z132 = ep.phasor(1.1,85)*0.6
6 zr1 = ep.phasor(0.5,85)
7 Rf = 0.75
8
9 # Generate Sequence Impedance Busses
10 zbus1 = np.linalg.inv(np.array([
11     [1/zs1+1/z11+1/z113, -1/z11, -1/z113],
12     [-1/z11, 1/z11+1/z132+1/zr1, -1/z132],
13     [-1/z113, -1/z132, 1/z113+1/z132]
14 ]))
15 zbus2 = zbus1
16 zbus0 = np.linalg.inv(np.array([
17     [1/(zs1*3)+1/(z11*3)+1/(z113*3), -1/(z11*3), -1/(z113*3)],
18     [-1/(z11*3), 1/(z11*3)+1/(z132*3)+1/(zr1*3), -1/(z132*3)],
19     [-1/(z113*3), -1/(z132*3), 1/(z113*3)+1/(z132*3)]
20 ]))
21 print("\nPositive Sequence Z-Bus:")
22 print(tabulate(np.asarray(np.around(zbus1,3),dtype=str),tablefmt="fancy_grid"))
23 print("\nNegative Sequence Z-Bus:")
24 print(tabulate(np.asarray(np.around(zbus2,3),dtype=str),tablefmt="fancy_grid"))
25 print("\nZero Sequence Z-Bus:")
26 print(tabulate(np.asarray(np.around(zbus0,3),dtype=str),tablefmt="fancy_grid"))

```

Positive Sequence Z-Bus:

(0.008+0.091j)	(0.004+0.043j)	(0.006+0.072j)
(0.004+0.043j)	(0.025+0.282j)	(0.012+0.139j)
(0.006+0.072j)	(0.012+0.139j)	(0.032+0.362j)

Negative Sequence Z-Bus:

(0.008+0.091j)	(0.004+0.043j)	(0.006+0.072j)
(0.004+0.043j)	(0.025+0.282j)	(0.012+0.139j)
(0.006+0.072j)	(0.012+0.139j)	(0.032+0.362j)

Zero Sequence Z-Bus:

(0.024+0.273j)	(0.011+0.13j)	(0.019+0.216j)
(0.011+0.13j)	(0.074+0.845j)	(0.036+0.416j)
(0.019+0.216j)	(0.036+0.416j)	(0.095+1.085j)

In [17]:

```
1 # Evaluate The Thevenin Set For Fault Calculations
2 Zth = [zbus0[2,2],zbus1[2,2],zbus2[2,2]]
3 print("Sequence Impedances at Bus B:",np.around(Zth,3))
4
5 # Evaluate Sequence Currents and Fault Voltages for SLG
6 I012 = flt.phs1g(1,Zth)
7 Vfault = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
8 Vrly1 = flt.busvolt(0,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
9 Vrly2 = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
10 print("\nSingle Line to Ground:")
11 ep.cprint(Vrly1,"V",["Relay1 VA:", "Relay1 VB:", "Relay1 VC:"])
12 ep.cprint((Vrly1-Vfault)/z113,"A",["Relay1 IA:", "Relay1 IB:", "Relay1 IC:"])
13 ep.cprint(Vrly2,"V",["Relay2 VA:", "Relay2 VB:", "Relay2 VC:"])
14 ep.cprint((Vrly2-Vfault)/z132,"A",["Relay2 IA:", "Relay2 IB:", "Relay2 IC:"])
15
16 # Evaluate Sequence Currents and Fault Voltages for LL
17 I012 = flt.phs2(1,Zth)
18 Vfault = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
19 Vrly1 = flt.busvolt(0,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
20 Vrly2 = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
21 print("\nLine to Line:")
22 ep.cprint(Vrly1,"V",["Relay1 VA:", "Relay1 VB:", "Relay1 VC:"])
23 ep.cprint((Vrly1-Vfault)/z113,"A",["Relay1 IA:", "Relay1 IB:", "Relay1 IC:"])
24 ep.cprint(Vrly2,"V",["Relay2 VA:", "Relay2 VB:", "Relay2 VC:"])
25 ep.cprint((Vrly2-Vfault)/z132,"A",["Relay2 IA:", "Relay2 IB:", "Relay2 IC:"])
26
27 # Evaluate Sequence Currents and Fault Voltages for DLG
28 I012 = flt.phs2g(1,Zth)
29 Vfault = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
30 Vrly1 = flt.busvolt(0,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
31 Vrly2 = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
32 print("\nDouble Line to Ground:")
33 ep.cprint(Vrly1,"V",["Relay1 VA:", "Relay1 VB:", "Relay1 VC:"])
34 ep.cprint((Vrly1-Vfault)/z113,"A",["Relay1 IA:", "Relay1 IB:", "Relay1 IC:"])
35 ep.cprint(Vrly2,"V",["Relay2 VA:", "Relay2 VB:", "Relay2 VC:"])
36 ep.cprint((Vrly2-Vfault)/z132,"A",["Relay2 IA:", "Relay2 IB:", "Relay2 IC:"])
```

Sequence Impedances at Bus B: [0.095+1.085j 0.032+0.362j 0.032+0.362j]

Single Line to Ground:

```
['Relay1 VA: 0.617 ∠ 0.0° V']
['Relay1 VB: 1.085 ∠ -127.031° V']
['Relay1 VC: 1.085 ∠ 127.031° V']
['Relay1 IA: 0.898 ∠ -85.0° A']
['Relay1 IB: 0.359 ∠ -85.0° A']
['Relay1 IC: 0.359 ∠ -85.0° A']
['Relay2 VA: 0.88 ∠ -0.0° V']
['Relay2 VB: 1.025 ∠ -122.321° V']
['Relay2 VC: 1.025 ∠ 122.321° V']
['Relay2 IA: 0.998 ∠ -85.0° A']
['Relay2 IB: 0.399 ∠ -85.0° A']
['Relay2 IC: 0.399 ∠ -85.0° A']
```

Line to Line:

```
['Relay1 VA: 1.0 ∠ 0.0° V']
['Relay1 VB: 0.732 ∠ -133.114° V']
['Relay1 VC: 0.732 ∠ 133.114° V']
['Relay1 IA: 0.0 ∠ 0.0° A']
['Relay1 IB: 0.778 ∠ -175.0° A']
['Relay1 IC: 0.778 ∠ 5.0° A']
['Relay2 VA: 1.0 ∠ 0.0° V']
['Relay2 VB: 0.912 ∠ -123.262° V']
['Relay2 VC: 0.912 ∠ 123.262° V']
['Relay2 IA: 0.0 ∠ 0.0° A']
['Relay2 IB: 0.865 ∠ -175.0° A']
['Relay2 IC: 0.865 ∠ 5.0° A']
```

Double Line to Ground:

```
['Relay1 VA: 1.11 ∠ -0.0° V']
['Relay1 VB: 0.617 ∠ -120.0° V']
['Relay1 VC: 0.617 ∠ 120.0° V']
['Relay1 IA: 0.257 ∠ 95.0° A']
['Relay1 IB: 0.898 ∠ 155.0° A']
['Relay1 IC: 0.898 ∠ 35.0° A']
['Relay2 VA: 1.034 ∠ -0.0° V']
['Relay2 VB: 0.88 ∠ -120.0° V']
['Relay2 VC: 0.88 ∠ 120.0° V']
['Relay2 IA: 0.285 ∠ 95.0° A']
['Relay2 IB: 0.998 ∠ 155.0° A']
['Relay2 IC: 0.998 ∠ 35.0° A']
```

```

In [18]: 1 # Evaluate Sequence Currents and Fault Voltages for SLG
2 I012 = flt.phs1g(1,Zth,Rf=Rf)
3 Vfault = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
4 Vrly1 = flt.busvolt(0,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
5 Vrly2 = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
6 print("Single Line to Ground:")
7 ep.cprint(Vrly1,"V",["Relay1 VA:", "Relay1 VB:", "Relay1 VC:"])
8 ep.cprint((Vrly1-Vfault)/z113,"A",["Relay1 IA:", "Relay1 IB:", "Relay1 IC:"])
9 ep.cprint(Vrly2,"V",["Relay2 VA:", "Relay2 VB:", "Relay2 VC:"])
10 ep.cprint((Vrly2-Vfault)/z132,"A",["Relay2 IA:", "Relay2 IB:", "Relay2 IC:"])
11
12 # Evaluate Sequence Currents and Fault Voltages for LL
13 I012 = flt.phs2g(1,Zth,Rf=Rf)
14 Vfault = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
15 Vrly1 = flt.busvolt(0,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
16 Vrly2 = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
17 print("\nLine to Line:")
18 ep.cprint(Vrly1,"V",["Relay1 VA:", "Relay1 VB:", "Relay1 VC:"])
19 ep.cprint((Vrly1-Vfault)/z113,"A",["Relay1 IA:", "Relay1 IB:", "Relay1 IC:"])
20 ep.cprint(Vrly2,"V",["Relay2 VA:", "Relay2 VB:", "Relay2 VC:"])
21 ep.cprint((Vrly2-Vfault)/z132,"A",["Relay2 IA:", "Relay2 IB:", "Relay2 IC:"])
22
23 # Evaluate Sequence Currents and Fault Voltages for DLG
24 I012 = flt.phs2g(1,Zth,Rf=Rf)
25 Vfault = flt.busvolt(2,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
26 Vrly1 = flt.busvolt(0,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
27 Vrly2 = flt.busvolt(1,2,1,zbus0,zbus1,zbus2,I012,sequence=False)
28 print("\nDouble Line to Ground:")
29 ep.cprint(Vrly1,"V",["Relay1 VA:", "Relay1 VB:", "Relay1 VC:"])
30 ep.cprint((Vrly1-Vfault)/z113,"A",["Relay1 IA:", "Relay1 IB:", "Relay1 IC:"])
31 ep.cprint(Vrly2,"V",["Relay2 VA:", "Relay2 VB:", "Relay2 VC:"])
32 ep.cprint((Vrly2-Vfault)/z132,"A",["Relay2 IA:", "Relay2 IB:", "Relay2 IC:"])

```

Single Line to Ground:

```

[['Relay1 VA: 0.863 ∠ -11.493° V']
 ['Relay1 VB: 1.091 ∠ -121.001° V']
 ['Relay1 VC: 0.975 ∠ 125.167° V']]
[['Relay1 IA: 0.541 ∠ -36.897° A']
 ['Relay1 IB: 0.217 ∠ -36.897° A']
 ['Relay1 IC: 0.217 ∠ -36.897° A']]
[['Relay2 VA: 0.953 ∠ -3.231° V']
 ['Relay2 VB: 1.028 ∠ -120.332° V']
 ['Relay2 VC: 0.991 ∠ 121.586° V']]
[['Relay2 IA: 0.602 ∠ -36.897° A']
 ['Relay2 IB: 0.241 ∠ -36.897° A']
 ['Relay2 IC: 0.241 ∠ -36.897° A']]

```

Line to Line:

```

[['Relay1 VA: 1.0 ∠ 0.0° V']
 ['Relay1 VB: 0.96 ∠ -132.763° V']
 ['Relay1 VC: 0.786 ∠ 116.27° V']]
[['Relay1 IA: 0.0 ∠ 0.0° A']
 ['Relay1 IB: 0.519 ∠ -131.643° A']
 ['Relay1 IC: 0.519 ∠ 48.357° A']]
[['Relay2 VA: 1.0 ∠ 0.0° V']
 ['Relay2 VB: 0.982 ∠ -123.87° V']
 ['Relay2 VC: 0.933 ∠ 119.018° V']]
[['Relay2 IA: 0.0 ∠ 0.0° A']
 ['Relay2 IB: 0.577 ∠ -131.643° A']
 ['Relay2 IC: 0.577 ∠ 48.357° A']]

```

Double Line to Ground:

```

[['Relay1 VA: 1.029 ∠ 2.42° V']
 ['Relay1 VB: 0.642 ∠ -134.511° V']
 ['Relay1 VC: 0.758 ∠ 126.425° V']]
[['Relay1 IA: 0.122 ∠ 151.806° A']
 ['Relay1 IB: 0.963 ∠ 178.046° A']
 ['Relay1 IC: 0.611 ∠ 16.005° A']]
[['Relay2 VA: 1.009 ∠ 0.771° V']
 ['Relay2 VB: 0.883 ∠ -123.264° V']
 ['Relay2 VC: 0.923 ∠ 121.646° V']]
[['Relay2 IA: 0.135 ∠ 151.806° A']
 ['Relay2 IB: 1.07 ∠ 178.046° A']
 ['Relay2 IC: 0.679 ∠ 16.005° A']]

```

In [] :

1