


Joe Stanley

ECE 524

Homework 1

```
In [23]: 1 # Import Libraries to Support Calculations
2 import numpy as np
3 import matplotlib.pyplot as plt
4 from scipy.integrate import quad as integrate
5 import eepower as eep
6 from eepower import u,m,k,M
```

Problem 1

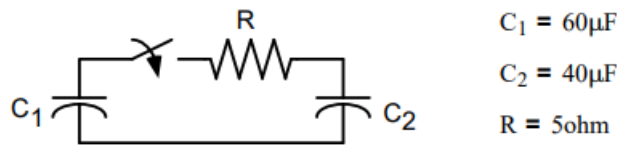

The capacitor C_1 in the figure has an initial charge of 1.0 Coulomb; C_2 is discharged. Calculate the following:


- The peak current through the switch
- The current 200 microseconds after the switch closes
- The total energy dissipated in the resistor
- The ultimate energy stored in C_2
- The ultimate voltage on C_1
- Verify that energy is conserved

In [18]:

```
1  # Define Givens
2  C1 = 60*u
3  C2 = 40*u
4  R = 5
5  Q1 = 1 # Coulomb
6  Q2 = 0
7
8  # Define Voltage from Charge
9  Vc1o = Q1/C1
10 Vc2o = Q2/C2
11 print("Cap1 V:",Vc1o,"Cap2 V:",Vc2o)
12
13 # A) Peak Current
14 Imax = (Vc1o - Vc2o)/R
15 print("A) Max Current:",Imax,"A")
16
17 # B) Current at 200uS after Close
18 # Define Capacitive Voltage Functions
19 def vcapdischarge(t,Vs,R,C):
20     Vc = Vs*(np.exp(-t/(R*C)))
21     return(Vc)
22 def vcapcharge(t,Vs,R,C):
23     Vc = Vs*(1-np.exp(-t/(R*C)))
24     return(Vc)
25
26 # Define Capacitor Charge transfer Function
27 def captransfer(t,Vs,R,Cs,Cd):
28     tau = (R*Cs*Cd) / (Cs+Cd)
29     rvolt = Vs*np.exp(-t/tau)
30     vfinal = Vs*Cs/(Cs+Cd)
31     return(rvolt,vfinal)
32
33 t_arr = np.linspace(0,200*u,1000)
34 Vr = captransfer(t_arr,Vc1o,R,C1,C2)
35 plt.title("Resistor Characteristics Over Time")
36 plt.plot(t_arr,Vr[0],label="Resistor Voltage")
37 plt.plot(t_arr,Vr[0]/R,label="Resistor Current")
38 plt.legend()
39 plt.show()
40
41 # Find Current
42 i200us = (Vr[0][-1:] / R)[0]
43 print("B) Current at 200uS:",i200us,"A")
44
45 # C) Energy Loss
46 # Define Capacitor Energy
47 def capenergy(c,v):
48     return(1/2 * c * v**2)
49 cap_eq = (C1*C2/(C1+C2))
50 eloss = capenergy(cap_eq,Vc1o)
51 print("C) Energy Lost in Resistor:",eloss)
52
53 # D) Find Final Energy for Cap-2
54 vfinal = Vr[1]
55 print("Final Voltage on Caps:",vfinal,"V")
56 efinal2 = capenergy(C2,vfinal)
57 print("D) Final Energy (Cap-2):",efinal2)
58
59 # E) Final energy for Cap-1
60 efinal1 = capenergy(C1,vfinal)
61 print("E) Final Energy (Cap-1):",efinal1)
62
63 # F) Energy Conservation Confirmation
64 einitial = capenergy(C1,Vc1o)
65 econserved = einitial - efinal1 - efinal2 - eloss
66 print("F) Difference in Energy Input/Output:",econserved)
```

Cap1 V: 16666.666666666668 Cap2 V: 0.0


A) Max Current: 3333.3333333333335 A

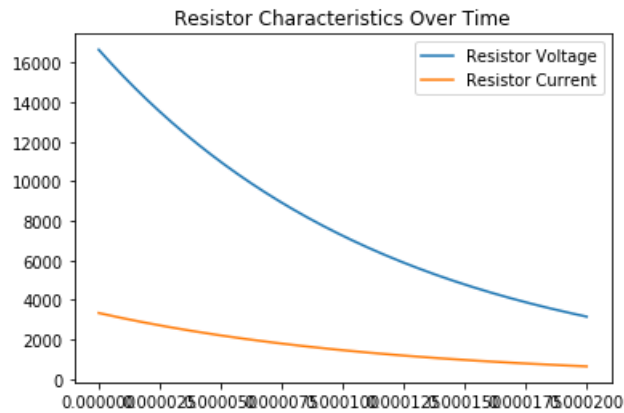

- B) Current at 200uS: 629.585342792 A
 C) Energy Lost in Resistor: 3333.33333333333
 Final Voltage on Caps: 10000.0 V
 D) Final Energy (Cap-2): 1999.999999999998
 E) Final Energy (Cap-1): 2999.999999999995
 F) Difference in Energy Input/Output: -9.094947017729282e-13

Problem 2

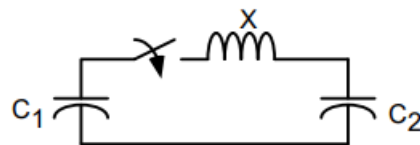Problem 2: Given the simple LC network with the conditions given below find the following:



$$C_1 = 60\mu\text{F} \quad Q_{C1} = 1\text{C}$$

$$C_2 = 40\mu\text{F} \quad Q_{C2} = 0\text{C}$$

$$X = 5\text{ohm} \quad \text{at } 60\text{Hz}$$

- Find the instantaneous current when the switch closes.
- Determine the peak current
- Find the energy stored in the inductor at $t = 1\text{ms}$
- Find the voltage across C_1 at $t = 1\text{ms}$.



```

In [14]: 1 # Define Givens
2 # ALL capacitor-related values remain unchanged
3 X = 5 # ohm @ 60Hz
4 L = eep.reactance(X)
5 print("Inductive Reactance:",L,"H")
6
7 # A) Instantaneous Current (Trick Question!)
8 ILo = 0
9 print("A) Instantaneous Current (t=0+):",ILo,"A")
10
11 # Iteratively Solve System to Evaluate Circuit
12 dt = 1e-7
13 t_arr = np.arange(0,1.5*m,dt)
14 I = np.array([ILo])
15 V1 = np.array([Vc1o])
16 V2 = np.array([Vc2o])
17 for t in t_arr:
18     v1 = V1[-1:]
19     v2 = V2[-1:]
20     i = I[-1:]
21     dV1 = i/C1*dt
22     dI = (v1-v2)/L*dt
23     V1 = np.append(V1, v1-dV1)
24     V2 = np.append(V2, v2+dV1)
25     I = np.append(I, i+dI)
26
27 # Plot
28 plt.plot(t_arr,V1[:-1],label="Cap-1")
29 plt.plot(t_arr,V2[:-1],label="Cap-2")
30 plt.title("Capacitor Voltages")
31 plt.axvline(1*m,linestyle='--')
32 plt.legend()
33 plt.show()
34 plt.plot(t_arr,I[:-1],label="Inductor")
35 plt.title("Current")
36 plt.axvline(1*m,linestyle='--')
37 plt.legend()
38 plt.show()
39
40 # B) Find Max Current
41 Imax = max(I)
42 print("B) Maximum Current:",Imax,"A")
43
44 # Define Inductor Energy Formula
45 def inductorenergy(L,I):
46     return(1/2 * L * I**2)
47
48 # C) Inductor Energy at 1ms
49 # Collect the current at 1ms
50 index = np.where(t_arr==1*m)[0].item(0)
51 i1ms = I.item(index)
52 print("Inductor Current at 1ms:",i1ms,"A")
53 eL1ms = inductorenergy(L,i1ms)
54 print("C) Energy Stored in Inductor (t=1ms):",eL1ms)
55
56 # D) Voltage on Cap 1 at 1ms
57 vc1_1ms = V1.item(index)
58 print("D) Voltage across Cap-1 (t=1ms):",vc1_1ms,"V")

```

Inductive Reactance: 0.013262911924324612 H

A) Instantaneous Current (t=0+): 0 A

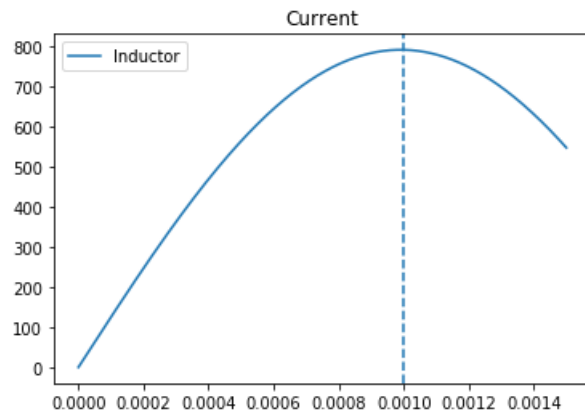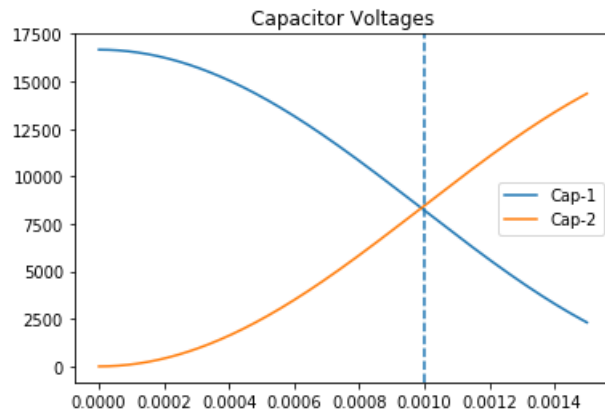


- B) Maximum Current: 792.764163871 A
 Inductor Current at 1ms: 792.6813391414418 A
 C) Energy Stored in Inductor (t=1ms): 4166.833611614969
 D) Voltage across Cap-1 (t=1ms): 8212.200885473283 V

Problem 3

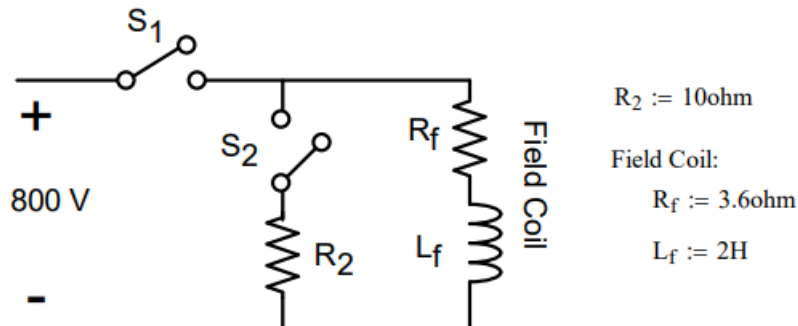Problem 3. The figure below shows the field coil of an electric machine. It is excited by closing switch S_1 onto an 800V d.c. bus. Determine the energy stored in the coil, and the energy dissipated in the coil resistance, 1 sec after S_1 is closed.


When the coil current has attained a steady value, S_1 is opened and S_2 is closed simultaneously. What will be the voltage across S_1 0.1 sec later? How much energy will eventually be dissipated in R_2 ?



- You need to have the system in steady-state before opening S_1
- Note: when simulation this, S_1 needs to be *set to interrupt the steady-state* load current
- S_2 needs to be commanded to close at the same time S_1 opens.

In [27]:

```
1  # Define Givens
2  Rf = 3.6
3  Lf = 2
4  XL = eep.phasorz(L=Lf)
5  R2 = 10
6  Vsrc = 800 # DC
7
8  # Define Inductor Charging/Discharging Functions
9  def inductorcharge(t,Vs,R,L):
10     Vl = Vs*np.exp(-R*t/L)
11     Il = Vs/R*(1-np.exp(-R*t/L))
12     return(Vl,Il)
13  def inductordischarge(t,Io,R,L):
14     Il = Io*np.exp(-R*t/L)
15     Vl = Io*R*(1-np.exp(-R*t/L))
16     return(Vl,Il)
17
18  # Calculate Current Through Field
19  t_arr = np.linspace(0,1.2,1000)
20  V, I = inductorcharge(t_arr,Vsrc,Rf,Lf)
21
22  # Plot
23  plt.plot(t_arr,V,label="Inductor Voltage (V)")
24  plt.plot(t_arr,I,label="Field Current (A)")
25  plt.title("Charging System")
26  plt.legend()
27  plt.show()
28
29  # Calculate Stored Energy in Inductor at 1 sec
30  eL1sec = inductorenergy(Lf,Ifield_chg(1))
31  print("Energy Stored in Inductor (t=1sec):",eL1sec)
32
33  # Define Resistor Power
34  Rpower = lambda t: Ifield_chg(t)*(Vsrc-vindcharge(t,Vsrc,Rf,Lf))
35
36  # Calculate Resistor Energy Dissipation
37  Renergy = integrate(Rpower,0,1)[0]
38  print("Energy Dissipated in Resistor:",Renergy)
39
40  # Evaluate "initial" current
41  Io = Vsrc / R
42
43  # Define VS1 Formula
44  def VS1(t):
45     # Evaluate Inductor Voltage/Current
46     VL, IL = inductordischarge(t,Io,Rf,Lf)
47     # Evaluate V-Leg
48     Vleg = VL + Rf*IL
49     # Evaluate VS1
50     return(Vsrc - Vleg)
51
52  # Calculate VS1 at 0.1 sec after switch change
53  VS1_pt1 = VS1(0.1)
54  print("Switch-1 Voltage (t=0.1sec):",VS1_pt1,"V")
55
56  # Find energy stored in inductor
57  energyTL = inductorenergy(Lf,Io)
58
59  # Find energy dissipated in R2 (as linearly related to Rf)
60  energyR2 = energyTL * R2 / (Rf+R2)
61  print("Total Energy Dissipated in R2:",energyR2)
```

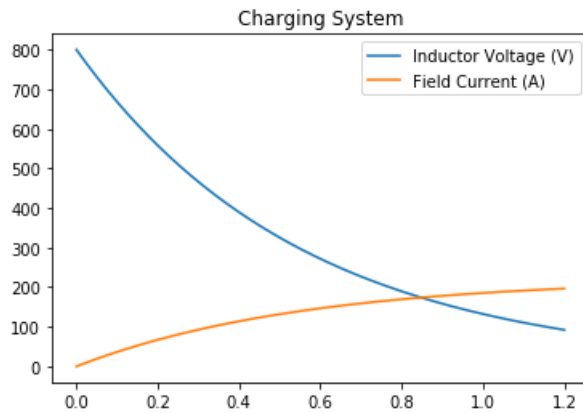

Energy Stored in Inductor (t=1sec): 34406.2195558
 Energy Dissipated in Resistor: 60931.94224390389
 Switch-1 Voltage (t=0.1sec): 224.0 V
 Total Energy Dissipated in R2: 18823.529411764706

Problem 4

Problem 4: A 230kV:69kV, 100MVA three phase transformer (wye grounded-wye grounded) has per unit leakage reactance of 10% with an X/R ratio of 15. This is supplied by a source impedance of $j0.05\text{pu}$. No change of base calculations are needed.

- A. Calculate the worst case peak fault current for a fault at the low voltage terminals. What is the angle of inception compared to the voltage waveform (assume a cosine voltage source)? Include the resistance.
 - B. Using simulation only, repeat part A if the X/R ratio of the transformer is 7.
- Model the system referred to the low voltage winding for your simulation, do not use the built-in transformer models yet. We will learn to use the transformer models in the simulation later in the semester.

```

In [39]: 1 # Define Givens:
2 HVside = 230*k
3 LVside = 69*k
4 S3p = 100*M
5 S = S3p / 3
6 Rleak = 0.1 # PU
7 XR = 15
8 Xleak = XR*Rleak
9 leak = Rleak + 1j*Xleak
10 Zsrc = 0.05j
11
12 # No Load is described, treat system as unloaded
13 # Worst-Case Fault will be 3-Phase Bolted Fault
14
15 # Start by finding Zeq
16 Zeq = leak + Zsrc
17 print("Equivalent System Impedance:",Zeq,"PU-ohms")
18
19 # Calculate Worst-Case Current
20 Ifault = eep.fault.phs3(1,(0,Zeq,0),sequence=False)
21 print("System Fault Currents:")
22 eep.cprint(Ifault,"PU-A",["Ia","Ib","Ic"])
23
24 # Demonstrate Inception Angle
25 inceptang = np.angle(Ifault[0],True)
26 print("Inception Angle:",inceptang,"°")

```

Equivalent System Impedance: (0.1+1.55j) PU-ohms

System Fault Currents:

```

[['Ia 0.644 ∠ -86.309° PU-A']
 ['Ib 0.644 ∠ 153.691° PU-A']
 ['Ic 0.644 ∠ 33.691° PU-A']]

```

Inception Angle: -86.3086140135 °

In []:

1

In []:

1