

# Joe Stanley

## ECE 524 - HWK 3

```
In [1]: 1 # Import Necessary Libraries
2 import numpy as np
3 import matplotlib.pyplot as plt
4 import eepower as eep
5 from eepower import u, m, k, M
```

```
In [2]: 1 # Define Givens
2
3 # Per-Unit Bases
4 Sbase = 30*M
5 Vb1 = 138*k
6 Vb2 = 13.8*k
7 Vb3 = 4.16*k
8
9 # Source
10 S_src = 3500*M #VA
11 XR_src = 15 #unitless
12 V_src = 138*k #V
13 Z_src = (0.0005701629473466338+0.008552444210199505j) # per-unit (from prev.
14
15 # Transformer(s)
16 S_xfm = 30*M #VA
17 Z_xfm = 7.5/100 #pu
18 XR_xfm = 18.6 #unitless
19 V_busA = 13.8*k #V
20 Z_xfm = (0.00402644303154544+0.07489184038674519j) # per-unit (from prev. as
21
22 # Generator
23 S_gen = 35.3*M #VA
24 Xdv_gen = 10/100 #pu
25 XR_gen = 48 #unitless
26 Z_gen = (0.0017705382436260624+0.08498583569405099j) # per-unit (from prev.
27
28 # Motor Load (each motor)
29 P_mot = 30000 #hp
30 Xd_mot = 16.7/100 #pu
31 XR_mot = 10 #unitless
32 pf_mot = 0.8 #lagging
33
34 # Cap Bank
35 S_cap = 10*M #VAr
36
37 # Load Transformer
38 S_xfm_ld = 5*M #VA
39 Z_xfm_ld = 5.5/100 #pu
40 XR_xfm_ld = 7 #unitless
41 V_ld = 4.16*k #V
```

In [13]:

```
1  # Validate Formulas Prior to Solving Homework
2
3  # Use Example provided in Lecture 14 Handout
4  C1 = eep.farads(18*M,34.5*k)
5  C2 = eep.farads(10*M,34.5*k)
6  print(C*M)
7  I,F = eep.capbacktoback(C1=C2,C2=C1,Lm=19.2*u,VLL=34.5*k)
8  print(I,F)
```

40.114667445972366

24332.9875341 9596.14794355

## Problem 1 (text 6.3)

Find inrush current and frequency.


In [55]:

```
1 # Define Problem-Specifics
2 C_sub = 5*M # VAR
3 Lm = 15*u # H
4
5 # Evaluate Capacitance (in Farads)
6 Cf = eep.farads(C_sub,Vb2)
7 print("Sub-Bank Capacitance (C1/C2):",Cf*M,"μF")
8
9 # Evaluate Inrush Current and Frequency
10 Iin, Fin = eep.capbacktoback(Cf,Cf,Lm,VLL=Vb2)
11 print("Inrush Current:",Iin/k,"kA")
12 print("Inrush Frequency:",Fin,"Hz")
13
14 # Load Data from File
15 data = np.genfromtxt("HWK-3-p1.ADF",delimiter='\t',skip_header=2,usecols=(0,
16 t_arr, Vcap = data
17
18 # Plot Data
19 plt.plot(t_arr,Vcap)
20 plt.title("Part 1")
21 plt.xlim(0.009,0.0125)
22 plt.show()
```

Sub-Bank Capacitance (C1/C2): 69.64351987147981 μF

Inrush Current: 17.1677423121 kA

Inrush Frequency: 6963.84576078 Hz

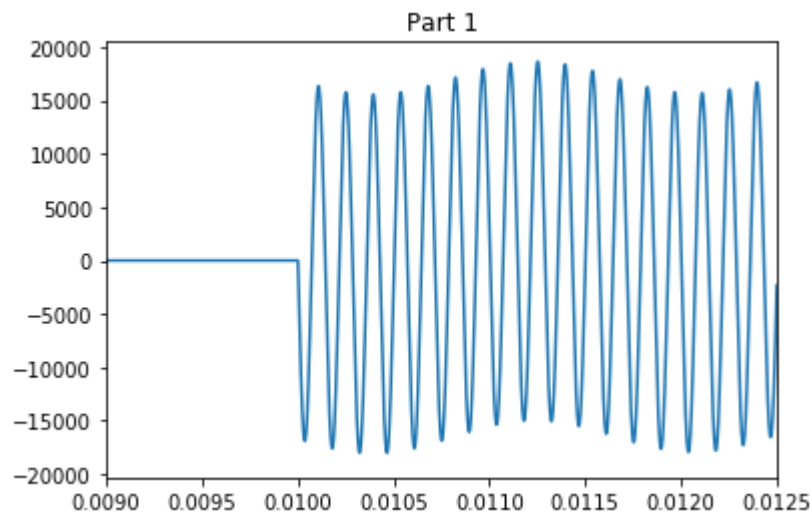

## Problem 2 (text 6.4)

Evaluate what  $L_m$  must be to reduce the inrush current to 15kA, and to reduce the frequency to 2000Hz.

In [58]:



```
1  # Specify Test Step-Size
2  step = 0.001*u
3
4  # Iteratively solve for current requirement
5  Ldesired = Lm # Start with Lm
6  while True:
7      # Solve for inrush current
8      Iin, x = eep.capbacktoback(Cf,Cf,Ldesired,VLL=Vb2)
9      # Test for completion
10     if Iin <= 15*k:
11         break # Found result
12     # Increment Inductance
13     Ldesired += step
14 print("Required Inductance (Lm):",Ldesired/m,"mH")
15 print("Resultant Inrush Current:",Iin/k,"kA")
16
17 # Iteratively solve for frequency requirement
18 Ldesired = Lm # Start with Lm
19 while True:
20     # Solve for inrush current
21     x, F = eep.capbacktoback(Cf,Cf,Ldesired,VLL=Vb2)
22     # Test for completion
23     if F <= 2000:
24         break # Found result
25     # Increment Inductance
26     Ldesired += step
27 print("Required Inductance (Lm):",Ldesired/m,"mH")
28 print("Resultant Inrush Frequency:",F,"Hz")
29
30 # Load Data from File
31 data = np.genfromtxt("HWK-3-p2.ADF",delimiter='\t',skip_header=2,usecols=(0,
32 t_arr, Vcap = data
33
34 # Plot Data
35 plt.plot(t_arr,Vcap)
36 plt.title("Part 2")
37 plt.xlim(0.009,0.0125)
38 plt.show()
39
40 # Load Data from File
41 data = np.genfromtxt("HWK-3-p2b.ADF",delimiter='\t',skip_header=2,usecols=(0
42 t_arr, Vcap = data
43
44 # Plot Data
45 plt.plot(t_arr,Vcap)
46 plt.title("Part 2")
47 plt.xlim(0.009,0.0125)
48 plt.show()
```

Required Inductance (Lm): 0.01964899999999488 mH

Resultant Inrush Current: 14.9999077837 kA

Required Inductance (Lm): 0.181856999999950347 mH

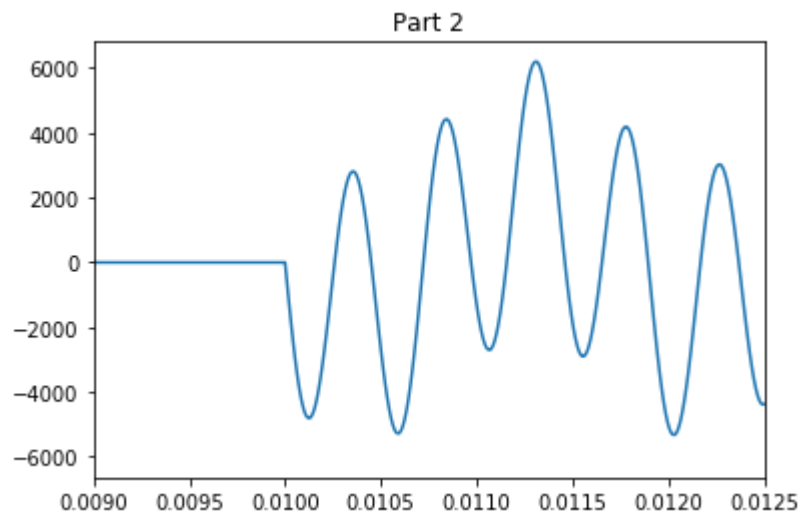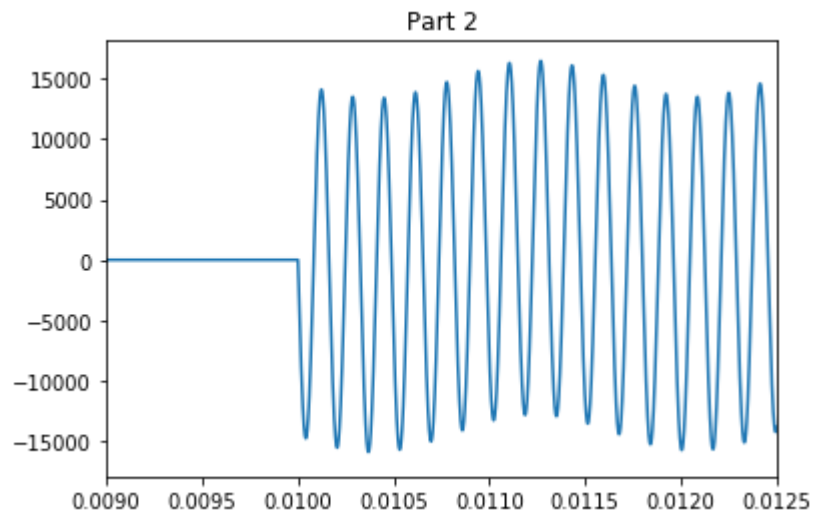Resultant Inrush Frequency: 1999.99892319 Hz



### Problem 3 (text 6.5)

Find the particular resistance for circuits (both open and closed bus-tie-breaker).

In [46]:

```
1  # Define Critically Damped Formula (from Lecture 12 Notes)
2  def critdamp(L,C):
3      R = np.sqrt(1/(L*C))*2*L
4      return(R)
5
6  # Define C - Delta-Cap-Bank
7  C = eep.farads(10*M,13.8*k)
8  print("Capacitance:",C/u,"μF")
9
10 # Define L (Breaker Open)
11 L = 0.0007096941825782752 # H (from HWK2)
12 # Evaluate R
13 CBO_R = critdamp(L,C)
14 print("CB-Open R:",CBO_R,"Ω")
15
16 # Define L (Breaker Closed)
17 L = 0.0005031692747875754 # H (from HWK2)
18 # Evaluate R
19 CBC_R = critdamp(L,C)
20 print("CB-Closed R:",CBC_R,"Ω")
```

Capacitance: 139.28703974295962 μF

CB-Open R: 4.51450630692 Ω

CB-Closed R: 3.80129608469 Ω

In [48]:

```
1  # Calculate Additional Bank Resistance
2  print("Additional CB-Open Resistor:",CBO_R-0.010184642321227273,"Ω")
3  print("Additional CB-Closed Resistor:",CBC_R-0.00828798310752,"Ω")
```



Additional CB-Open Resistor: 4.5043216646 Ω

Additional CB-Closed Resistor: 3.79300810159 Ω

```

In [51]: 1 # Load Data from File
2 data = np.genfromtxt("HWK-3-p3A.ADF",delimiter='\t',skip_header=2,usecols=(0
3 t_arr, Vcap = data
4
5 # Plot Data
6 plt.plot(t_arr,Vcap)
7 plt.title("Open Breaker")
8 plt.show()
9
10 # Load Data from File
11 data = np.genfromtxt("HWK-3-p3B.ADF",delimiter='\t',skip_header=2,usecols=(0
12 t_arr, Vcap = data
13
14 # Plot Data
15 plt.plot(t_arr,Vcap)
16 plt.title("Closed Breaker")
17 plt.show()

```

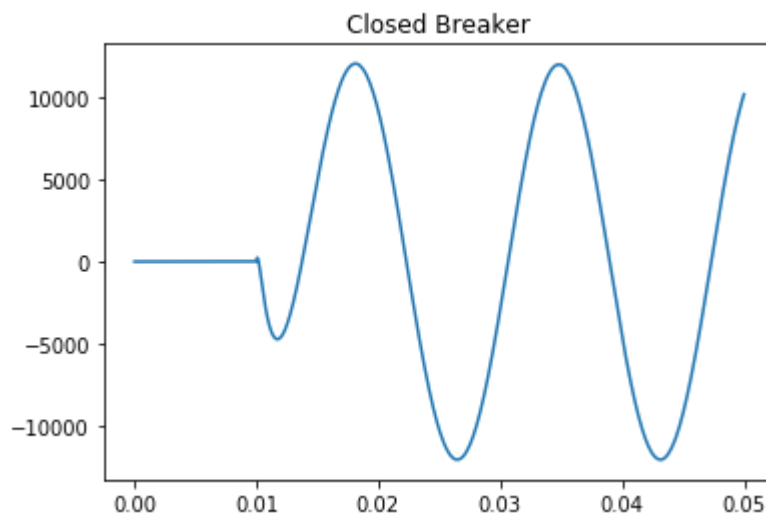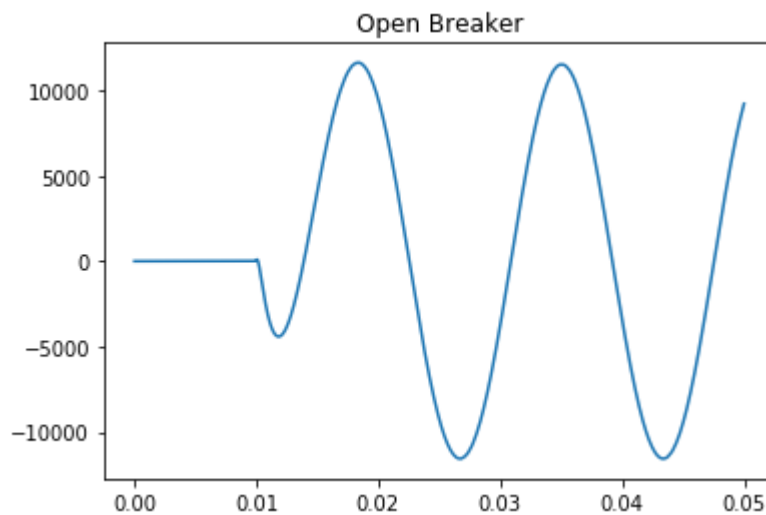

```

In [ ]: 1

```

```

In [ ]: 1

```

