

ECE 525

Final Exam

July 2019

EXAMINATION RULES

1. This is an open-book/open-note take-home exam.
2. I can e-mail a MathCAD file with the exam problems to you if you would like a copy.
3. Do your own work on this examination. You are on your honor. Therefore, you will neither give nor receive aid on this examination, except from the *course* instructor. If you violate this trust, you will receive the grade of zero for this examination.
4. Show all of your work! Make it neat. *No* partial credit will be given if I can not easily follow your work.
5. You have 3 days to complete the exam the exam from the time you receive it from your proctor.
6. Please read and sign the following statement when you finish the exam:
7. I certify that I have neither given nor have I received any help on this examination, except from the course instructor.

SIGNED: _____

PRINTED NAME: _____

DATE: _____


1. _____ /46 pts

2. _____ /36 pts

3. _____ /18 pts

Total: _____ /100 pts

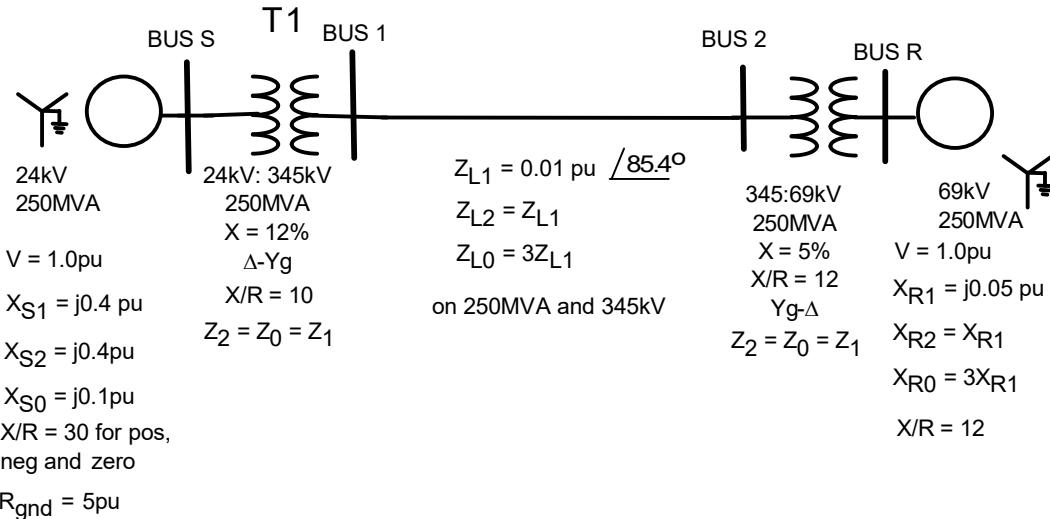1. (46 pts) Given the simple power system below, consider transformer protection options for T1.



- Assuming the transformer, T1, above is connected to meet the standard ANSI phase shift, show how the windings are connected with a sketch and supporting description as needed. Include CT connections, first assuming you have electromechanical relays and second assuming you have a microprocessor relay. Also determine CT ratios for the microprocessor relay case.
- Calculate the TAP settings to for the primary and secondary windings and choose appropriate connection compensation matrices for a differential protection scheme in a microprocessor relay.
- Suggest a setting for an unrestrained overcurrent. What would you base this setting on?
- Explain the difference between harmonic restraint and harmonic blocking in transformer differential protection. Recommend settings for each. When should these be acting?
- Suppose you are instructed to choose a slope setting, assuming the relay can make a decision prior to CT saturation. The transformer also has a tap changer on the HV winding, with limits of +10% and -10%. Incorporate this in the slope setting (show your work).

F. Using the results of the earlier parts of the problem, calculate the IOP and IRT currents for the following external events. Will the element be secure using a slope setting of 40%. Currents in primary Amps

Case 1: Rated load, with nominal tap position:

$$|I_{HV_F1}| = \begin{pmatrix} 418.37 \\ 418.37 \\ 418.37 \end{pmatrix} A \quad \arg(I_{HV_F1}) = \begin{pmatrix} -175.84 \\ 64.16 \\ -55.84 \end{pmatrix} \text{deg} \quad |I_{LV_F1}| = \begin{pmatrix} 6014.06 \\ 6014.06 \\ 6014.06 \end{pmatrix} A \quad \arg(I_{LV_F1}) = \begin{pmatrix} -25.84 \\ -145.84 \\ 94.158 \end{pmatrix} \text{deg}$$

Case 2: Rated load, with off nominal tap position on HV side (LV doesn't change):

$$|I_{HV_F2}| = \begin{pmatrix} 469.504 \\ 469.504 \\ 469.504 \end{pmatrix} A \quad \arg(I_{HV_F2}) = \begin{pmatrix} -175.84 \\ 64.16 \\ -55.84 \end{pmatrix} \text{deg} \quad |I_{LV_F2}| = \begin{pmatrix} 6224.557 \\ 6224.557 \\ 6224.557 \end{pmatrix} A \quad \arg(I_{LV_F2}) = \begin{pmatrix} -25.84 \\ -145.84 \\ 94.158 \end{pmatrix} \text{deg}$$

Case 3: Phase open condition on the transmission line

$$|I_{HV_F3}| = \begin{pmatrix} 134.270 \\ 0 \\ 136.266 \end{pmatrix} A \quad \arg(I_{HV_F3}) = \begin{pmatrix} -129.79 \\ 100.62 \\ -43.052 \end{pmatrix} \text{deg} \quad |I_{LV_F3}| = \begin{pmatrix} 1580.052 \\ 1141.957 \\ 1158.921 \end{pmatrix} A \quad \arg(I_{LV_F3}) = \begin{pmatrix} 3.132 \\ -129.79 \\ 136.948 \end{pmatrix} \text{deg}$$

Case 4: External SLG

$$|I_{HV_F4}| = \begin{pmatrix} 1296.862 \\ 341.511 \\ 341.511 \end{pmatrix} A \quad \arg(I_{HV_F4}) = \begin{pmatrix} 94.049 \\ 97.217 \\ 97.217 \end{pmatrix} \text{deg} \quad |I_{LV_F4}| = \begin{pmatrix} 8106.92 \\ 8106.92 \\ 0 \end{pmatrix} A \quad \arg(I_{LV_F4}) = \begin{pmatrix} -87.074 \\ 92.926 \\ 104.036 \end{pmatrix} \text{deg}$$

Case 5: Repeat case 4, with only 20% of the current coming from the Phase A CT on the HV side.

2. (36 pts) Short Answer:

(a) (12 pts) Low impedance bus differential protection scheme:

- (1) Explain how CT saturation could impact performance for faults internal to the zone
- (2) Explain how CT saturation could impact performance for faults external to the zone. Which is more of a concern, internal or external
- (3) What could be modified to create a bus protection scheme be set up to reduce the effect of saturation on security (list and describe at least 2 options).

(b) (8 pts) Describe how you would set up a bus protection scheme for a configuration that doesn't lend itself to differential protection, such as a ring bus.

(c) (8 pts) Describe the basic concept of a breaker failure scheme and create and describe a simple application example with a failure at a transmission bus.

(d) (8 pts) Suppose a station has two transformers in parallel, each with tap changers. How would a protection and control scheme be implemented to minimize circulating currents between the two transformers

3. (18 pts) You are given a bus with 3 incoming lines, as shown in the figure below. Each as a 1200/5, C600 CT with the characteristics shown on the next page. Assume a resistance of 0.0024 ohm/turn. The lead resistance is 0.81 ohm. from any CT to the junction point. Determine the settings for a high impedance bus differential relay which has a stabilizing resistance of 2000 ohms. Assume VLLrated = 230kV, Sbase = 100 MVA


The maximum fault external fault currents seen at any CT are as follows:

- Three phase fault: 45 kA
- SLG fault: 40 kA
- LL fault: 37 kA


Do the following:

- Determine the voltage set point using the equation (1) below (slightly modified from Lecture 23 and also equations (1) and (2) from the paper "Considerations for Using High-Impedance or Low-Impedance Relays for Bus Differential Protection" linked from lecture 24).
- Determine the minimum primary internal fault current this relay can detect using equation (2) below (also equation (3) from the paper above).
- Repeat A and B if the stabilizer resistor is 1200 ohm
- Repeat parts A and B if an additional feeder is added to the circuit, with a CT identical to the others. The available fault currents increase to 50 kA for the 3 phase fault, 45 kA for the SLG and 39 kA for LL.

System Diagram for Parts A-C:

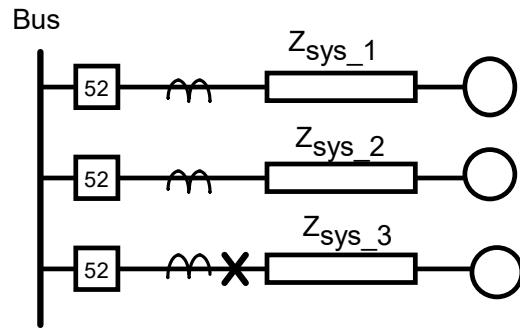

System Diagram for Part D:

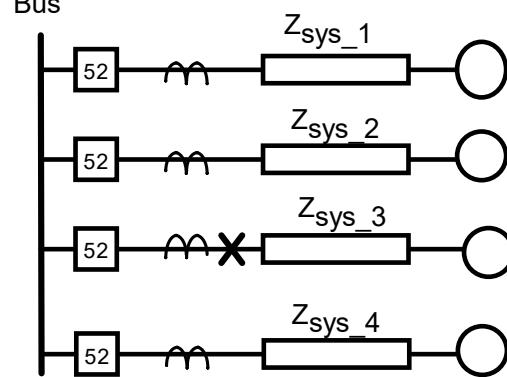

$$V_R = 1.5(R_{CT} + k \cdot R_{Lead}) \cdot \frac{I_{Fmax}}{CTR} \quad (1) \quad \text{Where: } k=1 \text{ for a 3 phase fault, and } k=2 \text{ for unbalanced faults.}$$

$$I_{min} = (n \cdot I_e + I_{relay} + I_m) \cdot CTR \quad (2)$$

Where: I_e is the CT excitation current for the voltage across the magnetizing branch

n is the number of CTs in parallel

I_{relay} the current through the relay for the applied voltage (in this case, to determine the minimum fault current, use the setpoint voltage, V_R , divided by the stabilizing resistance)

I_m MOV leakage current at the applied voltage (0A in the minimum fault detectable fault current case).

CT data


CT Data: C600 class, 1200/5

ORIGIN := 1

	CT Excitation Curve	TAPS
excitation :=	.001 0.09	(240)
	.04 90	200
	.1 428	180
	.12 520	160
	.14 600	120
	.2 700	100
	.3 780	80
	.4 800	60
	40 927	40
		20

$t :=$
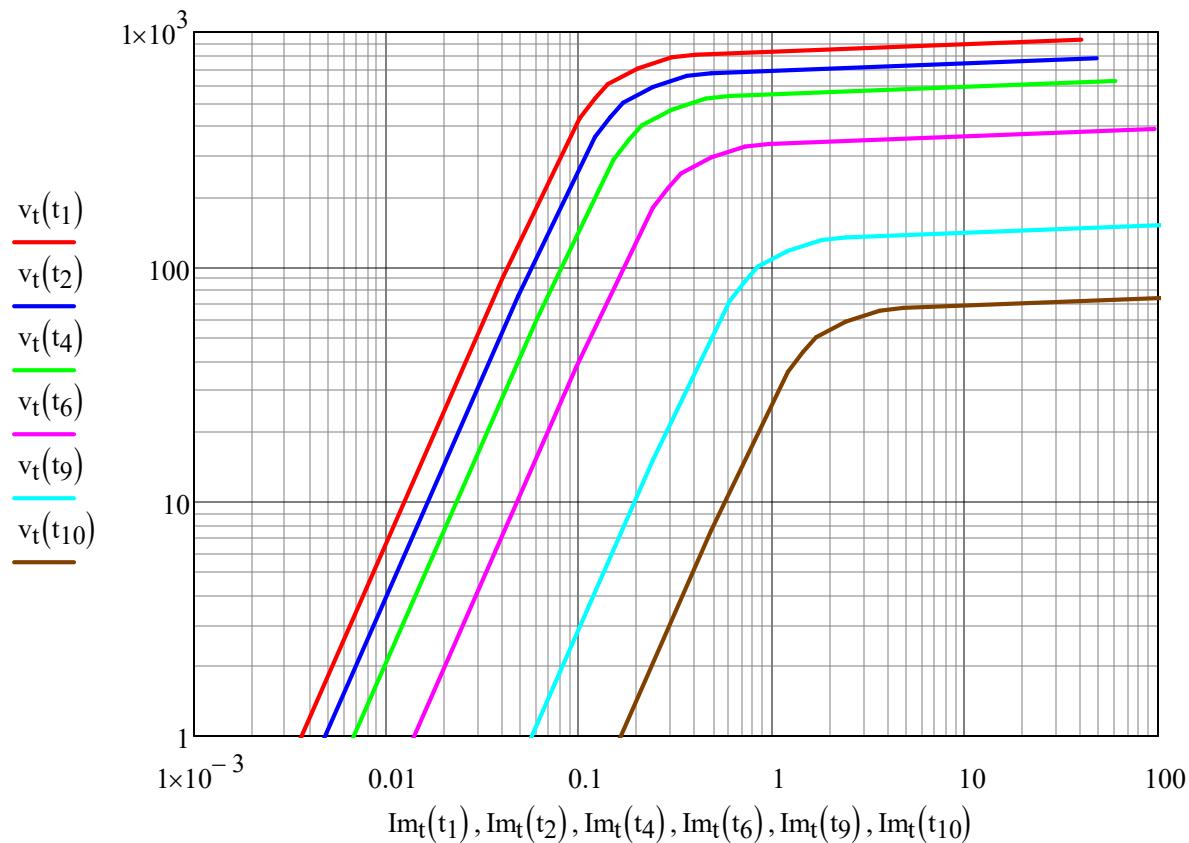
$$v_t(N2) := \left(\frac{N2}{t_1} \right) \cdot \text{excitation}^{(2)} \quad Im_t(N2) := \left(\frac{t_1}{N2} \right) \cdot \text{excitation}^{(1)}$$



Joe Stanley

ECE 525 - FINAL EXAM

In [1]:

```
1 # Import Libraries
2 import numpy as np
3 import matplotlib.pyplot as plt
4 import eepower as eep
5 from eepower import p,n,u,m,k,M
```

```

In [2]: 1 # Define CTR Printing Method
2 CTR = lambda x: print(x[2],int(np.ceil(x[0])),"/",x[1]," ->\t",int(np.ceil(x[0]/x[1])))
3 # Define Transformer Shift Correction Matricies
4 XFMY0 = np.array([[1,0,0],[0,1,0],[0,0,1]])
5 XFMD1 = 1/np.sqrt(3) * np.array([[1,-1,0],[0,1,-1],[-1,0,1]])
6 XFMD11 = 1/np.sqrt(3) * np.array([[1,0,-1],[-1,1,0],[0,-1,1]])
7 XFM12 = 1/3 * np.array([[2,-1,-1],[-1,2,-1],[-1,-1,2]])
8 # Define TAP Calculator
9 def protectiontap(CTR,S,VLN=None,VLL=None):
10     """
11         protectiontap Function
12
13         Evaluates the required TAP setting based on the rated power of
14         a transformer (the object being protected) and the voltage
15         (either primary or secondary) in conjunction with the CTR
16         (current transformer ratio) for the side in question (primary/
17         secondary).
18
19         Parameters
20         -----
21         CTR: float
22             The Current Transformer Ratio.
23         S: float
24             Rated apparent power magnitude (VA/VAR/W).
25         VLN: float, exclusive
26             Line-to-Neutral voltage in volts.
27         VLL: float, exclusive
28             Line-to-Line voltage in volts.
29
30         Returns
31         -----
32         TAP: float
33             The TAP setting required to meet the specifications.
34     """
35     # Condition Voltage(s)
36     if VLL != None:
37         V = abs(np.sqrt(3)*VLL)
38     elif VLN != None:
39         V = abs(3 * VLN)
40     else:
41         raise ValueError("One or more voltages must be provided.")
42     # Calculate TAP
43     TAP = abs(S) / (V*CTR)
44     return(TAP)
45 # Define Current Correction Calculator
46 def correctedcurrents(Ipri,TAP,correction="Y",CTR=1):
47     """
48         correctedcurrents Function:
49
50         Function to evaluate the currents as corrected for microprocessor-
51         based relay protection schemes.
52
53         Parameters
54         -----
55         Ipri: list of complex
56             Three-phase set (IA, IB, IC) of primary currents.
57         TAP: float
58             Relay's TAP setting.
59         correction: string, optional
60             String defining correction factor, may be one of:
61             (Y, D+, D-, Z); Y denotes Y (Y0) connection, D+
62             denotes Dab (D1) connection, D- denotes Dac (D11)
63             connection, and Z (Z12) denotes zero-sequence
64             removal. default="Y"
65         CTR: float
66             Current Transformer Ratio, default=1
67
68         Returns
69         -----
70         Isec_corr: list of complex
71             The corrected currents to perform operate/restraint
72             calculations with.
73     """
74     # Define Matrix Lookup
75     MAT = { "Y" : XFMY0,
76             "D+" : XFMD1,
77             "D-" : XFMD11,
78             "Z" : XFM12}
79     # Condition Inputs
80     Ipri = np.asarray(Ipri)
81     if isinstance(correction,list):

```


```

82         mult = MAT[correction[0]]
83         for i in correction[1:]:
84             mult = mult.dot(MAT[i])
85     elif isinstance(correction,str):
86         mult = MAT[correction]
87     elif isinstance(correction,np.ndarray):
88         mult = correction
89     else:
90         raise ValueError("Correction must be string or list of strings.")
91     # Evaluate Corrected Current
92     Isec_corr = 1/TAP * mult.dot(Ipri/CTR)
93     return(Isec_corr)
94 # Define Iop/Irt Calculator
95 def iopirt(IpriHV,IpriLV,TAPHV,TAPLV,corrHV="Y",corrLV="Y",CTRHV=1,CTRLV=1):
96     """
97     iopirt Function:
98
99     Calculates the operating current (Iop) and the restraint
100    current (Irt) as well as the slope.
101
102    Parameters
103    -----
104    IpriHV:      list of complex
105            Three-phase set (IA, IB, IC) of primary currents
106            on the high-voltage side of power transformer.
107    IpriLV:      list of complex
108            Three-phase set (IA, IB, IC) of primary currents
109            on the low-voltage side of power transformer.
110    TAPHV:       float
111            Relay's TAP setting for high-voltage side of
112            power transformer.
113    TAPLV:       float
114            Relay's TAP setting for low-voltage side of
115            power transformer.
116    corrHV:      string, optional
117            String defining correction factor on high-voltage
118            side of power transformer, may be one of:
119            (Y, D+, D-, Z); Y denotes Y (Y0) connection, D+
120            denotes Dab (D1) connection, D- denotes Dac (D11)
121            connection, and Z (Z12) denotes zero-sequence
122            removal. default="Y"
123    corrLV:      string, optional
124            String defining correction factor on low-voltage
125            side of power transformer, may be one of:
126            (Y, D+, D-, Z); Y denotes Y (Y0) connection, D+
127            denotes Dab (D1) connection, D- denotes Dac (D11)
128            connection, and Z (Z12) denotes zero-sequence
129            removal. default="Y"
130    CTRHV:       float
131            Current Transformer Ratio for high-voltage side
132            of power transformer, default=1
133    CTRLV:       float
134            Current Transformer Ratio for low-voltage side
135            of power transformer, default=1
136
137    Returns
138    -----
139    Iop:        list of float
140            The operating currents for phases A, B, and C.
141    Irt:        list of float
142            The restraint currents for phases A, B, and C.
143    slope:      list of float
144            The calculated slopes for phases A, B, and C.
145    """
146    # Calculate Corrected Currents
147    IcorHV = correctedcurrents(IpriHV,TAPHV,corrHV,CTRHV)
148    IcorLV = correctedcurrents(IpriLV,TAPLV,corrLV,CTRLV)
149    # Calculate Operate/Restraint Currents
150    Iop = np.absolute( IcorHV + IcorLV )
151    Irt = np.absolute(IcorHV) + np.absolute(IcorLV)
152    # Calculate Slopes
153    slope = Iop/Irt
154    return(Iop,Irt,slope)

```

Problem 1:

A) Connection Diagrams:

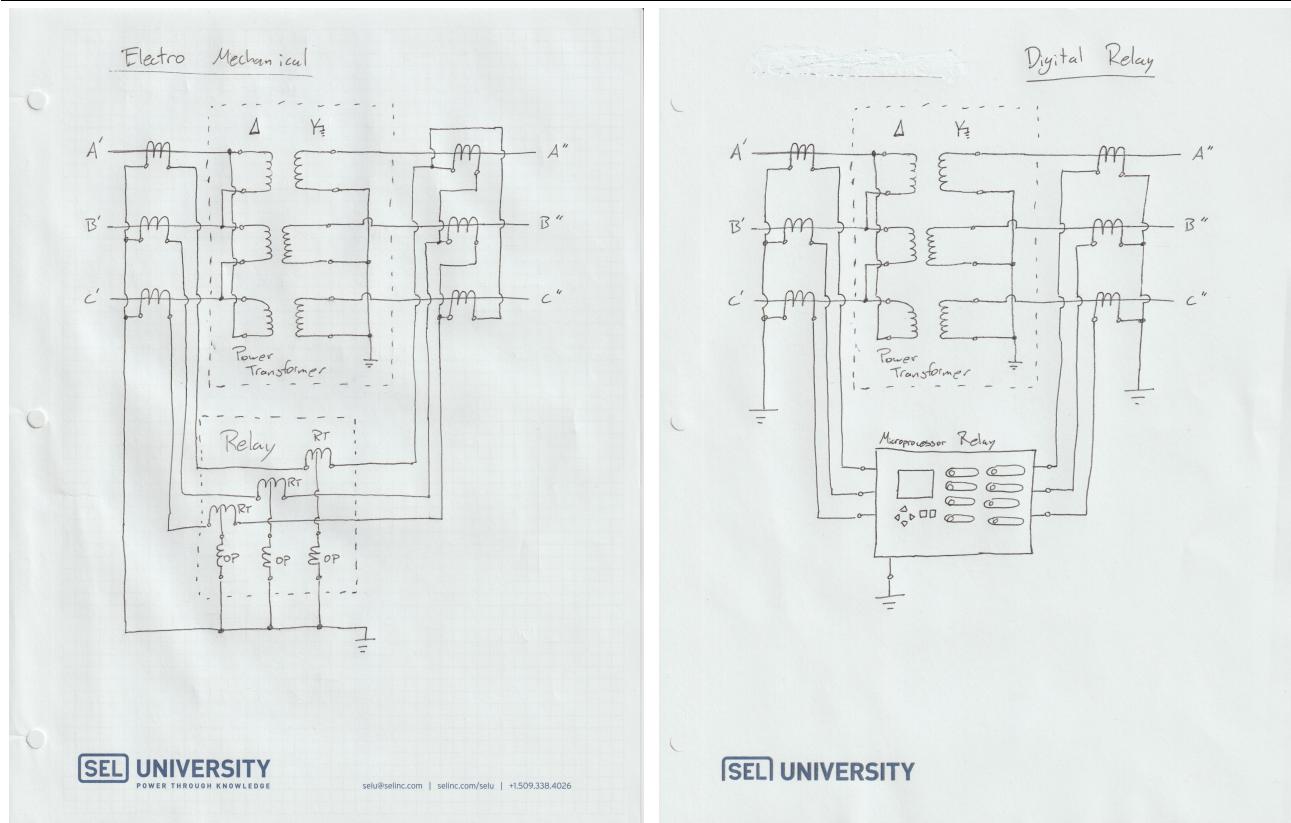

```
In [3]: 1 # Define Parameters:
2 SrcXs1 = 0.4
3 SrcXoR = 30
4 SrcRg = 5/100
5 XfmX = 12/100
6 XfmXoR = 10
7 XfmN = eep.phaseline(Iline=24/345,complex=True)
8 ZL1 = eep.phasor(0.01,85.4)
9
10 # A)
11
12 # Evaluate Impedances
13 Zsrc1 = (SrcRg + SrcXs1 / SrcXoR + 1j*SrcXs1)*eep.zpu(S=250*M,VLL=24*k)
14 print("Source Impedance:",Zsrc1,"Ω")
15 Zxfm1 = (XfmX / XfmXoR + 1j*XfmX)*eep.zpu(S=250*M,VLL=24*k)
16 print("Transformer Impedance:",Zxfm1,"Ω")
17
18 # Evaluate Worst-Case Currents:
19 ILV = eep.phaseline(VLL=24*k)/Zsrc1
20 eep.cprint(ILV/k,"kA","Worst Case Current (Low-Side):")
21 IHV = eep.phaseline(VLL=24*k)/(Zsrc1+Zxfm1) * XfmN
22 eep.cprint(IHV/k,"kA","Worst Case Current (High-Side):")
23
24 # Calculate CT Ratios:
25 print("\nA")
26 CT((abs(ILV),5,"Low-Side CTR:"))
27 CT((abs(IHV),5,"High-Side CTR:"))
28
29
30 # B)
31
32 # Calculate TAP settings
33 LvTAP = protectiontap(abs(ILV)/5,250*M,VLL=24*k)
34 HvTAP = protectiontap(abs(IHV)/5,250*M,VLL=345*k)
35 print("\nB")
36 print("Low-Side TAP Setting:",LvTAP,"A")
37 print("High-Side TAP Setting:",HvTAP,"A")
38
39 # Demonstrate Correction Matrices
40 print("LV-Correction Matrix:\n",XFMD11,"\t(D11)")
41 print("HV-Correction Matrix:\n",XFMY0,"\t(Y0)")
```

Source Impedance: (0.14592+0.9216j) Ω
 Transformer Impedance: (0.027648+0.2764799999999995j) Ω
 Worst Case Current (Low-Side): 14.85 ∠ -81.003° kA
 Worst Case Current (High-Side): 0.46 ∠ -51.757° kA

A)
 Low-Side CTR: 14851 / 5 → 2971
 High-Side CTR: 460 / 5 → 92

B)
 Low-Side TAP Setting: 2.0249142643030043 A
 High-Side TAP Setting: 4.550344309316969 A
 LV-Correction Matrix:

$$\begin{bmatrix} 0.57735027 & -0.57735027 \\ -0.57735027 & 0.57735027 \end{bmatrix}$$
 (D11)
 HV-Correction Matrix:

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$
 (Y0)

C) Pickup setting for the unrestrained overcurrent should be based on the fault current available for faults at 80% of the line (or less) which equates to what is commonly known as zone 1. To calculate these currents in a simple manner, we will use the three-phase fault current available. It's worth noting that this current should only be applied for the phase-protection. Ground and negative sequence currents should be calculated for the other protection elements (50G and 50Q).

```
In [4]: 1 # Evaluate the phase fault current
2 Zeq = Zsrc1+Zxfm1 + 0.8*ZL1*eep.zpu(S=250*M,VLL=24*k)
3 Ifaultzone1 = eep.phaseline(VLL=24*k)/Zeq
4 print("Fault Current:",abs(Ifaultzone1),"A")
5 print("Low-Side Pickup Setting:",abs(Ifaultzone1)/(abs(ILV)/5),"A-secondary")
6 print("High-Side Pickup Setting:",abs(Ifaultzone1 * XfmN)/(abs(IHV)/5),"A-secondary")
```

Fault Current: 11274.69721925425 A
 Low-Side Pickup Setting: 3.7961502030179632 A-secondary
 High-Side Pickup Setting: 4.925160415766922 A-secondary

D) Harmonic restraint and harmonic blocking are two methods primarily used to avoid erroneously tripping during transformer energization (and subsequent inrush). Harmonic restraint was typically applied in electro-mechanical relays as a mode of restraining the operate coil and trip mechanism. Harmonic blocking is a method typically applied in microprocessor relays which monitors the level of second harmonic to make decisions on whether the transformer is currently being energized. These methods should be acting when the transformer is being energized and presents a significant load as itself. During these circumstances, the transformer differential protection will appear to have detected an internal fault. Although it is possible for an internal fault to actually be present, it is likely just the fact that most current is being consumed by the magnetization branch of the transformer to induce the flux appropriately.

E) Slope Setting Calculation

```
In [5]: 1 # Test with some arbitrary balanced current
2 Imag = 100
3 ILV_abc = np.array([eep.phasor(Imag,0),eep.phasor(Imag,-120),eep.phasor(Imag,-240)])
4 IHV_abc = -ILV_abc * XfmN * 0.9 # -10% of nominal turns ratio
5 eep.cprint(ILV_abc,label="Low-Side:")
6 eep.cprint(IHV_abc,label="High-Side:")
7
8 x,x,slp = iopirt(IHV_abc,ILV_abc,HvTAP,LvTAP,corrHV="D-",corrLV="Y",CTRLHV=abs(IHV)/5,CTRLV=abs(ILV)/5)
9
10 print("Calculated Slopes:",slp*100,"%")
11 print("Selected Slope Setting:",np.ceil(slp[0]*100),"%")

[['Low-Side: 100.0 ∠ 0.0° ']
 ['Low-Side: 100.0 ∠ -120.0° ']
 ['Low-Side: 100.0 ∠ 120.0° ']
 [['High-Side: 3.615 ∠ -150.0° ']
 ['High-Side: 3.615 ∠ 90.0° ']
 ['High-Side: 3.615 ∠ -30.0° ']]
Calculated Slopes: [31.61226239 31.61226239 31.61226239] %
Selected Slope Setting: 32.0 %
```

```
In [6]: 1 # F)
2
3 # Define Case Currents
4 CASES = [
5 {"IHV": np.array([eep.phasor(418.37,-175.84),eep.phasor(418.37,64.16),eep.phasor(418.37,-55.84)]),
6 "ILV": np.array([eep.phasor(6014.06,-25.84),eep.phasor(6014.06,-145.84),eep.phasor(6014.06,94.158)]),
7 {"IHV": np.array([eep.phasor(469.504,-175.84),eep.phasor(469.504,64.16),eep.phasor(469.504,-55.84)]),
8 "ILV": np.array([eep.phasor(6224.557,-25.84),eep.phasor(6224.557,-145.84),eep.phasor(6224.557,94.158)]),
9 {"IHV": np.array([eep.phasor(134.270,-129.79),eep.phasor(1*p,100.62),eep.phasor(136.266,-43.052)]),
10 "ILV": np.array([eep.phasor(1580.052,3.132),eep.phasor(1141.957,-129.79),eep.phasor(1158.921,136.948)]),
11 {"IHV": np.array([eep.phasor(1296.862,94.049),eep.phasor(341.511,97.217),eep.phasor(341.511,97.217)]),
12 "ILV": np.array([eep.phasor(8106.92,-87.074),eep.phasor(8106.92,92.926),eep.phasor(1*p,104.036)]),
13 {"IHV": np.array([eep.phasor(1296.862*0.2,94.049),eep.phasor(341.511,97.217),eep.phasor(341.511,97.217)]),
14 "ILV": np.array([eep.phasor(8106.92,-87.074),eep.phasor(8106.92,92.926),eep.phasor(1*p,104.036)]),
15 ]
16
17 # Evaluate Each Set of Top and Int
18 for n,case in enumerate(CASES):
19     IHV = case["IHV"]
20     ILV = case["ILV"]
21     iop,irt,slp = iopirt(IHV,ILV,HvTAP,LvTAP,corrHV="D-",corrLV="Y",CTRLHV=abs(IHV)/5,CTRLV=abs(ILV)/5)
22     print("Case",n+1,"Operate Current:",iop,"A")
23     print("      Restrain Current:",irt,"A")
24     print("      Slope:",np.ceil(slp*100),"%")
```

```
Case 1 Operate Current: [1.3704224 1.3704224 1.3704224] A
      Restrain Current: [3.5680583 3.5680583 3.5680583] A
      Slope: [39. 39. 39.] %
Case 2 Operate Current: [1.3704224 1.3704224 1.3704224] A
      Restrain Current: [3.5680583 3.5680583 3.5680583] A
      Slope: [39. 39. 39.] %
Case 3 Operate Current: [1.5979997 1.51177128 1.3760546] A
      Restrain Current: [3.34052197 3.6172429 3.67481904] A
      Slope: [48. 42. 38.] %
Case 4 Operate Current: [2.46783259 2.46783259 2.46924035] A
      Restrain Current: [2.5043133 2.5043133 2.46924035] A
      Slope: [ 99. 99. 100.] %
Case 5 Operate Current: [2.46783259 2.46783259 2.46924035] A
      Restrain Current: [2.5043133 2.5043133 2.46924035] A
      Slope: [ 99. 99. 100.] %
```

Assuming that the relay should trip the breaker for cases 3, 4, and 5, but should remain closed for cases 1 and 2, it is likely that the slope setting of 40% is safe and secure.

Problem 2:

A)

1. CT saturation can impact internal faults by "limiting" a fault current to a specific level so that in protection logic, the bus currents still sum to zero, even if they really don't. This is an extremely unlikely event due to the circumstances that would have to be aligned to support such operation.
2. CT saturation can affect external faults by making them appear (to the relay) as if they are internal. Because the fault current on one or more CTs press the CT into saturation, and the secondary currents don't accurately reflect the primary currents, the relay will perceive the fault as internal since the bus currents will no longer sum to zero. External faults are more of a concern as this behavior will negatively impact protection coordination and potentially cause false trips and incur large expenses for utilities and their customers.
3. A few options will help reduce saturations effects on security.
 - Increasing CT ratings to reduce risk of saturation will certainly have a great benefit.
 - Using coordinated and communications-assisted protection may be of benefit. In substations, there are no doubt additional relays monitoring the lines fed by busses, the relays protecting these lines (if not using the same CTs as the bus protection relay) could provide confirmation that validates the current differential issue perceived by the bus protection relay. If the line relay's current doesn't match that of the bus protection relay, there is likely a case of saturation.
 - Reducing CT burden can also significantly improve performance by reducing the likelihood of CT saturation.
 - High-speed fault identification and supervisory logic can also be used to determine a fault's presence as internal or external and provide supervisory control to block tripping when necessary.


B) Although ring busses may not be quite as simple to apply differential protection, the method may still apply. Since the driving law (KCL) still applies to ring bus configurations, differential protection can still be used, it just may not be as easy to apply. However, in cases where differential protection cannot be applied, breaking bus protection into two or more zones may also be useful. In such cases, the ability to have a dynamically configurable protection relay (like the SEL-487B) is very useful. Such relays can make decisions on the fly to reconfigure zone protection based on breaker status, load status, or other factors. Such performance can improve overall reliability and security of the system.

C) Breaker failure is essentially just as the name implies. The breaker fails to either open or close on command. In many cases, this issue is presented as a breaker that fails to close, creating what is known as a "phase-open" case where one of three phases remains open and creates unbalance. Such phenomena on a transmission system can cause extremely adverse conditions by welding "fault-like" conditions at other protective devices, or conditions that cause a larger system-wide issue, potentially cascading to system instability. Using breaker monitor logic (monitoring the ANSI 52 contact status of the breaker) and sequence logic, relays should accurately be able to detect such failure and either trip as necessary or transfer the trip command (via communications channel) to another protective device whose action is better suited.

D) In combination with differential logic monitoring the current flow through the transformers, contact and status monitoring devices could be implemented to identify the current tap states for the two transformers. Additionally, directional protection supervision could be utilized to aid in identifying where the current is circulating.

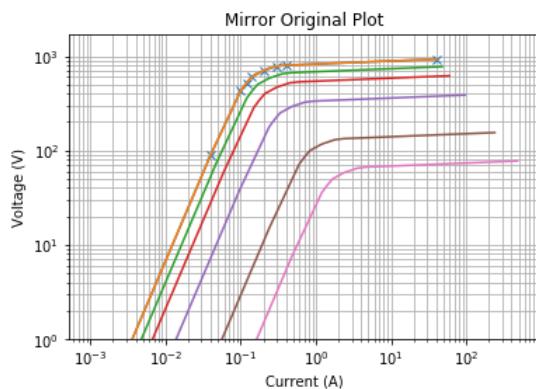Problem 3:

```
In [8]: 1 # Define Givens:
2 CTR = 1200/5
3 CTR_cclass = 600
4 CTR_RpTurn = 0.0024
5 Rlead = 0.81
6 Rstb = 2000
7 VLL_rat = 230*k
8 Sbase = 100*M
9
10 # Define Fault Characteristics
11 PHS3 = 45*k
12 SLG = 40*k
13 LL = 37*k
14
15 # Define CT Data
16 excitation = np.array([[0.001, 0.09],
17                         [0.04, 90],
18                         [0.1, 428],
19                         [0.12, 520],
20                         [0.14, 600],
21                         [0.2, 700],
22                         [0.3, 780],
23                         [0.4, 800],
24                         [40, 927]])
25 TAPS = np.array([240,200,180,160,120,100,80,60,40,20])
26
27 # Define Required Functions
28 def vsetpoint(Rct,k,Rlead,Ifmx,CTR):
29     return(1.5*(Rct+k*Rlead)*Ifmx/CTR)
30 def imin(n,Ie,Irelay,Im,CTR):
31     return((n*Ie+Irelay+Im)*CTR)
32
33 # Define Curve Functions
34 vt = lambda N2 : (N2/CTR * excitation[:,[1]]).reshape(9)
35 Imt = lambda N2 : (CTR/N2 * excitation[:,[0]]).reshape(9)
36 interpolation = lambda x: np.interp(x,Imt(CTR),vt(CTR))
37 neginterp = lambda x: np.interp(x,vt(CTR),Imt(CTR))
38
39 # Plot ALL Curves
40 plt.plot(Imt(CTR),interpolation(Imt(CTR)),'-x')
41 for i in [1,2,4,6,9,10]:
42     tap = TAPS[i-1]
43     plt.plot(Imt(tap),vt(tap))
44 plt.xscale("log")
45 plt.yscale("log")
46 plt.ylim((1,12**3))
47 plt.grid(which="both")
48 plt.title("Mirror Original Plot")
49 plt.xlabel("Current (A)")
50 plt.ylabel("Voltage (V)")
51 plt.show()
```



```
In [9]: 1 # A)
2
3 # Calculate Setpoint Voltage
4 CT_R = CTR_RpTurn * CTR
5 print("CT Resistance:",CT_R,"Ω\n\nA")
6 phs3_set = vsetpoint(CT_R,1,Rlead+Rstb,PHS3,CTR)
7 print("Setpoint Voltage 3-Phase:",phs3_set/k,"kV")
8 slg_set = vsetpoint(CT_R,2,Rlead+Rstb,SLG,CTR)
9 print("Setpoint Voltage SLG:",slg_set/k,"kV")
10 ll_set = vsetpoint(CT_R,2,Rlead+Rstb,LL,CTR)
11 print("Setpoint Voltage Line-Line:",ll_set/k,"kV\n")
12
13 # B)
14
15 # Calculate Minimum Primary Internal Fault Current
16 print("B)")
17 phs3_min = imin(3,neginterp(phs3_set),phs3_set/Rstb,0,CTR)
18 print("Minimum Detectable Current (3-Phase):",phs3_min/k,"kA")
19 slg_min = imin(3,neginterp(slg_set),slg_set/Rstb,0,CTR)
20 print("Minimum Detectable Current (SLG):",slg_min/k,"kA")
21 ll_min = imin(3,neginterp(ll_set),ll_set/Rstb,0,CTR)
22 print("Minimum Detectable Current (Line-Line):",ll_min/k,"kA")
23
24 # C)
25
26 # Recalculate and Print Results
27 print("\nC)")
28 phs3_set = vsetpoint(CT_R,1,Rlead+1200,PHS3,CTR)
29 print("Setpoint Voltage 3-Phase:",phs3_set/k,"kV")
30 slg_set = vsetpoint(CT_R,2,Rlead+1200,SLG,CTR)
31 print("Setpoint Voltage SLG:",slg_set/k,"kV")
32 ll_set = vsetpoint(CT_R,2,Rlead+1200,LL,CTR)
33 print("Setpoint Voltage Line-Line:",ll_set/k,"kV\n")
34 phs3_min = imin(3,neginterp(phs3_set),phs3_set/Rstb,0,CTR)
35 print("Minimum Detectable Current (3-Phase):",phs3_min/k,"kA")
36 slg_min = imin(3,neginterp(slg_set),slg_set/Rstb,0,CTR)
37 print("Minimum Detectable Current (SLG):",slg_min/k,"kA")
38 ll_min = imin(3,neginterp(ll_set),ll_set/Rstb,0,CTR)
39 print("Minimum Detectable Current (Line-Line):",ll_min/k,"kA")
40
41 # D)
42
43 # Recalculate and Print Results
44 print("\nD)")
45 phs3_set = vsetpoint(CT_R,1,Rlead+Rstb,50*k,CTR)
46 print("Setpoint Voltage 3-Phase:",phs3_set/k,"kV")
47 slg_set = vsetpoint(CT_R,2,Rlead+Rstb,45*k,CTR)
48 print("Setpoint Voltage SLG:",slg_set/k,"kV")
49 ll_set = vsetpoint(CT_R,2,Rlead+Rstb,39*k,CTR)
50 print("Setpoint Voltage Line-Line:",ll_set/k,"kV\n")
51 phs3_min = imin(4,neginterp(phs3_set),phs3_set/Rstb,0,CTR)
52 print("Minimum Detectable Current (3-Phase):",phs3_min/k,"kA")
53 slg_min = imin(4,neginterp(slg_set),slg_set/Rstb,0,CTR)
54 print("Minimum Detectable Current (SLG):",slg_min/k,"kA")
55 ll_min = imin(4,neginterp(ll_set),ll_set/Rstb,0,CTR)
56 print("Minimum Detectable Current (Line-Line):",ll_min/k,"kA")
```

CT Resistance: 0.576 Ω

A)

Setpoint Voltage 3-Phase: 562.8898125 kV
 Setpoint Voltage SLG: 1000.549 kV
 Setpoint Voltage Line-Line: 925.5078249999999 kV

B)

Minimum Detectable Current (3-Phase): 96.3467775 kA
 Minimum Detectable Current (SLG): 148.86588 kA
 Minimum Detectable Current (Line-Line): 139.8609389999997 kA

C)

Setpoint Voltage 3-Phase: 337.8898125 kV
 Setpoint Voltage SLG: 600.549 kV
 Setpoint Voltage Line-Line: 555.5078249999999 kV

Minimum Detectable Current (3-Phase): 69.3467775000002 kA
 Minimum Detectable Current (SLG): 100.86588 kA
 Minimum Detectable Current (Line-Line): 95.46093899999998 kA

D)

Setpoint Voltage 3-Phase: 625.433125 kV
 Setpoint Voltage SLG: 1125.617625 kV

Setpoint Voltage Line-Line: 975.5352750000001 kV

Minimum Detectable Current (3-Phase): 113.451975 kA

Minimum Detectable Current (SLG): 173.474115 kA

Minimum Detectable Current (Line-Line): 155.464233 kA

In []:

1