


Joe Stanley

ECE 525

Homework 1

```
In [1]: 1 # Import Libraries to Support Calculations
2 import numpy as np
3 import matplotlib.pyplot as plt
4 import eepower as eep
5 from eepower import u,m,k,M
```

Problem 1

 

Where the following are given as CT and VT secondary quantities::

$$E_{SA} := 70V \cdot e^{j \cdot 0 \text{deg}}$$

$$E_{SB} := 70V \cdot e^{-j \cdot 30 \text{deg}}$$

$$Z_{SA1} := 1.5 \text{ohm} \cdot e^{j \cdot 87 \text{deg}}$$

$$Z_{SA2} := Z_{SA1}$$

$$Z_{SA0} := 5 \text{ohm} \cdot e^{j \cdot 87 \text{deg}}$$

$$Z_{SB1} := 0.8 \text{ohm} \cdot e^{j \cdot 83 \text{deg}}$$

$$Z_{SB2} := Z_{SB1}$$

$$Z_{SB0} := 2.5 \text{ohm} \cdot e^{j \cdot 83 \text{deg}}$$

$$Z_{L1} := 5 \text{ohm} \cdot e^{j \cdot 82 \text{deg}}$$

$$Z_{L0} := 18 \text{ohm} \cdot e^{j \cdot 82 \text{deg}}$$

The current transformer ratios are: $CTR := \frac{1200}{5}$

The voltage transformer ratios are: $VTR := \frac{132.8 \text{kV}}{70V}$ Line-to-neutral

In [2]:

```
1  # Define Givens
2  Esa = eep.phasor(70,0)
3  Esb = eep.phasor(70,-30)
4  Zsa1 = eep.phasor(1.5,87)
5  Zsa2 = Zsa1
6  Zsa0 = eep.phasor(5,87)
7  Zsb1 = eep.phasor(0.8,83)
8  Zsb2 = Zsb1
9  Zsb0 = eep.phasor(2.5,83)
10 ZL1 = eep.phasor(5,82)
11 ZL2 = eep.phasor(18,82)
12 CTR = 1200/5
13 VTR = PTR = 132.8*k/70 # Line-Neutral
14 ZR = PTR/CTR
15
16 # A) Convert to primary values
17 Zsa1_prim = Zsa1 * ZR
18 Zsa2_prim = Zsa1_prim
19 Zsa0_prim = Zsa0 * ZR
20 Zsb1_prim = Zsb1 * ZR
21 Zsb2_prim = Zsb1_prim
22 Zsb0_prim = Zsb0 * ZR
23 ZL1_prim = ZL1 * ZR
24 ZL2_prim = ZL2 * ZR
25 eep.cprint(Zsa1_prim,"Ohms", "ZSA1-Primary")
26 eep.cprint(Zsa2_prim,"Ohms", "ZSA2-Primary")
27 eep.cprint(Zsa0_prim,"Ohms", "ZSA0-Primary")
28 eep.cprint(Zsb1_prim,"Ohms", "ZSB1-Primary")
29 eep.cprint(Zsb2_prim,"Ohms", "ZSB2-Primary")
30 eep.cprint(Zsb0_prim,"Ohms", "ZSB0-Primary")
31 eep.cprint(ZL1_prim,"Ohms", "ZL1-Primary")
32 eep.cprint(ZL2_prim,"Ohms", "ZL2-Primary")
33 Esa_prim = Esa * PTR
34 Esb_prim = Esb * PTR
35 eep.cprint(Esa_prim/k,"kV", "ESA-Primary")
36 eep.cprint(Esb_prim/k,"kV", "ESB-Primary")
37 # Evaluate Zeq to find Line Current
38 Zeq1 = Zsa1_prim + Zsb1_prim + ZL1_prim
39 Zeq2 = Zsa2_prim + Zsb2_prim + ZL2_prim
40 Zeq0 = Zsa0_prim + Zsb0_prim
41 # Find Line Current
42 Iline_prim = (Esa_prim - Esb_prim) / Zeq1
43 eep.cprint(Iline_prim,"A", "Line Current (Primary):")
44 # Convert Line Current to Secondary, Accounting for Polarity
45 Iline_sec_R1 = Iline_prim / CTR
46 Iline_sec_R2 = - Iline_sec_R1
47 eep.cprint(Iline_sec_R1,"A", "Relay-1 Line Current:")
48 eep.cprint(Iline_sec_R2,"A", "Relay-2 Line Current:")
```

ZSA1-Primary 11.857 \angle 87.0° Ohms
ZSA2-Primary 11.857 \angle 87.0° Ohms
ZSA0-Primary 39.524 \angle 87.0° Ohms
ZSB1-Primary 6.324 \angle 83.0° Ohms
ZSB2-Primary 6.324 \angle 83.0° Ohms
ZSB0-Primary 19.762 \angle 83.0° Ohms
ZL1-Primary 39.524 \angle 82.0° Ohms
ZL2-Primary 142.286 \angle 82.0° Ohms
ESA-Primary 132.8 \angle 0.0° kV
ESB-Primary 132.8 \angle -30.0° kV
Line Current (Primary): 1191.994 \angle -8.136° A
Relay-1 Line Current: 4.967 \angle -8.136° A
Relay-2 Line Current: 4.967 \angle 171.864° A

In [6]:

```
1 # B) Repeat Part A in Per-Unit
2 # Define Per-Unit Quantities
3 Sbase = 100*M
4 VbLN = 132.8*k
5 VbLL = eep.phaseline(VLN = VbLN)
6 Zbase = eep.zpu(Sbase,VLN=VbLN)
7 Ibase = eep.ipu(Sbase,VLL=VbLL)
8 # Display Results
9 eep.cprint(Zsa1_prim/Zbase,"PU-Ohms","ZSA1-Primary")
10 eep.cprint(Zsa2_prim/Zbase,"PU-Ohms","ZSA2-Primary")
11 eep.cprint(Zsa0_prim/Zbase,"PU-Ohms","ZSA0-Primary")
12 eep.cprint(Zsb1_prim/Zbase,"PU-Ohms","ZSB1-Primary")
13 eep.cprint(Zsb2_prim/Zbase,"PU-Ohms","ZSB2-Primary")
14 eep.cprint(Zsb0_prim/Zbase,"PU-Ohms","ZSB0-Primary")
15 eep.cprint(ZL1_prim/Zbase,"PU-Ohms","ZL1-Primary")
16 eep.cprint(ZL2_prim/Zbase,"PU-Ohms","ZL2-Primary")
17 eep.cprint(Esa_prim/VbLL,"PU-V","ESA-Primary")
18 eep.cprint(Esb_prim/VbLL,"PU-V","ESB-Primary")
```

```
ZSA1-Primary 0.022 ∠ 87.0° PU-Ohms
ZSA2-Primary 0.022 ∠ 87.0° PU-Ohms
ZSA0-Primary 0.075 ∠ 87.0° PU-Ohms
ZSB1-Primary 0.012 ∠ 83.0° PU-Ohms
ZSB2-Primary 0.012 ∠ 83.0° PU-Ohms
ZSB0-Primary 0.037 ∠ 83.0° PU-Ohms
ZL1-Primary 0.075 ∠ 82.0° PU-Ohms
ZL2-Primary 0.269 ∠ 82.0° PU-Ohms
ESA-Primary 0.577 ∠ 0.0° PU-V
ESB-Primary 0.577 ∠ -30.0° PU-V
```

In [20]:

```
1 # C) Evaluate Power Flow
2 # Define Power Flow from Bus Function
3 def pflowatbus(VLNsrc,Zsrc,Iline,phs=3,scale=k,round=None):
4     # Condition Inputs
5     scale = float(scale)
6     phs = int(phs)
7     # Find Bus Voltage
8     Vbus = VLNsrc - Iline * Zsrc
9     # Find Power Flow at Bus
10    Sbus = (phs) * Vbus * np.conj(Iline) / scale
11    # Break into Real/Reactive
12    Pbus = Sbus.real
13    Qbus = Sbus.imag
14    ret = [Pbus,Qbus,abs(Sbus)]
15    if round is not None:
16        ret = np.around(ret,round)
17    return(ret)
18
19 Pa, Qa, Sa = pflowatbus(Esa_prim,Zsa1_prim,Iline_prim,scale=M,round=3)
20 print("Real Power Measured at Bus-A:",Pa,"MW")
21 print("Reactive Power Meas. at Bus-A:",Qa,"MVar")
22
23 Pb, Qb, Sb = pflowatbus(Esb_prim,Zsb1_prim,-Iline_prim,scale=M,round=3)
24 print("Real Power Measured at Bus-B:",Pb,"MW")
25 print("Reactive Power Meas. at Bus-B:",Qb,"MVar")
```

```
Real Power Measured at Bus-A: 467.465 MW
Reactive Power Meas. at Bus-A: 16.739 MVar
Real Power Measured at Bus-B: -444.018 MW
Reactive Power Meas. at Bus-B: 150.093 MVar
```

```

In [58]: 1 # D) Find the Effective Impedance
2 # Define effective element calculator function
3 def effectivez(VLNsrc,Zsrc,Ilineseq,Zlineseq,PTR,CTR,round=None):
4     # Break out Sequence Terms
5     I0, I1, I2 = Ilineseq
6     Z0, Z1, Z2 = Zlineseq
7     # Ensure that Z-components are imaginary
8     if(not isinstance(Z0, complex)): Z0 *= 1j
9     if(not isinstance(Z1, complex)): Z1 *= 1j
10    if(not isinstance(Z2, complex)): Z2 *= 1j
11    # Find Bus Voltage
12    Vbus = VLNsrc - I1 * Zsrc
13    # Evaluate Secondary Bus Voltage
14    Vbus2nd = Vbus / PTR
15    # Calculate ko
16    ko = (Z0-Z1)/Z0
17    # Find the Secondary Current
18    Irelay = I1 / CTR
19    # Calculate Effective Z-AG
20    Zag_eff = Vbus2nd / (Irelay + ko*I0)
21    ret = [Zag_eff]
22    if round is not None:
23        ret = np.around(ret,round)
24    return(ret)
25
26 eep.cprint(effectivez(Esa_prim,Zsa1_prim,[0,Iline_prim,0],
27                      [Zsa0_prim,Zsa1_prim,Zsa2_prim],PTR,CTR,3),
28            "ohms","Effective Impedance From Relay 1:")
29 eep.cprint(effectivez(Esb_prim,Zsb1_prim,[0,-Iline_prim,0],
30                      [Zsb0_prim,Zsb1_prim,Zsb2_prim],PTR,CTR,3),
31            "ohms","Effective Impedance From Relay 2:")

```

Effective Impedance From Relay 1: 13.883 \angle 2.052° ohms
Effective Impedance From Relay 2: 13.911 \angle 161.321° ohms

In [69]:

```
1  # E) 3-Phase Fault (Load Flow Ignored!)
2  # Evaluate the line impedance
3  Za = Zsa1 + 0.3*ZL1
4  Zb = Zsb1 + 0.7*ZL1
5  Zth = eep.parallelz((Za,Zb))
6  # Calculate Fault Current
7  Ifault_sec = eep.fault.phs3(Esa,[None,Zth,None],sequence=False)
8  eep.cprint(Ifault_sec,"A-sec",["IA-Fault","IB-Fault","IC-Fault"])
9  # Scale Fault Current to Primary
10 Ifault_pri = Ifault_sec * CTR
11 eep.cprint(Ifault_pri,"A-pri",["IA-Fault","IB-Fault","IC-Fault"])
12 print()
13 # Divide Currents into Different Branches
14 IA_sec = Ifault_sec[0]
15 IA_pri = Ifault_pri[0]
16 IR1_sec = eep.curdiv(Za,(Zb,),Iin=IA_sec)
17 IR2_sec = eep.curdiv(Zb,(Za,),Iin=IA_sec)
18 eep.cprint([IR1_sec,IR2_sec],"A-sec",["Relay-1 Current","Relay-2 Current"])
19 IR1_pri = eep.curdiv(Za,(Zb,),Iin=IA_pri)
20 IR2_pri = eep.curdiv(Zb,(Za,),Iin=IA_pri)
21 eep.cprint([IR1_pri,IR2_pri],"A-pri",["Relay-1 Current","Relay-2 Current"])
22 print()
23
24 # Compare with Load Flow
25 print("Relay 1:")
26 eep.cprint(Iline_sec_R1,"A-sec","\tLoad Current:")
27 eep.cprint(IR1_sec,"A-sec","\tFault Current:")
28 eep.cprint(IR1_sec/Iline_sec_R1,"",""\tRatio:")
29 print("Relay 2:")
30 eep.cprint(Iline_sec_R2,"A-sec","\tLoad Current:")
31 eep.cprint(IR2_sec,"A-sec","\tFault Current:")
32 eep.cprint(IR2_sec/Iline_sec_R2,"",""\tRatio:")
33 print()
34
35 # Calculate Effective Impedance
36 eep.cprint(effectivez(Esa_prim,Zsa1_prim,[0,IR1_pri,0],
37                     [Zsa0_prim,Zsa1_prim,Zsa2_prim],PTR,CTR,3),
38           "ohms","Effective Impedance From Relay 1:")
39 eep.cprint(effectivez(Esb_prim,Zsb1_prim,[0,IR2_pri,0],
40                     [Zsb0_prim,Zsb1_prim,Zsb2_prim],PTR,CTR,3),
41           "ohms","Effective Impedance From Relay 2:")
42
43 # Ioperate and Irestraint
44 Icap_a_sec = (100/2)/CTR * 1j
45 Icap_b_sec = Icap_a_sec
46 Ioperate = Icap_a_sec + Icap_b_sec + Iline_sec_R2 + Iline_sec_R1
47 eep.cprint(Ioperate,"A-sec","I-Operate (Load)")
48 Irestrain = abs(Icap_a_sec) + abs(Icap_b_sec) + abs(Iline_sec_R2) + abs(Iline_sec_R1)
49 print("I-Restrain (Load)",Irestrain,"A-sec")
50 Ioperate = Icap_a_sec + Icap_b_sec + IR2_sec + IR1_sec
51 eep.cprint(Ioperate,"A-sec","I-Operate (Fault)")
52 Irestrain = abs(Icap_a_sec) + abs(Icap_b_sec) + abs(IR2_sec) + abs(IR1_sec)
53 print("I-Restrain (Fault)",Irestrain,"A-sec")
```

```
[['IA-Fault 39.627 ∠ -83.55° A-sec']
 ['IB-Fault 39.627 ∠ 156.45° A-sec']
 ['IC-Fault 39.627 ∠ 36.45° A-sec']]
[['IA-Fault 9510.524 ∠ -83.55° A-pri']
 ['IB-Fault 9510.524 ∠ 156.45° A-pri']
 ['IC-Fault 9510.524 ∠ 36.45° A-pri']]
```

```
[['Relay-1 Current 23.356 ∠ -84.5° A-sec']
 ['Relay-2 Current 16.279 ∠ -82.186° A-sec']]
[['Relay-1 Current 5605.335 ∠ -84.5° A-pri']
 ['Relay-2 Current 3907.067 ∠ -82.186° A-pri']]
```

Relay 1:

Load Current: 4.967 ∠ -8.136° A-sec
Fault Current: 23.356 ∠ -84.5° A-sec
Ratio: 4.702 ∠ -76.364°

Relay 2:

Load Current: $4.967 \angle 171.864^\circ$ A-sec
Fault Current: $16.279 \angle -82.186^\circ$ A-sec
Ratio: $3.278 \angle 105.95^\circ$

Effective Impedance From Relay 1: $1.5 \angle 81.989^\circ$ ohms
Effective Impedance From Relay 2: $3.636 \angle 45.713^\circ$ ohms
I-Operate (Load) $0.417 \angle 90.0^\circ$ A-sec
I-Restrain (Load) 10.349952568074297 A-sec
I-Operate (Fault) $39.213 \angle -83.481^\circ$ A-sec
I-Restrain (Fault) 40.0516745616 A-sec

In []: 1

In []: 1