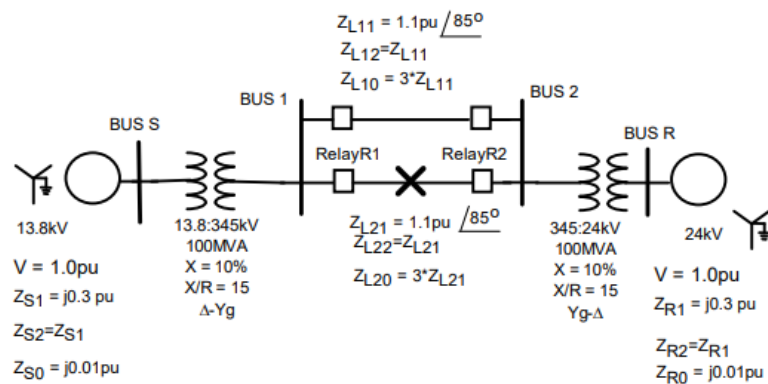


# Joe Stanley

## ECE 523 - HWK 4

```
In [1]: 1 # Import Libraries
2 import numpy as np
3 import matplotlib.pyplot as plt
4 import tabulate as tab
5 import electricpy as ep
6 from electricpy.constants import *
7 import numdifftools as ndt
```

1. Do the following for the circuit below using  $Z_{bus}$  matrix methods assuming faults 33% of the way down line 2 (the lower of the two lines). No change of base calculations needed.
  - a. Set the voltage source at Bus S is 1.0 at -30 degrees (this is to account for the transformer phase shift), and the voltage at Bus R to be 1.0 is -50 degrees. Calculate the prefault voltage magnitude and angle at each bus, including the fault point based on the prefault power flow. Check your results with a Powerworld or a similar program.
  - b. Calculate the voltages and currents in the sequence domain and in the abc domain at RelayR1 and RelayR2, for 3 phase, SLG, LL, and DLG faults with  $R_f = 0.3$  pu (for the DLG put the resistance in the ground path). Again, check your results with Powerworld or a similar program.



In [16]:

```
1 # Define Parameters
2 ZS1 = 0.3j
3 ZS0 = 0.01j
4 ZR1 = ZS1
5 ZR0 = ZS0
6 ZL11 = ep.phasor(1.1,85)
7 print(ZL11)
8 ZL10 = 3*ZL11
9 print(ZL10)
10 ZL21 = ZL11
11 ZL20 = 3*ZL21
12 ZT1 = ep.rxrecompose(0.1,15)
13 ZT2 = ZT1
14
15 # Generate Z-Bus Matrices
16 # 1 - 2 - f - S - R
17 ybus1 = np.array([
18     [1/ZL11+1/(ZL21*33/100)+1/ZT1, -1/ZL11, -1/(ZL21*33/100), -en30/ZT1, 0],
19     [-1/ZL11, 1/ZL11+1/(ZL21*67/100)+1/ZT2, -1/(ZL21*67/100), 0, -en30/ZT2],
20     [-1/(ZL21*33/100), -1/(ZL21*67/100), 1/(ZL21*33/100)+1/(ZL21*67/100), 0, 0],
21     [-en30/ZT1, 0, 0, 1/ZT1+1/ZS1, 0],
22     [0, -en30/ZT2, 0, 0, 1/ZT2+1/ZR1]
23 ])
24 zbus1 = np.linalg.inv(ybus1)
25 zbus2 = np.linalg.inv(np.array([
26     [1/ZL11+1/(ZL21*33/100)+1/ZT1, -1/ZL11, -1/(ZL21*33/100), -en30/ZT1, 0],
27     [-1/ZL11, 1/ZL11+1/(ZL21*67/100)+1/ZT2, -1/(ZL21*67/100), 0, -en30/ZT2],
28     [-1/(ZL21*33/100), -1/(ZL21*67/100), 1/(ZL21*33/100)+1/(ZL21*67/100), 0, 0],
29     [-en30/ZT1, 0, 0, 1/ZT1+1/ZS1, 0],
30     [0, -en30/ZT2, 0, 0, 1/ZT2+1/ZR1]
31 ]))
32 zbus0 = np.linalg.inv(np.array([
33     [1/ZL10+1/(ZL20*33/100), -1/ZL10, -1/(ZL20*33/100), 0, 0],
34     [-1/ZL10, 1/ZL10+1/(ZL20*67/100), -1/(ZL20*67/100), 0, 0],
35     [-1/(ZL20*33/100), -1/(ZL20*67/100), 1/(ZL20*33/100)+1/(ZL20*67/100), 0, 0],
36     [0, 0, 0, 1/ZS0, 0],
37     [0, 0, 0, 0, 1/ZR0]
38 ]))
39 def around(arr,val):
40     tol = 1e+14
41     arr = np.around(arr,val)
42     arr.real[abs(arr.real) > tol] = 0.0
43     arr.imag[abs(arr.imag) > tol] = 0.0
44     return(arr)
45 print("\nPositive Sequence Z-Bus:")
46 print(tab.tabulate(np.asarray(np.around(zbus1,3),dtype=str),tablefmt="fancy_grid"))
47 print("\nNegative Sequence Z-Bus:")
48 print(tab.tabulate(np.asarray(np.around(zbus2,3),dtype=str),tablefmt="fancy_grid"))
49 print("\nZero Sequence Z-Bus:")
50 print(tab.tabulate(np.asarray(around(zbus0,5),dtype=str),tablefmt="fancy_grid"))
51
52 # Calculate Basic Power Transfer from Sending to Receiving
53 Vsnd = ep.phasor(1,-30)
54 Vrec = ep.phasor(1,-50)
55 Zsr1 = zbus1[3][4]
56 print("Send-Receive Positive Sequence Impedance:",np.around(Zsr1,3),"Ω-pu")
57 Pflow = ep.powerflow(Vsnd,Vrec,Zsr1)
58 print("Power Flow:",Pflow,"pu-VA")
59
60 # Define Lists for Power Flow Analysis
61 Vlist = [[None,None],[None,None],[None,None],[1,-np.radians(30)],[None,None]]
62 Plist = [0,0,0,None,-round(Pflow.real,3)]
63 Qlist = [0,0,0,None,-round(Pflow.imag,3)]
64
65 # Perform Power Flow Calculation
66 res, ct = ep.sim.mbuspowerflow(ybus1,Vlist,Plist,Qlist,
67     degrees=True,split=True,returnct=True,slackbus=3)
68 ang, mag = res
69 print(ang,mag)
70 print(ct)
```

(0.09587131702242396+1.0958141679009201j)  
(0.2876139510672719+3.2874425037027604j)

Positive Sequence Z-Bus:

(0.008+0.281j)	(-0.001+0.119j)	(0.005+0.228j)	(0.108+0.182j)	(0.042+0.078j)
----------------	-----------------	----------------	----------------	----------------

$(-0.001+0.119j)$	$(0.008+0.281j)$	$(0.002+0.172j)$	$(0.042+0.078j)$	$(0.108+0.182j)$
$(0.005+0.228j)$	$(0.002+0.172j)$	$(0.025+0.452j)$	$(0.086+0.147j)$	$(0.064+0.112j)$
$(-0.103+0.184j)$	$(-0.047+0.076j)$	$(-0.085+0.148j)$	$(0.003+0.233j)$	$(-0.003+0.067j)$
$(-0.047+0.076j)$	$(-0.103+0.184j)$	$(-0.065+0.111j)$	$(-0.003+0.067j)$	$(0.003+0.233j)$

Negative Sequence Z-Bus:

$(0.008+0.281j)$	$(-0.001+0.119j)$	$(0.005+0.228j)$	$(-0.103+0.184j)$	$(-0.047+0.076j)$
$(-0.001+0.119j)$	$(0.008+0.281j)$	$(0.002+0.172j)$	$(-0.047+0.076j)$	$(-0.103+0.184j)$
$(0.005+0.228j)$	$(0.002+0.172j)$	$(0.025+0.452j)$	$(-0.085+0.148j)$	$(-0.065+0.111j)$
$(0.108+0.182j)$	$(0.042+0.078j)$	$(0.086+0.147j)$	$(0.003+0.233j)$	$(-0.003+0.067j)$
$(0.042+0.078j)$	$(0.108+0.182j)$	$(0.064+0.112j)$	$(-0.003+0.067j)$	$(0.003+0.233j)$

Zero Sequence Z-Bus:

0j	0j	0j	0j	0j
0j	0j	0j	0j	0j
0j	0j	0j	0j	0j
0j	0j	0j	0.01j	0j
0j	0j	0j	0j	0.01j

Send-Receive Positive Sequence Impedance:  $(-0.003+0.067j)$   $\Omega$ -pu

Power Flow:  $(-0.23283588191211826-5.12234860047134j)$  pu-VA


C:\Users\Joe Stanley\Anaconda3\lib\site-packages\electricpy-0.0.6-py3.6.egg\electricpy\sim.py:806: UserWarning: WARNING: Singular matrix, attempting LSQ method.

$[-1.02277047e+12 \quad 3.55713241e+01 \quad 8.42739959e-01 \quad -3.45680717e+00] \quad [-1.10405705e-10 \quad 1.00000000e+00 \quad 1.00000000e+00 \quad 1.00000000e+00]$

7

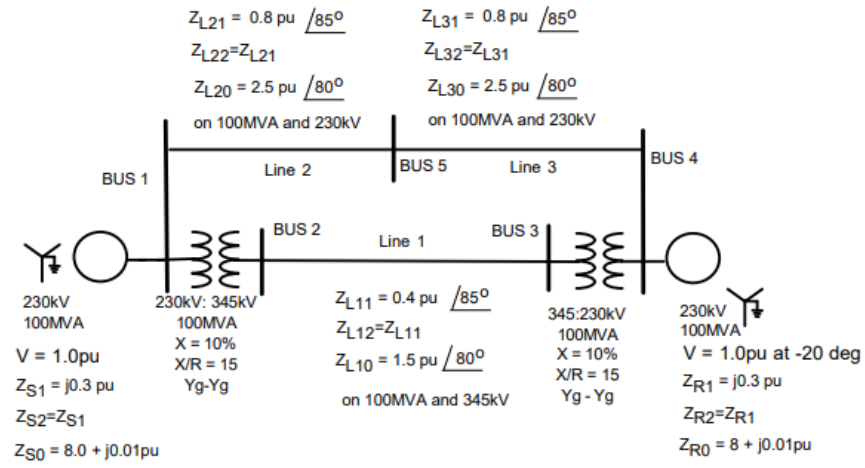2. Given the system below do the following:

- Sketch the sequence equivalent circuits series faults occurring on line 1 (Bus 2-Bus3) and reduce them to simplified equivalents. The voltages given are at BUS1 and BUS4, **not the voltages behind the source impedances**.
- Determine the phase currents from Bus1 to Bus 5 and from Bus 2 to Bus 3 if phase C is open on line 1 (treat it as the breakers at Bus 2 on phase C is open and phases A and B are closed)
- Repeat part (b) if the transformer from Bus 1-Bus 2 is Y ungrounded on the HV side.
- Determine the phase currents from Bus1 to Bus 5 and from Bus 2 to Bus 3 if phases B and C are open on line 1 (treat this as the breaker having phase A closed and phases B and C open)
- Repeat part (d) if the transformer from Bus 1-Bus 2 is Y ungrounded on the HV side.
- Suppose that line 3 is series compensated, with each phase having a capacitive impedance of  $-j0.3pu$ . The capacitor on phase A is bypassed by a misoperating circuit breaker and phases B and C are inserted. Calculate the currents from Bus1 to Bus 5 and from Bus 2 to Bus 3. Model Za and Zb as being the capacitor only. Do not lump in the line impedance.
- Verify your results using transient simulation



In [19]:

```
1 # Define Givens
2 VR = ep.phasor(1,-20)
3 VS = 1 # no known angle
4 Zs1 = 0.3j
5 Zs0 = 8+0.01j
6 Zr1 = 0.3j
7 Zr0 = 8+0.01j
8 Zt1 = ep.rxrecompose(0.1,15)
9 Zt2 = ep.rxrecompose(0.1,15)
10 ZL11 = ep.phasor(0.4,85)
11 ZL10 = ep.phasor(1.5,80)
12 ZL21 = ep.phasor(0.8,85)
13 ZL20 = ep.phasor(2.5,80)
14 ZL31 = ep.phasor(0.8,85)
15 ZL30 = ep.phasor(2.5,80)
16
17 # Define Positive Sequence Y-Bus Matrix
18 # BUS: 1 - 2 - 3 - 4 - 5
19 ybus1 = np.array([
20     [1/Zs1+1/ZL21+1/Zt1, -1/Zt1,0,0,-1/ZL21],
21     [-1/Zt1,1/Zt1+1/ZL11,-1/ZL11,0,0],
22     [0,-1/ZL11,1/ZL11+1/Zt2,-1/Zt2,0],
23     [0,0,-1/Zt2,1/Zt2+1/ZL31+1/Zr1,-1/ZL31],
24     [-1/ZL21,0,0,-1/ZL31,1/ZL21+1/ZL31],
25 ])
26 # Define Zero Sequence Y-Bus Matrix
27 ybus0 = np.array([
28     [1/Zs0+1/ZL20+1/Zt1, -1/Zt1,0,0,-1/ZL20],
29     [-1/Zt1,1/Zt1+1/ZL10,-1/ZL10,0,0],
30     [0,-1/ZL10,1/ZL10+1/Zt2,-1/Zt2,0],
31     [0,0,-1/Zt2,1/Zt2+1/ZL30+1/Zr0,-1/ZL30],
32     [-1/ZL20,0,0,-1/ZL30,1/ZL20+1/ZL30],
33 ])
34
35 # Calculate Z-Bus Matrices
36 zbus1 = np.linalg.inv(ybus1)
37 zbus2 = np.linalg.inv(ybus1)
38 zbus0 = np.linalg.inv(ybus0)
39 print("\nPositive Sequence Z-Bus:")
40 print(tab.tabulate(np.asarray(np.around(zbus1,3),dtype=str),tablefmt="fancy_grid"))
41 print("\nNegative Sequence Z-Bus:")
42 print(tab.tabulate(np.asarray(np.around(zbus2,3),dtype=str),tablefmt="fancy_grid"))
43 print("\nZero Sequence Z-Bus:")
44 print(tab.tabulate(np.asarray(np.around(zbus0,3),dtype=str),tablefmt="fancy_grid"))
45
46 # Evaluate the Voltage at Faulted Bus
47 Pflow = ep.powerflow(VR,VS,zbus1[1][4])
48 Pflow = 0 + Pflow.imag*1j # Real Part is Essentially Zero
49 print("\nPower Flow:",Pflow,"pu-VA")
50
51 # Evaluate Faults for 1-Pole-Open
52 Zseq = [zbus0[2][2], zbus1[2][2], zbus2[2][2]]
53 Iphs = ep.fault.poleopen1(1,Zseq,sequence=False,reference='C')
54 print("\nBus 2 Phase Currents (1-Pole Open Case):")
55 ep.cprint(Iphs,"A-pu",["IA","IB","IC"])
56
57 # Evaluate Fault for 2-Pole-Open
58 Zseq = [zbus0[2][2], zbus1[2][2], zbus2[2][2]]
59 Iphs = ep.fault.poleopen2(1,Zseq,sequence=False,reference='A')
60 print("\nBus 2 Phase Currents (2-Pole Open Case):")
61 ep.cprint(Iphs,"A-pu",["IA","IB","IC"])
```

Positive Sequence Z-Bus:

(0.003+0.213j)	(0.002+0.192j)	(-0.002+0.108j)	(-0.003+0.087j)	(-0+0.15j)
(0.002+0.192j)	(0.008+0.261j)	(-0.001+0.139j)	(-0.002+0.108j)	(-0+0.15j)
(-0.002+0.108j)	(-0.001+0.139j)	(0.008+0.261j)	(0.002+0.192j)	(-0+0.15j)
(-0.003+0.087j)	(-0.002+0.108j)	(0.002+0.192j)	(0.003+0.213j)	(-0+0.15j)
(-0+0.15j)	(-0+0.15j)	(-0+0.15j)	(-0+0.15j)	(0.035+0.548j)

Negative Sequence Z-Bus:

(0.003+0.213j)	(0.002+0.192j)	(-0.002+0.108j)	(-0.003+0.087j)	(-0+0.15j)
(0.002+0.192j)	(0.008+0.261j)	(-0.001+0.139j)	(-0.002+0.108j)	(-0+0.15j)
(-0.002+0.108j)	(-0.001+0.139j)	(0.008+0.261j)	(0.002+0.192j)	(-0+0.15j)
(-0.003+0.087j)	(-0.002+0.108j)	(0.002+0.192j)	(0.003+0.213j)	(-0+0.15j)
(-0+0.15j)	(-0+0.15j)	(-0+0.15j)	(-0+0.15j)	(0.035+0.548j)

Zero Sequence Z-Bus:

(4.075+0.308j)	(4.069+0.272j)	(3.931-0.262j)	(3.925-0.298j)	(4+0.005j)
(4.069+0.272j)	(4.071+0.334j)	(3.936-0.224j)	(3.931-0.262j)	(4+0.005j)
(3.931-0.262j)	(3.936-0.224j)	(4.071+0.334j)	(4.069+0.272j)	(4+0.005j)
(3.925-0.298j)	(3.931-0.262j)	(4.069+0.272j)	(4.075+0.308j)	(4+0.005j)
(4+0.005j)	(4+0.005j)	(4+0.005j)	(4+0.005j)	(4.217+1.236j)

Power Flow: 2.280134288837792j pu-VA

Bus 2 Phase Currents (1-Pole Open Case):

```
[['IA 3.494 ∠ -178.779° A-pu']
 ['IB 3.132 ∠ 2.12° A-pu']
 ['IC 0.0 ∠ 0.0° A-pu']]
```

Bus 2 Phase Currents (2-Pole Open Case):

```
[['IA 0.719 ∠ -11.834° A-pu']
 ['IB 0.0 ∠ 90.0° A-pu']
 ['IC 0.0 ∠ 90.0° A-pu']]
```

In [4]:

1

(0.0066666666666667+0.1j)

In [ ]:

1