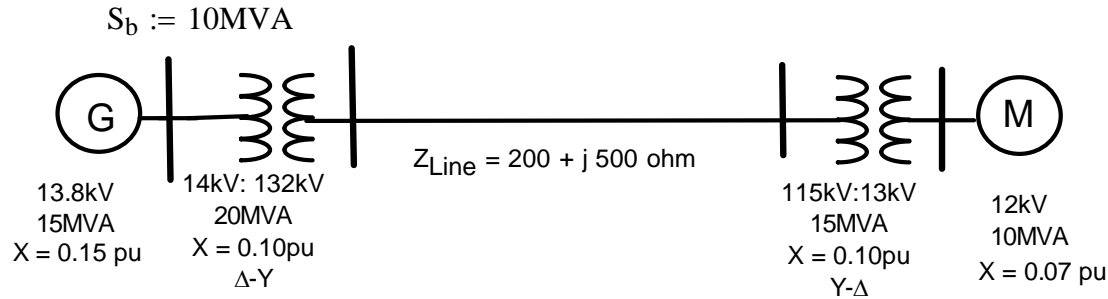


ECE 523: Homework #1

Solution

$$\text{MVA} := 1000\text{kW} \quad \text{MVAR} := \text{MVA} \quad \text{pu} := 1$$

1. Problem 1.1 in the text book



Divide the system into 3 zones. Zone I is the generator, Zone II is the transmission line, and Zone III is the motor. The transformers are the boundaries between zones.

Zone II Calculations:

$$V_{b2} := 100\text{kV}$$

$$Z_{b2} := \frac{V_{b2}^2}{S_b} \quad Z_{b2} = 1000 \Omega$$

$$Z_{\text{line}} := 200\text{ohm} + j \cdot 500\text{ohm}$$

$$Z_{\text{line_pu}} := \frac{Z_{\text{line}}}{Z_{b2}} \quad Z_{\text{line_pu}} = (0.2 + 0.5j) \cdot \text{pu}$$

Zone I Calculations

$$V_{b1} := V_{b2} \cdot \left(\frac{14\text{kV}}{132\text{kV}} \right) \quad V_{b1} = 10.61 \cdot \text{kV}$$

- Change of base calculation on the generator reactance:

$$V_{\text{gen_rated}} := 13.8\text{kV} \quad S_{\text{gen_rated}} := 15\text{MVA}$$

$$X_{\text{gen_pu_new}} := 0.15\text{pu} \cdot \left(\frac{V_{\text{gen_rated}}}{V_{b1}} \right)^2 \cdot \left(\frac{S_b}{S_{\text{gen_rated}}} \right)$$

$$X_{\text{gen_pu_new}} = 0.1693 \cdot \text{pu}$$

- Transformer T1 change of base:

$$V_{\text{low_T1_rated}} := 14\text{kV} \quad S_{\text{T1_rated}} := 20\text{MVA}$$

$$X_{\text{T1_pu_new}} := 0.10\text{pu} \left(\frac{V_{\text{low_T1_rated}}}{V_{\text{b1}}} \right)^2 \cdot \left(\frac{S_{\text{b}}}{S_{\text{T1_rated}}} \right)$$

$$X_{\text{T1_pu_new}} = 0.0871 \cdot \text{pu}$$

Zone III Calculations:

$$V_{\text{b3}} := V_{\text{b2}} \cdot \left(\frac{13\text{kV}}{115\text{kV}} \right) \quad V_{\text{b3}} = 11.3 \cdot \text{kV}$$

- Transformer T2 change of base:

$$V_{\text{low_T2_rated}} := 13\text{kV} \quad S_{\text{T2_rated}} := 15\text{MVA}$$

$$X_{\text{T2_pu_new}} := 0.10\text{pu} \left(\frac{V_{\text{low_T2_rated}}}{V_{\text{b3}}} \right)^2 \cdot \left(\frac{S_{\text{b}}}{S_{\text{T2_rated}}} \right)$$


$$X_{\text{T2_pu_new}} = 0.09 \cdot \text{pu}$$

- Motor impedance change of base:


$$V_{\text{motor_rated}} := 12\text{kV} \quad S_{\text{motor_rated}} := 10\text{MVA}$$

$$X_{\text{motor_pu_new}} := 0.07\text{pu} \left(\frac{V_{\text{motor_rated}}}{V_{\text{b3}}} \right)^2 \cdot \left(\frac{S_{\text{b}}}{S_{\text{motor_rated}}} \right)$$
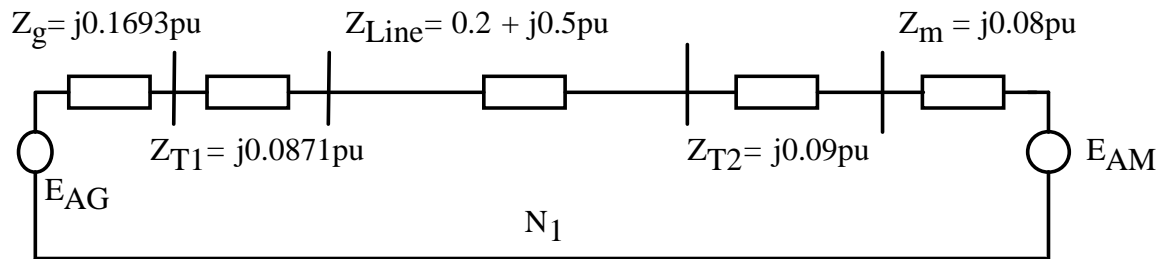
$$X_{\text{motor_pu_new}} = 0.08 \cdot \text{pu}$$



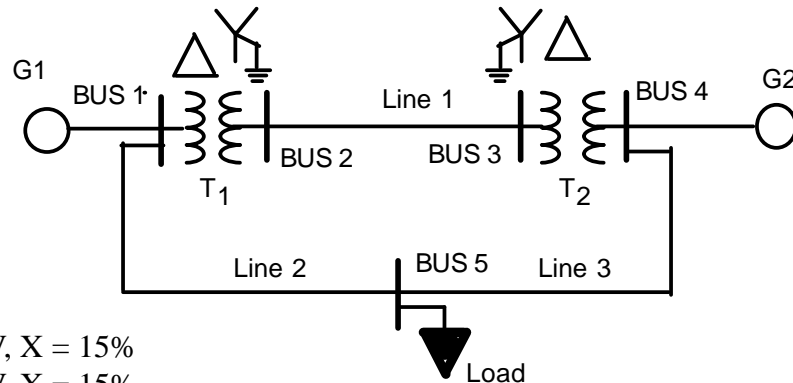2. Sketch a per phase, per unit equivalent circuit for the system below. Use a system MVA base of 100MVA, and a voltage base of 220 kV on the high voltage transmission line section.



Using the following equipment nameplate data:

- G1: 50 MVA, 13.8 kV, $X = 15\%$
- G2: 25 MVA, 14.4 kV, $X = 15\%$
- T1: 60 MVA, 13.8 : 230 kV, $X = 10\%$
- T2: 30 MVA, 230 : 13.8 kV, $X = 10\%$
- Line 1: $10 + j100 \text{ Ohm}$
- Line 2: $0.05 + j0.5 \text{ Ohm}$
- Line 3: $0.05 + j0.5 \text{ Ohm}$
- Load: 25 MVA, 0.9pf lagging

- System MVA Base

$$S_B := 100\text{MVA}$$

- Voltage base for the high voltage part of the system (Line 1):

$$V_{B2} := 220\text{kV}$$

- Voltage base for the rest of the system

$$V_{B1} := V_{B2} \cdot \left(\frac{13.8\text{kV}}{230\text{kV}} \right) \quad V_{B1} = 13.2\text{kV}$$

- Impedance Bases

$$Z_{B1} := \frac{V_{B1}^2}{S_B} \quad Z_{B1} = 1.74 \Omega$$

$$Z_{B2} := \frac{V_{B2}^2}{S_B} \quad Z_{B2} = 484 \Omega$$

- Change of Base Calculations:

$$\text{Generator G1} \quad X_{G1} := 0.15\text{pu} \cdot \left(\frac{13.8\text{kV}}{V_{B1}} \right)^2 \cdot \left(\frac{S_B}{50\text{MVA}} \right) \quad \boxed{X_{G1} = 0.33\text{pu}}$$

$$\text{Generator G2} \quad X_{G2} := 0.15\text{pu} \cdot \left(\frac{14.4\text{kV}}{V_{B1}} \right)^2 \cdot \left(\frac{S_B}{25\text{MVA}} \right) \quad \boxed{X_{G2} = 0.71 \cdot \text{pu}}$$

$$\text{Transformer T1:} \quad X_{t1} := 0.10\text{pu} \cdot \left(\frac{13.8\text{kV}}{V_{B1}} \right)^2 \cdot \left(\frac{S_B}{60\text{MVA}} \right) \quad \boxed{X_{t1} = 0.18 \cdot \text{pu}}$$

$$\text{Transformer T2:} \quad X_{t2} := 0.10\text{pu} \cdot \left(\frac{13.8\text{kV}}{V_{B1}} \right)^2 \cdot \left(\frac{S_B}{30\text{MVA}} \right) \quad \boxed{X_{t2} = 0.36 \cdot \text{pu}}$$

- Convert Line Impedances to Per Unit

$$Z_{L1} := 10\text{ohm} + j \cdot 100\text{ohm}$$

$$Z_{L1\text{pu}} := \frac{Z_{L1}}{Z_{B2}} \quad \boxed{Z_{L1\text{pu}} = (0.02 + 0.21j) \cdot \text{pu}}$$

$$Z_{L2} := 0.05\text{ohm} + j \cdot 0.5\text{ohm}$$

$$Z_{L2\text{pu}} := \frac{Z_{L2}}{Z_{B1}} \quad \boxed{Z_{L2\text{pu}} = (0.03 + 0.29j) \cdot \text{pu}}$$

$$Z_{L3} := 0.05\text{ohm} + j \cdot 0.5\text{ohm}$$

$$Z_{L3\text{pu}} := \frac{Z_{L3}}{Z_{B1}} \quad \boxed{Z_{L3\text{pu}} = (0.03 + 0.29j) \cdot \text{pu}}$$

- Equivalent Load Impedance (can consider it parallel or series connected RL circuit)

$$\text{MagSload} := 25\text{MVA} \quad \text{pload} := 0.9 \quad \text{lagging}$$

$$P_{\text{load}} := \text{MagSload} \cdot \text{pload} \quad P_{\text{load}} = 22.5 \cdot \text{MW}$$

$$\theta_{\text{load}} := \arccos(\text{pload}) \quad \theta_{\text{load}} = 25.84 \cdot \text{deg}$$

$$Q_{\text{load}} := \text{MagSload} \cdot \sin(\theta_{\text{load}}) \quad Q_{\text{load}} = 10.9 \cdot \text{MVAR}$$

$$S_{\text{load}} := P_{\text{load}} + j \cdot Q_{\text{load}} \quad S_{\text{load}} = (22.5 + 10.9j) \cdot \text{MVA}$$

$$S_{\text{load_pu}} := \frac{S_{\text{load}}}{S_B} \quad |S_{\text{load_pu}}| = 0.25 \cdot \text{pu}$$

Parallel Load

$$R_{\text{load}} := \frac{V_{B1}^2}{P_{\text{load}}} \quad R_{\text{load}} = 7.74 \Omega$$

$$R_{\text{load_pu}} := \frac{R_{\text{load}}}{Z_{B1}} \quad R_{\text{load_pu}} = 4.44 \cdot \text{pu}$$

$$X_{\text{load}} := \frac{V_{B1}^2}{Q_{\text{load}}} \quad X_{\text{load}} = 15.99 \Omega$$

$$X_{\text{load_pu}} := \frac{X_{\text{load}}}{Z_{B1}} \quad X_{\text{load_pu}} = 9.18 \cdot \text{pu}$$

- As a check: $V_{\text{rated}} := 1.0 \text{pu}$

$$S_{\text{check}} := \frac{V_{\text{rated}}^2}{R_{\text{load_pu}}} + \frac{jV_{\text{rated}}^2}{X_{\text{load_pu}}} \quad S_{\text{check}} = 0.23 + 0.11i$$

$$|S_{\text{check}}| = 0.25 \cdot \text{pu} \quad \text{Correct magnitude}$$

$$\frac{\text{Re}(S_{\text{check}})}{|S_{\text{check}}|} = 0.9 \quad \text{Correct power factor, and since imaginary part is positive, it is lagging}$$

- Series Connected Load

$$\text{Recall: } S = V \cdot \bar{I} \quad (\text{Complex conjugate of } I)$$

$$S = V \cdot \overline{\left(\frac{V}{Z}\right)} = \frac{(|V|)^2}{\bar{Z}} \quad \text{So: } Z := \overline{\left[\frac{(|V|)^2}{S}\right]} \quad \text{Take complex conjugate of both sides...}$$

$$Z_{\text{load_series}} := \overline{\left[\frac{(V_{\text{rated}})(V_{B1})^2}{S_{\text{load}}}\right]} \quad Z_{\text{load_series}} = (6.27 + 3.04i) \Omega$$

$$Z_{\text{load_series_pu}} := \frac{Z_{\text{load_series}}}{Z_{B1}} \quad Z_{\text{load_series_pu}} = (3.6 + 1.74i) \cdot \text{pu}$$

- Check result:


$$S_{\text{check_ser}} := \frac{V_{\text{rated}}^2}{Z_{\text{load_series_pu}}}$$

$$S_{\text{check_ser}} = 0.23 + 0.11i$$

$$|S_{\text{check_ser}}| = 0.25 \cdot \text{pu} \quad \arg(S_{\text{check_ser}}) = 25.84 \cdot \text{deg} \quad \text{positive angle, lagging pf}$$


$$\frac{\text{Re}(S_{\text{check_ser}})}{|S_{\text{check_ser}}|} = 0.9 \quad \text{correct power factor.}$$

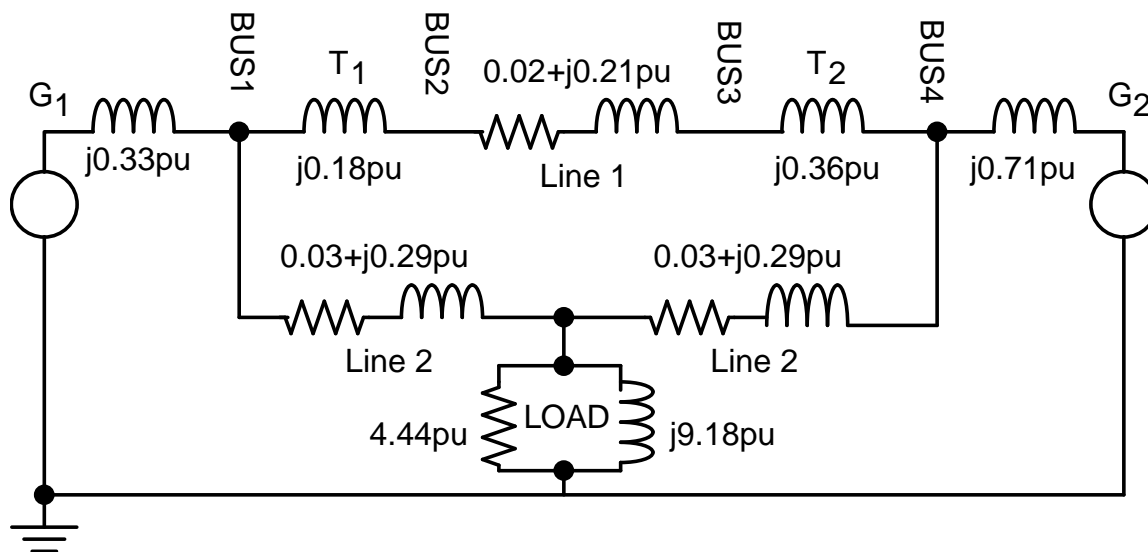- Per Phase/Per Unit Equivalent Circuit (using parallel R-L load):



3. A three-phase generator feeds three large synchronous motors over a 16km, 115kV transmission line, through a 115kV:13.8kV transformer bank, as shown below.

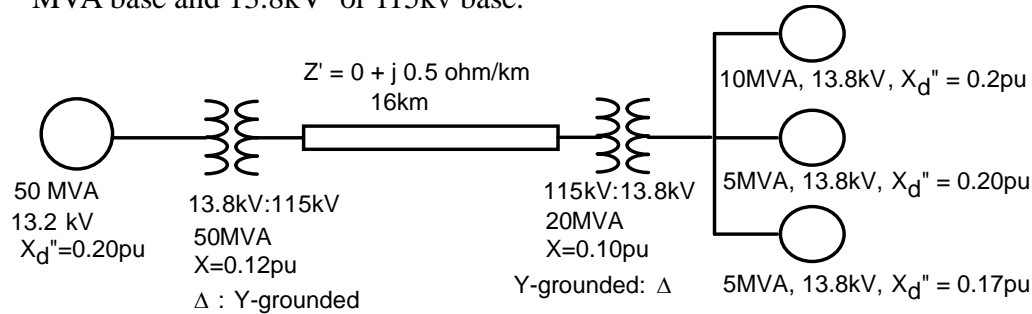(a) Draw a per unit, per phase equivalent circuit with all reactances indicated in per unit on a 100 MVA base and 13.8kV or 115kv base.



(a) Draw a per unit, per phase equivalent circuit with all reactances indicated in per unit on a 100 MVA base and 13.8kV or 115kv base.

$$S_B := 100\text{MVA}$$

$$V_{B1} := 13.8\text{kV}$$

$$V_{B2} := V_{B1} \cdot \left(\frac{115}{13.8} \right) \quad V_{B2} = 115 \cdot \text{kV}$$

$$V_{B3} := V_{B2} \cdot \left(\frac{13.8}{115} \right) \quad V_{B3} = 13.8 \cdot \text{kV}$$

$$\text{Generator} \quad X_{dpp} := 0.20\text{pu} \cdot \left(\frac{13.2\text{kV}}{V_{B1}} \right)^2 \cdot \left(\frac{S_B}{50\text{MVA}} \right) \quad X_{dpp} = 0.37 \cdot \text{pu}$$

$$\text{Transformer 1:} \quad X_{t1} := 0.12\text{pu} \cdot \left(\frac{13.8\text{kV}}{V_{B1}} \right)^2 \cdot \left(\frac{S_B}{50\text{MVA}} \right) \quad X_{t1} = 0.24 \cdot \text{pu}$$

$$Z_{bII} := \frac{(V_{B2})^2}{S_B} \quad Z_{bII} = 132.25 \Omega$$

$$\text{Per unit line impedance} \quad X_{\text{line_pu}} := \frac{\left(0.5 \frac{\text{ohm}}{\text{km}} \right) \cdot 16\text{km}}{Z_{bII}} \quad X_{\text{line_pu}} = 0.06 \cdot \text{pu}$$


$$\text{Transformer 2:} \quad X_{t2} := 0.10 \cdot \left(\frac{115\text{kV}}{V_{B2}} \right)^2 \cdot \left(\frac{S_B}{20\text{MVA}} \right) \quad X_{t2} = 0.5$$

$$\text{Motor 1:} \quad X_{m1} := 0.2 \cdot \left(\frac{13.8\text{kV}}{V_{B3}} \right)^2 \cdot \left(\frac{S_B}{10\text{MVA}} \right) \quad X_{m1} = 2 \cdot \text{pu}$$

$$\text{Motor 2:} \quad X_{m2} := 0.2 \cdot \left(\frac{13.8\text{kV}}{V_{B3}} \right)^2 \cdot \left(\frac{S_B}{5\text{MVA}} \right) \quad X_{m2} = 4 \cdot \text{pu}$$

$$\text{Motor 3:} \quad X_{m3} := 0.17 \cdot \left(\frac{13.8\text{kV}}{V_{B3}} \right)^2 \cdot \left(\frac{S_B}{5\text{MVA}} \right) \quad X_{m3} = 3.4 \cdot \text{pu}$$

Per unit equivalent circuit diagram:

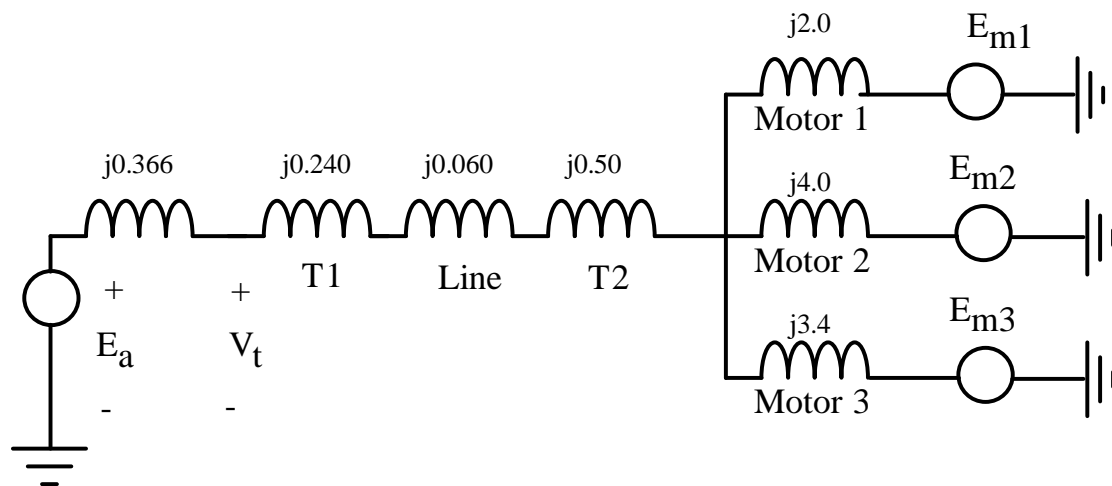

(b) The generator is controlled to maintain the voltage at the motor bus at 1.0pu at an angle of 0 degrees. The three motors are operating at full rating and 90% PF lagging. Determine the voltage required at the generator terminals assuming that there is no voltage regulating taps or similar equipment in this system.

The motors have a total rating of 20 MVA

$$S_{\text{load_mag}} := 20\text{MVA} \quad \text{pload} := 0.90 \quad \phi_{\text{load}} := \text{acos}(0.90) \quad \phi_{\text{load}} = 25.84 \cdot \text{deg}$$

$$S_{\text{load}} := S_{\text{load_mag}} \cdot e^{j \cdot \phi_{\text{load}}}$$

$$S_{\text{load_pu}} := \frac{S_{\text{load}}}{100\text{MVA}} \quad S_{\text{load_pu}} = 0.18 + 0.09i \quad |S_{\text{load_pu}}| = 0.2$$

$$V_{\text{load_pu}} := 1.0e^{j \cdot 0}$$

$$I_{\text{load_pu}} := \frac{\overline{S_{\text{load_pu}}}}{V_{\text{load_pu}}} \quad I_{\text{load_pu}} = 0.18 - 0.09i$$

$$|I_{\text{load_pu}}| = 0.2 \quad \arg(I_{\text{load_pu}}) = -25.84 \cdot \text{deg}$$

Generator Terminal Voltage:

$$V_t := V_{\text{load_pu}} + I_{\text{load_pu}} \cdot (j \cdot X_{t1} + j \cdot X_{\text{line_pu}} + j \cdot X_{t2})$$

$$|V_t| = 1.08 \quad \arg(V_t) = 7.67 \cdot \text{deg} \quad |V_t| \cdot V_{B1} = 14.9 \cdot \text{kV} \quad \text{line to line}$$

(c) Calculate the voltage required behind the subtransient reactance for the generator and each of the motors

Generator Internal Voltage:

$$E_a := V_t + I_{\text{load_pu}} \cdot (j \cdot X_{dpp})$$

$$|E_a| = 1.12 \quad \arg(E_a) = 10.79 \cdot \text{deg} \quad |E_a| \cdot \frac{V_{B3}}{\sqrt{3}} = 8.94 \cdot \text{kV} \quad \text{line to neutral}$$

Motor 1:

$$I_{\text{motor1}} := I_{\text{load_pu}} \cdot \left(\frac{10 \text{MVA}}{|S_{\text{load}}|} \right) \quad I_{\text{motor1}} = (0.09 - 0.04i) \cdot \text{pu}$$

$$|I_{\text{motor1}}| = 0.1 \cdot \text{pu} \quad \arg(I_{\text{motor1}}) = -25.84 \cdot \text{deg}$$

$$E_{a1} := V_{\text{load_pu}} - I_{\text{motor1}} \cdot (j \cdot X_{m1})$$

$$|E_{a1}| = 0.93 \quad \arg(E_{a1}) = -11.16 \cdot \text{deg} \quad |E_{a1}| \cdot \frac{V_{B3}}{\sqrt{3}} = 7.41 \cdot \text{kV} \quad \text{line to neutral}$$

Motor 2:

$$I_{\text{motor2}} := I_{\text{load_pu}} \cdot \left(\frac{5 \text{MVA}}{|S_{\text{load}}|} \right) \quad I_{\text{motor2}} = (0.05 - 0.02i) \cdot \text{pu}$$

$$|I_{\text{motor2}}| = 0.05 \cdot \text{pu} \quad \arg(I_{\text{motor2}}) = -25.84 \cdot \text{deg}$$

$$E_{am2} := V_{load_pu} - I_{motor2} \cdot (j \cdot X_{m2})$$

$$|E_{am2}| = 0.93$$

$$\arg(E_{am2}) = -11.16 \cdot \text{deg}$$

$$|E_{am2}| \cdot \frac{V_{B3}}{\sqrt{3}} = 7.41 \cdot \text{kV}$$

line to neutral

Motor 3:

$$I_{motor3} := I_{load_pu} \cdot \left(\frac{5 \text{MVA}}{|S_{load}|} \right)$$

$$I_{motor3} = (0.05 - 0.02i) \cdot \text{pu}$$

$$|I_{motor3}| = 0.05 \cdot \text{pu}$$

$$\arg(I_{motor3}) = -25.84 \cdot \text{deg}$$

$$E_{am3} := V_{load_pu} - I_{motor3} \cdot (j \cdot X_{m3})$$

$$|E_{am3}| = 0.94$$

$$\arg(E_{am3}) = -9.38 \cdot \text{deg}$$

$$|E_{am3}| \cdot \frac{V_{B3}}{\sqrt{3}} = 7.48 \cdot \text{kV}$$

line to neutral

(d) Calculate the line current in Amperes

Base current on the transmission line segment:

$$I_{B2} := \frac{S_B}{\sqrt{3} \cdot V_{B2}}$$

$$I_{B2} = 502.04 \text{ A}$$

$$I_{line} := I_{load_pu} \cdot I_{B2}$$

$$|I_{line}| = 100.41 \text{ A}$$

4. Draw the per unit, Thevenin equivalent circuit for the system below looking out from the load bus if:

- The generator internal voltages are equal in magnitude and angle (label both as E_1 and present your results as a function of E_1)
- The generator internal voltages are not equal (label one as E_1 and the other E_2 in your solution, and present your results as a function of E_1 and E_2)

Impedance values (all on consistent bases, no change of base needed):


G1: $X = 0.1$ pu

G2: $X = 0.1$ pu

Line 1: $X = 0.1$ pu

Line 2: $X = 0.1$ pu

Load: $Z = j 0.1$ pu

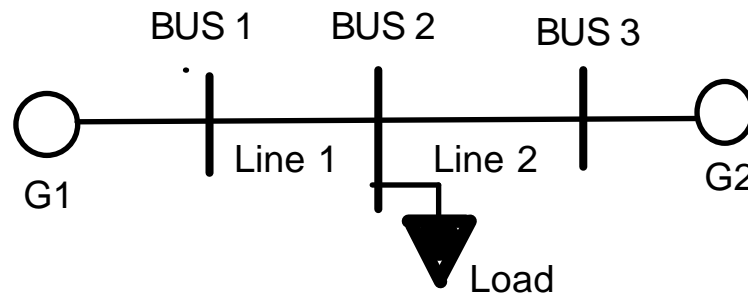

Answer part (b) first to get a general approach, and then apply that result to part (a)

- The generator internal voltages are not equal (label one as E_1 and the other E_2 in your solution, and present your results as a function of E_1 and E_2)

$$Z_{g1} := j \cdot 0.1 \text{ pu}$$

$$Z_{\text{Line1}} := j \cdot 0.1 \text{ pu}$$

$$Z_{\text{load}} := j \cdot 0.1 \text{ pu}$$

$$Z_{g2} := j \cdot 0.1 \text{ pu}$$

$$Z_{\text{Line2}} := j \cdot 0.1 \text{ pu}$$

- Impedance to the left of the load:

$$Z_{\text{left}} := Z_{g1} + Z_{\text{Line1}}$$


$$Z_{\text{left}} = 0.2j \cdot \text{pu}$$

- Impedance to the right of the load:


$$Z_{\text{right}} := Z_{g2} + Z_{\text{Line2}}$$

$$Z_{\text{right}} = 0.2j \cdot \text{pu}$$

- Resulting equivalent circuit

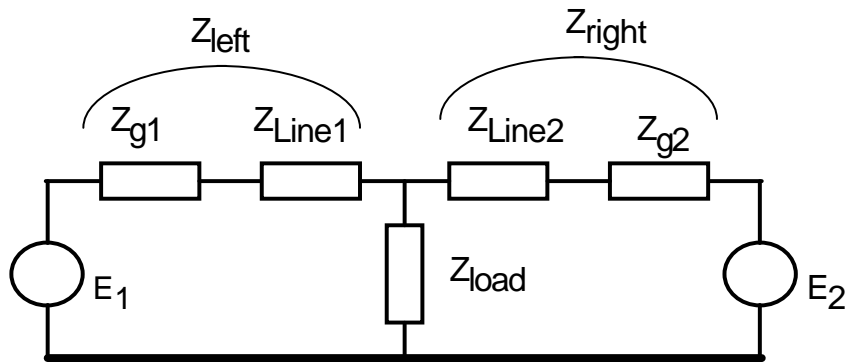

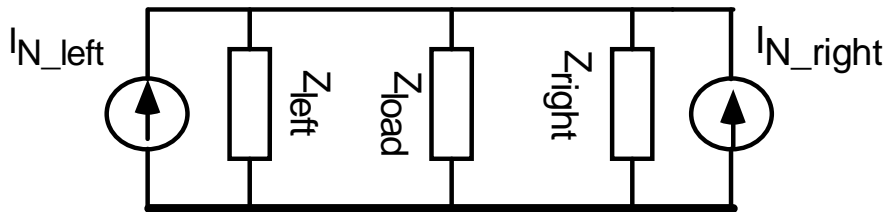
- Now take Norton Equivalent to left and the right, leading to this circuit:



$$I_{N_left} = \frac{E_1}{Z_{left}}$$

$$I_{N_right} = \frac{E_2}{Z_{right}}$$

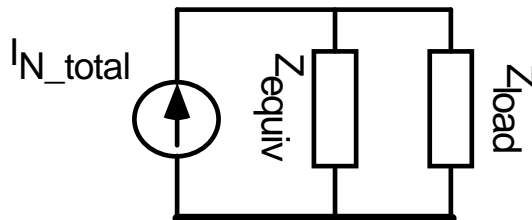- Now combine the two Norton equivalents in parallel



$$I_{N_total} = I_{N_left} + I_{N_right} = \frac{E_1}{Z_{left}} + \frac{E_2}{Z_{right}}$$


- Equivalent impedance

$$Z_{equiv} := \left(\frac{1}{Z_{left}} + \frac{1}{Z_{right}} \right)^{-1}$$

$$Z_{equiv} = 0.1i \cdot pu$$

- Convert Norton Equivalent Back to Thevenin' Equivalent
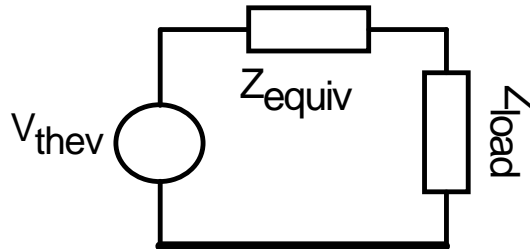
$$V_{\text{th}} = I_{N_total} \cdot Z_{\text{equiv}} = E_1 \cdot \frac{Z_{\text{equiv}}}{Z_{\text{left}}} + E_2 \cdot \frac{Z_{\text{equiv}}}{Z_{\text{right}}}$$



- In this case:

$$V_{\text{th}} = E_1 \cdot \left(\frac{j \cdot 0.1}{j \cdot 0.2} \right) + E_2 \cdot \left(\frac{j \cdot 0.1}{j \cdot 0.2} \right) = 0.5 \cdot E_1 + 0.5 \cdot E_2$$

- (a) The generator internal voltages are equal in magnitude and angle (label both as E_1 and present your results as a function of E_1)

Now we have identical voltages, so:

$$V_{\text{th}} = 0.5 \cdot E_1 + 0.5 \cdot E_1 = E_1 \quad \text{As one would expect.....}$$

Z_{equiv} stays the same, it does not depend on the voltage output of the source

5. Problem 1.4 in the text book

The following table of values has been prepared for various line sections in a small electric system. Find the total p.u. impedance and shunt susceptance of each line on a 10 MVA base, using the nominal line voltage as a base.

$$S_{b4} := 10 \text{ MVA}$$

The table has two different voltage bases:

$$V_{b13_8} := 13.8 \text{ kV} \quad V_{b69} := 69 \text{ kV}$$

Impedance and admittance bases

$$Z_{b13_8} := \frac{V_{b13_8}^2}{S_{b4}} \quad Z_{b13_8} = 19.04 \Omega$$

$$Y_{b13_8} := \frac{1}{Z_{b13_8}} \quad Y_{b13_8} = 0.05 \cdot \text{mho}$$

$$Z_{b69} := \frac{V_{b69}^2}{S_{b4}} \quad Z_{b69} = 476.1 \Omega$$

$$Y_{b69} := \frac{1}{Z_{b69}} \quad Y_{b69} = 0.0021 \frac{1}{\Omega}$$

Line 1:

$$\text{Length1} := 5\text{mi} \quad R_1 := 0.278 \frac{\text{ohm}}{\text{mi}} \quad X_1 := 0.690 \frac{\text{ohm}}{\text{mi}} \quad X_{c1} := 0.16\text{M}\Omega \cdot \text{mi}$$

$$Z_{\text{total1}} := (R_1 + j \cdot X_1) \cdot \text{Length1} \quad Z_{\text{total1}} = (1.39 + 3.45i) \Omega$$

$$B_{c1} := \frac{\text{Length1}}{X_{c1}} \quad B_{c1} = 3.13 \times 10^{-5} \cdot \text{mho}$$

Per Unit results:

$$Z_{1_pu} := \frac{Z_{\text{total1}}}{Z_{b13_8}} \quad Z_{1_pu} = (0.07 + 0.18i) \cdot \text{pu}$$

$$B_{c1_pu} := \frac{B_{c1}}{Y_{b13_8}} \quad B_{c1_pu} = 0.000595 \cdot \text{pu} \quad \text{Admittance}$$

It is ok to express Bc as a capacitive reactance instead:

$$X_{c1_pu} := \frac{1}{B_{c1_pu}} \quad X_{c1_pu} = 1680.32 \cdot \text{pu}$$

Line 2:

$$\text{Length2} := 2\text{mi} \quad R_2 := 1.374 \frac{\text{ohm}}{\text{mi}} \quad X_2 := 0.816 \frac{\text{ohm}}{\text{mi}} \quad X_{c2} := 0.193\text{M}\Omega \cdot \text{mi}$$

$$Z_{\text{total2}} := (R_2 + j \cdot X_2) \cdot \text{Length2} \quad Z_{\text{total2}} = (2.75 + 1.63i) \Omega$$

$$B_{c2} := \frac{\text{Length2}}{X_{c2}} \quad B_{c2} = 1.04 \times 10^{-5} \cdot \text{mho}$$

Per Unit results:

$$Z_{2_pu} := \frac{Z_{total2}}{Z_{b13_8}}$$

$$Z_{2_pu} = 0.14 + 0.09i$$

$$B_{c2_pu} := \frac{B_{c2}}{Y_{b13_8}}$$

$$B_{c2_pu} = 0.000197$$

It is ok to express Bc as a capacitive reactance instead:

$$X_{c2_pu} := \frac{1}{B_{c2_pu}}$$

$$X_{c2_pu} = 5067.21 \cdot pu$$

Line 3:

$$Length3 := 3.9mi \quad R_3 := 0.445 \frac{ohm}{mi}$$

$$X_3 := 0.711 \frac{ohm}{mi}$$

$$X_{c3} := 0.157M\Omega \cdot mi$$

$$Z_{total3} := (R_3 + j \cdot X_3) \cdot Length3$$

$$Z_{total3} = (1.74 + 2.77i) \Omega$$

$$B_{c3} := \frac{Length3}{X_{c3}}$$

$$B_{c3} = 2.48 \times 10^{-5} \cdot mho$$

Per Unit results:

$$Z_{3_pu} := \frac{Z_{total3}}{Z_{b13_8}}$$

$$Z_{3_pu} = 0.09 + 0.15i$$

$$B_{c3_pu} := \frac{B_{c3}}{Y_{b13_8}}$$

$$B_{c3_pu} = 0.000473$$

It is ok to express Bc as a capacitive reactance instead:

$$X_{c3_pu} := \frac{1}{B_{c3_pu}}$$

$$X_{c3_pu} = 2113.86 \cdot pu$$

Line 4:

$$Length4 := 6.2mi \quad R_4 := 0.278 \frac{ohm}{mi}$$

$$X_4 := 0.730 \frac{ohm}{mi}$$

$$X_{c4} := 0.172M\Omega \cdot mi$$

$$Z_{total4} := (R_4 + j \cdot X_4) \cdot Length4$$

$$Z_{total4} = (1.72 + 4.53i) \Omega$$

$$B_{c4} := \frac{Length4}{X_{c4}}$$

$$B_{c4} = 3.6 \times 10^{-5} \cdot mho$$

Per Unit results:

$$Z_{4_pu} := \frac{Z_{total4}}{Z_{b13_8}} \quad \boxed{Z_{4_pu} = 0.09 + 0.24i}$$

$$B_{c4_pu} := \frac{B_{c4}}{Y_{b13_8}} \quad \boxed{B_{c4_pu} = 0.000686}$$

It is ok to express Bc as a capacitive reactance instead:

$$X_{c4_pu} := \frac{1}{B_{c4_pu}} \quad \boxed{X_{c4_pu} = 1456.73 \cdot pu}$$

Line 5:

$$\text{Length5} := 7.3 \text{mi} \quad R_5 := 0.088 \frac{\text{ohm}}{\text{mi}} \quad X_5 := 0.330 \frac{\text{ohm}}{\text{mi}} \quad X_{c5} := 0.142 \text{M}\Omega \cdot \text{mi}$$

$$Z_{total5} := (R_5 + j \cdot X_5) \cdot \text{Length5} \quad Z_{total5} = (0.64 + 2.41i) \Omega$$

$$B_{c5} := \frac{\text{Length5}}{X_{c5}} \quad B_{c5} = 5.14 \times 10^{-5} \cdot \text{mho}$$

Per Unit results:

$$Z_{5_pu} := \frac{Z_{total5}}{Z_{b13_8}} \quad \boxed{Z_{5_pu} = 0.03 + 0.13i}$$

$$B_{c5_pu} := \frac{B_{c5}}{Y_{b13_8}} \quad \boxed{B_{c5_pu} = 0.000979}$$

It is ok to express Bc as a capacitive reactance instead:

$$X_{c5_pu} := \frac{1}{B_{c5_pu}} \quad \boxed{X_{c5_pu} = 1021.43 \cdot pu}$$

Line 6:

$$\text{Length6} := 10.0 \text{mi} \quad R_6 := 0.445 \frac{\text{ohm}}{\text{mi}} \quad X_6 := 0.711 \frac{\text{ohm}}{\text{mi}} \quad X_{c6} := 0.157 \text{M}\Omega \cdot \text{mi}$$

$$Z_{total6} := (R_6 + j \cdot X_6) \cdot \text{Length6} \quad Z_{total6} = (4.45 + 7.11i) \Omega$$

$$B_{c6} := \frac{\text{Length6}}{X_{c6}} \quad B_{c6} = 6.37 \times 10^{-5} \cdot \text{mho}$$

Per Unit results:

$$Z_{6_pu} := \frac{Z_{total6}}{Z_{b69}} \quad \boxed{Z_{6_pu} = 0.01 + 0.01i}$$

$$B_{c6_pu} := \frac{B_{c6}}{Y_{b69}}$$

$$B_{c6_pu} = 0.030325$$

It is ok to express Bc as a capacitive reactance instead:

$$X_{c6_pu} := \frac{1}{B_{c6_pu}}$$

$$X_{c6_pu} = 32.98 \cdot pu$$

Line 7:

$$\text{Length7} := 25 \text{mi} \quad R_7 := 0.278 \frac{\text{ohm}}{\text{mi}} \quad X_7 := 0.730 \frac{\text{ohm}}{\text{mi}} \quad X_{c7} := 0.172 \text{M}\Omega \cdot \text{mi}$$

$$Z_{\text{total7}} := (R_7 + j \cdot X_7) \cdot \text{Length7} \quad Z_{\text{total7}} = (6.95 + 18.25i) \Omega$$

$$B_{c7} := \frac{\text{Length7}}{X_{c7}} \quad B_{c7} = 1.45 \times 10^{-4} \cdot \text{mho}$$

Per Unit results:

$$Z_{7_pu} := \frac{Z_{\text{total7}}}{Z_{b69}} \quad Z_{7_pu} = 0.01 + 0.04i$$

$$B_{c7_pu} := \frac{B_{c7}}{Y_{b69}} \quad B_{c7_pu} = 0.069201$$

It is ok to express Bc as a capacitive reactance instead:

$$X_{c7_pu} := \frac{1}{B_{c7_pu}} \quad X_{c7_pu} = 14.45 \cdot pu$$

Summary =

Line	Rpu	Xpu	Bcpu	Xcpu
1	0.073	0.1812	0.000595	1680.32
2	0.1443	0.0857	0.000197	5067.21
3	0.0911	0.1456	0.000473	2113.86
4	0.0905	0.2377	0.000686	1456.73
5	0.0337	0.1265	0.000979	1021.43
6	0.0094	0.0149	0.030325	32.98
7	0.0146	0.0383	0.06920	14.45