

# Joe Stanley

## ECE 524 - HWK2

### Problem 1

(Analytical Operations)

Reduce the circuit to a simple RLC system.

```
In [1]: 1 # Import Necessary Libraries  
2 import numpy as np  
3 import matplotlib.pyplot as plt  
4 import eepower as eep  
5 from eepower import u, m, k, M
```

In [2]:

```
1  # Define Givens
2
3  # Per-Unit Bases
4  Sbase = 30*M
5  Vb1 = 138*k
6  Vb2 = 13.8*k
7  Vb3 = 4.16*k
8
9  # Source
10 S_src = 3500*M #VA
11 XR_src = 15 #unitless
12 V_src = 138*k #V
13
14 # Transformer(s)
15 S_xfm = 30*M #VA
16 Z_xfm = 7.5/100 #pu
17 XR_xfm = 18.6 #unitless
18 V_busA = 13.8*k #V
19
20 # Generator
21 S_gen = 35.3*M #VA
22 Xdv_gen = 10/100 #pu
23 XR_gen = 48 #unitless
24
25 # Motor Load (each motor)
26 P_mot = 30000 #hp
27 Xd_mot = 16.7/100 #pu
28 XR_mot = 10 #unitless
29 pf_mot = 0.8 #lagging
30
31 # Cap Bank
32 S_cap = 10*M #VAr
33
34 # Load Transformer
35 S_xfm_ld = 5*M #VA
36 Z_xfm_ld = 5.5/100 #pu
37 XR_xfm_ld = 7 #unitless
38 V_ld = 4.16*k #V
```

In [3]:

```
1  # Define Formulas, Algorithms, and Functions
2
3  # Define Impedance From Power and X/R
4  def zsource(S,V,XoverR,Sbase=None,Vbase=None):
5      """
6          zsource Function
7
8          Used to calculate the source impedance given the apparent power
9          magnitude and the X/R ratio.
10
11         Parameters
12         -----
13         S:          float
14                     The (rated) apparent power magnitude of the source.
15                     This may also be referred to as the "Short-Circuit MVA"
16         V:          float
17                     The (rated) voltage of the source terminals.
18         XoverR:     float
19                     The X/R ratio rated for the source.
20         Sbase:      float, optional
21                     The per-unit base for the apparent power. If set to
22                     None, will automatically force Sbase to equal S.
23                     If set to True will treat S as the per-unit value.
24         Vbase:      float, optional
25                     The per-unit base for the terminal voltage. If set to
26                     None, will automaticlaly force Vbase to equal V. If
27                     set to True, will treat V as the per-unit value.
28
29         Returns
30         -----
31         Zsource_pu: complex
32                     The per-unit evaluation of the source impedance.
33         """
34         # Force Sbase and Vbase if needed
35         if Vbase == None:
36             Vbase = V
37         if Sbase == None:
38             Sbase = S
39         # Prevent scaling if per-unit already applied
40         if Vbase == True:
41             Vbase = 1
42         if Sbase == True:
43             Sbase = 1
44         # Set to per-unit
45         Spu = S/Sbase
46         Vpu = V/Vbase
47         # Evaluate Zsource Magnitude
48         Zsource_pu = Vpu**2/Spu
49         # Evaluate the angle
50         nu = np.degrees(np.arctan(XoverR))
51         Zsource_pu = eep.phasor(Zsource_pu, nu)
52         return(Zsource_pu)
53
54     # Define Impedance Decomposer
55     def zdecompose(Zmag,XoverR):
56         """
```

```

57     zdecompose Function
58
59     A function to decompose the impedance magnitude into its
60     corresponding resistance and reactance using the X/R ratio.
61
62     It is possible to "neglect" R, or make it a very small number;
63     this is done by setting the X/R ratio to a very large number
64     (X being much larger than R).
65
66     Parameters
67     -----
68     Zmag:      float
69                The magnitude of the impedance.
70     XoverR:    float
71                The X/R ratio.
72
73     Returns
74     -----
75     R:         float
76                The resistance (in ohms)
77     X:         float
78                The reactance (in ohms)
79     """
80     # Evaluate Resistance
81     R = Zmag/np.sqrt(XoverR**2+1)
82     # Evaluate Reactance
83     X = R * XoverR
84     # Return
85     return(R,X)
86
87 # Define HP to Watts Calculation
88 def watts(hp):
89     """
90     watts Formula
91
92     Calculates the power (in watts) given the
93     horsepower.
94
95     Parameters
96     -----
97     hp:         float
98                The horsepower to compute.
99
100    Returns
101    watts:      float
102                The power in watts.
103    """
104    return(hp * 745.699872)
105
106 # Define Apparent Power to Farad Conversion
107 def farads(VAR,V,freq=60):
108     """
109     farads Formula
110
111     Function to calculate the required capacitance
112     in Farads to provide the desired power rating
113     (VARs).

```

```

114
115     Parameters
116     -----
117     VAR:          float
118                  The rated power to meet.
119     V:           float
120                  The voltage across the capacitor;
121                  not described as VLL or VLN, merely
122                  the capacitor voltage.
123     freq:        float, optional
124                  The System frequency
125
126     Returns
127     -----
128     C:           float
129                  The evaluated capacitance (in Farads).
130     """
131     return(VAR / (2*np.pi*freq*V**2))
132
133 # Define Power Reactance Calculator
134 def powerimpedance(S,V,parallel=False):
135     """
136     powerreactance Function
137
138     Function to determine the ohmic resistance/reactance
139     (impedance) represented by the apparent power (S).
140
141     Formula:      Z = V^2 / S          (series components)
142                  Z = V^2 / (3*S)      (parallel components)
143
144     Parameters
145     -----
146     S:           complex
147                  The apparent power of the passive element,
148                  may be purely resistive or purely reactive.
149     V:           float
150                  The operating voltage of the passive element.
151     parallel:    bool, optional
152                  Control point to specify whether the ohmic
153                  impedance should be returned as series components
154                  (False opt.) or parallel components (True opt.).
155
156     Returns
157     -----
158     R:           float
159                  The ohmic resistance required to consume the
160                  specified apparent power (S) at the rated
161                  voltage (V).
162     X:           float
163                  The ohmic reactance required to consume the
164                  specified apparent power (S) at the rated
165                  voltage (V).
166     """
167     # Condition Inputs
168     V = abs(V)
169     # Test for Parallel Component Option and Evaluate
170     if isinstance(S,complex):

```

```

171         # Complex Power (both R and X)
172         if parallel:
173             R = V**2 / (3*S.real)
174             X = V**2 / (3*S.imag)
175         else:
176             R = V**2 / (S.real)
177             X = V**2 / (S.imag)
178         return( R, X )
179     # Not Complex (just R)
180     R = V**2 / S
181     return( R )

```

In [4]:

```

1  # Evaluate Impedance Terms
2
3  # Source
4  Zsrc_pu = zsource(S_src,V_src,XR_src,Sbase,Vb1)
5  print("Source Impedance:",np.around(Zsrc_pu,4),"pu-ohms")
6
7  # Generator
8  Rgen = Xdv_gen/XR_gen
9  Zgen = Rgen + 1j*Xdv_gen
10 Zgen = eep.convert(Zgen,eep.zpu(35.3*M,VLL=13.8*k),eep.zpu(30*M,VLL=13.8*k))
11 print("Generator Impedance:",np.around(Zgen,4),"pu-ohms")
12
13 # Transformer
14 Rxfm,Xxfm = zdecompose(Z_xfm,XR_xfm)
15 Zxfm = Rxfm + 1j*Xxfm
16 print("Transformer Impedance:",np.around(Zxfm,4),"pu-ohms")

```

Source Impedance: (0.0006+0.0086j) pu-ohms  
 Generator Impedance: (0.0018+0.085j) pu-ohms  
 Transformer Impedance: (0.004+0.0749j) pu-ohms

In [5]:

```
1  # Base Impedance
2  Zbase = eep.zpu(Sbase,Vb2)
3
4  # Combine impedances into Zeq
5  Zeq_src = eep.parallelz((Zxfm,Zxfm))+Zsrc_pu
6  print("Source Zeq:",eep.reactance(Zeq_src*Zbase),"( $\Omega$ , H)")
7  print("Generator Z:",eep.reactance(Zgen*Zbase),"( $\Omega$ , H)")
8  #      Parallel(      Parallel( Trans1, Trans2)+Source, Generator )
9  Zeq_pu = eep.parallelz((Zeq_src,Zgen))
10
11 # Return to actual impedance (in ohms)
12 Zeq = Zeq_pu*Zbase
13 print("Thevenin RLC:",Zeq," $\Omega$ ")
14 print("Thevenin RLC:",eep.reactance(Zeq),"( $\Omega$ , H)")
15
16 # Demonstrate LC system, Neglecting R
17 print("Thevenin LC:",Zeq.imag,"ohms")
18 print("Thevenin LC:",eep.reactance(Zeq.imag*1j),"H")
```

Source Zeq: (0.01639932457188166, 0.00077576832486166657) ( $\Omega$ , H)  
Generator Z: (0.011239376770538243, 0.0014313524185196062) ( $\Omega$ , H)  
Thevenin RLC: (0.00828798310752+0.189509201181j)  $\Omega$   
Thevenin RLC: (0.0082879831075199639, 0.00050316927478757543) ( $\Omega$ , H)  
Thevenin LC: 0.189509201181 ohms  
Thevenin LC: 0.000502688768822 H

In [6]:

```
1 # Evaluate Motor Systems
2
3 # Find wattage of motor
4 P_mtr = watts(P_mot)
5 print("Motor Power:",P_mtr/M,"MW")
6 S_mtr = P_mtr/pf_mot
7 Q_mtr = np.sqrt(S_mtr**2 - P_mtr**2)
8 print("Motor Apparent Power:",S_mtr/M,"MVA")
9
10 # Find Impedance
11 R_mtr = powerimpedance(P_mtr,Vb2)
12 XL_mtr = powerimpedance(Q_mtr,Vb2)
13 X_mtr = eep.reactance(XL_mtr)
14 print("Motor Resistance:",R_mtr,"Ω")
15 print("Motor Inductance:",X_mtr*k,"mH")
16
17 # Calculate Current Magnitude
18 Imag_mtr = S_mtr/Vb2
19 print("Motor Current:",Imag_mtr,"A (each)")
20
21 # Evaluate Motor's Internal Voltage
22 # Use basic ohm's Law
23 V_bus = 13.8*k
24 XL = X_mtr * Zbase
25 Vmtr = V_bus - XL*Imag_mtr
26 print("Motor Internal Voltage:",Vmtr,"V")
```

Motor Power: 22.37099616 MW  
Motor Apparent Power: 27.963745199999998 MVA  
Motor Resistance: 8.51280821998049 Ω  
Motor Inductance: 30.1079001734 mH  
Motor Current: 2026.3583478260869 A (each)  
Motor Internal Voltage: 13412.7123615 V

In [7]:

```
1 # Evaluate Non-Linear Load
2
3 # Transformer
4 Rx_fm,Xx_fm = zdecompose(Z_x_fm_ld,XR_x_fm_ld)
5 Zx_fm_ld = Rx_fm + 1j*Xx_fm
6 Zx_fm_ld *= Zbase
7 print("Load Transformer Impedance:",Zx_fm_ld,"Ω")
8 print("Load Transformer Inductance:",eep.reactance(Zx_fm_ld.imag)*k,"mH")
9
10 # Find Current
11 P_nll = 4.5*M
12 I_nll = P_nll / Vb2
13 print("Non-Linear Load Current Mag.:",I_nll,"A")
14
15 # Find Resistance
16 R_nll = Vb2 / I_nll
17 print("Non-Linear Load Resistance:",R_nll,"Ω")
```

Load Transformer Impedance: (0.0493758523167+0.345630966217j) Ω  
Load Transformer Inductance: 0.916814612651 mH  
Non-Linear Load Current Mag.: 326.0869565217391 A  
Non-Linear Load Resistance: 42.32 Ω



In [8]:

```
1 # Determine Cap-Bank Capacitance in Farads
2 Vcap = 13.8*k
3 print("Voltage Across one Capacitor (Line-Neutral):",Vcap,"V")
4 print("Cap-Bank Value:",farads(10*M,Vcap)*1e6,"μF")
```


Voltage Across one Capacitor (Line-Neutral): 13800.0 V

Cap-Bank Value: 139.28703974295962 μF

```

In [9]: 1 # Load Data from File for Part A
2 data = np.genfromtxt("PartA_data.ADF",delimiter='\t',skip_header=2,usecols=(
3 t_arr, LC_V, RLC_V = data
4
5 # Plot Data
6 plt.plot(t_arr,LC_V,label="LC-Voltage")
7 plt.plot(t_arr,RLC_V,label="RLC-Voltage")
8 plt.legend()
9 plt.title("Part 1.1")
10 plt.show()
11
12 # Plot Data
13 plt.subplot(1,2,1)
14 plt.plot(t_arr,LC_V,label="LC-Voltage")
15 plt.plot(t_arr,RLC_V,label="RLC-Voltage")
16 plt.legend()
17 plt.xlim(0,0.05)
18 plt.subplot(1,2,2)
19 plt.plot(t_arr,LC_V,label="LC-Voltage")
20 plt.plot(t_arr,RLC_V,label="RLC-Voltage")
21 plt.legend()
22 plt.xlim(0.45,0.5)
23 plt.show()


```

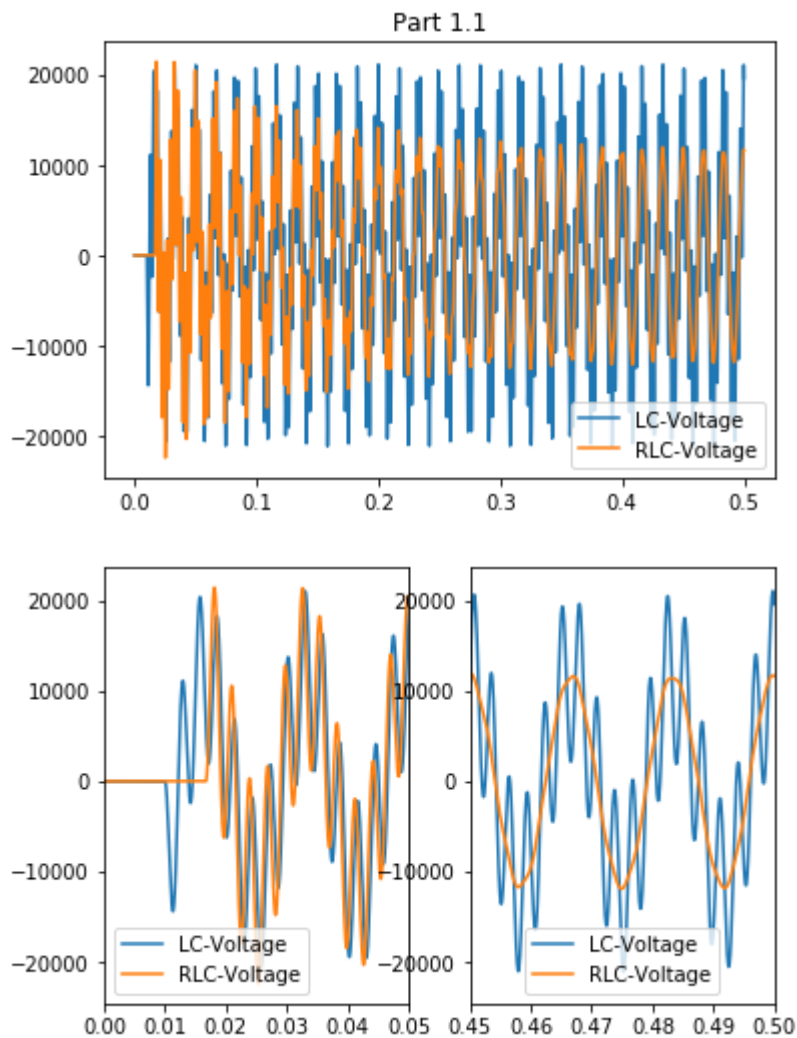
 
### Remarks:

It is interesting to note that the voltage of the RLC simplified circuit shows an exponential decay towards the steady state. This is quite the expected behavior, as it makes sense that the resistor would damp out the voltage.


```
In [10]: 1 # Load Data from File for Part B
2 data = np.genfromtxt("PartB_data.ADF",delimiter='\t',skip_header=2,usecols=(
3 t_arr, VCAP = data
4
5 # Plot Data
6 plt.plot(t_arr,VCAP,label="Capacitor Voltage")
7 plt.legend()
8 plt.title("Part 1.2")
9 plt.show()
```



 
### Remarks

It is worth noting that this graph shows remarkable resemblance to those shown previously.

```
In [11]: 1 # Load Data from File for Part C
2 data = np.genfromtxt("PartC_data.ADF",delimiter='\t',skip_header=2,usecols=(
3 t_arr, VCAP_c= data
4
5 # Plot Data
6 plt.plot(t_arr,VCAP_c,label="Capacitor Voltage")
7 plt.legend()
8 plt.title("Part 1.3 Cap. Voltage")
9 plt.show()
```


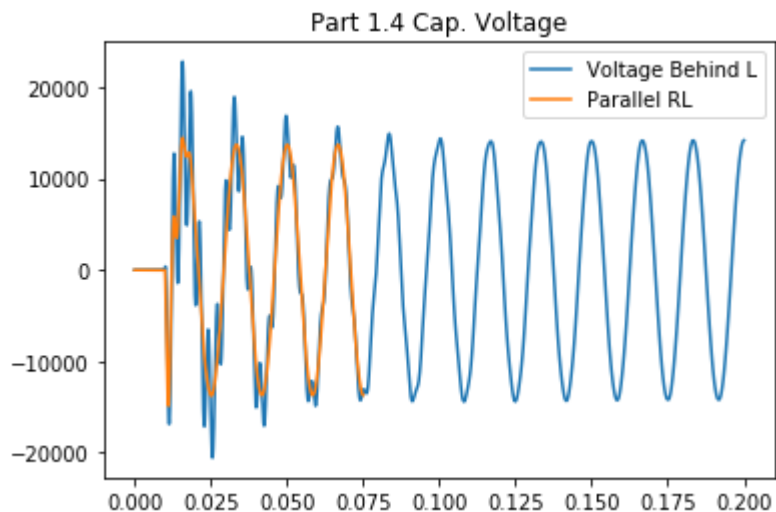
```
In [12]: 1 # Load Data from File for Part D
2 data = np.genfromtxt("PartD_data.ADF",delimiter='\t',skip_header=2,usecols=(
3 t_d, VCAP_d= data
4
5 # Plot Data
6 plt.plot(t_d,VCAP_d,label="Voltage Behind L")
7 plt.plot(t_arr,VCAP_c,label="Parallel RL")
8 plt.legend()
9 plt.title("Part 1.4 Cap. Voltage")
10 plt.show()
```



**Remarks**

Note here that the RL model seems to provide a remarkable amount of damping. It is likely not very accurate as the internal voltage of the motors will drive the system just like an additional source of generation. Thus the RL model is likely invalid.

## Problem 2:

Repeat Problem 1 (analysis and modeling of parts 1 and 4) with the bus circuit breaker open.

In [13]:

```
1  # Evaluate RLC System
2
3  # Base impedance remains unaltered
4  # Zsrc_pu
5  # Zgen
6  # Zxfm
7
8  # Evaluate the simplified EQ impedance
9  Zeq = eep.parallelz((Zsrc_pu+Zxfm),Zgen) * Zbase
10 print("Equivalent Circuit Impedance:",Zeq,"Ω")
11 print("Zeq Elements:",eep.reactance(Zeq),"(Ω, H)")
```

Equivalent Circuit Impedance: (0.0101846423212+0.267354486306j) Ω

Zeq Elements: (0.010184642321227273, 0.00070969418257827517) (Ω, H)

In [14]:

```
1  # Display Available Impedances
2
3  print("Source Impedance:",eep.reactance(Zsrc_pu*Zbase),"(Ω, H)")
4  print("Transformer Impedance:",eep.reactance(Zxfm*Zbase),"(Ω, H)")
5  print("Generator Z:",eep.reactance(Zgen*Zbase),"(Ω, H)")
```

Source Impedance: (0.0036193943897564313, 0.00014433079696390735) (Ω, H)


Transformer Impedance: (0.025559860364250453, 0.0012628944734341895) (Ω, H)

Generator Z: (0.011239376770538243, 0.0014313524185196062) (Ω, H)

```

In [15]: 1 # Load Data from File for Part A
2 data = np.genfromtxt("PartAA_data.ADF",delimiter='\t',skip_header=2,usecols=
3 t_arr, LC_V, RLC_V = data
4
5 # Plot Data
6 plt.plot(t_arr,LC_V,label="LC-Voltage")
7 plt.plot(t_arr,RLC_V,label="RLC-Voltage")
8 plt.legend()
9 plt.title("Part 2.1")
10 plt.show()
11
12 # Plot Data
13 plt.subplot(1,2,1)
14 plt.plot(t_arr,LC_V,label="LC-Voltage")
15 plt.plot(t_arr,RLC_V,label="RLC-Voltage")
16 plt.legend()
17 plt.xlim(0,0.05)
18 plt.subplot(1,2,2)
19 plt.plot(t_arr,LC_V,label="LC-Voltage")
20 plt.plot(t_arr,RLC_V,label="RLC-Voltage")
21 plt.legend()
22 plt.xlim(0.45,0.5)
23 plt.show()

```

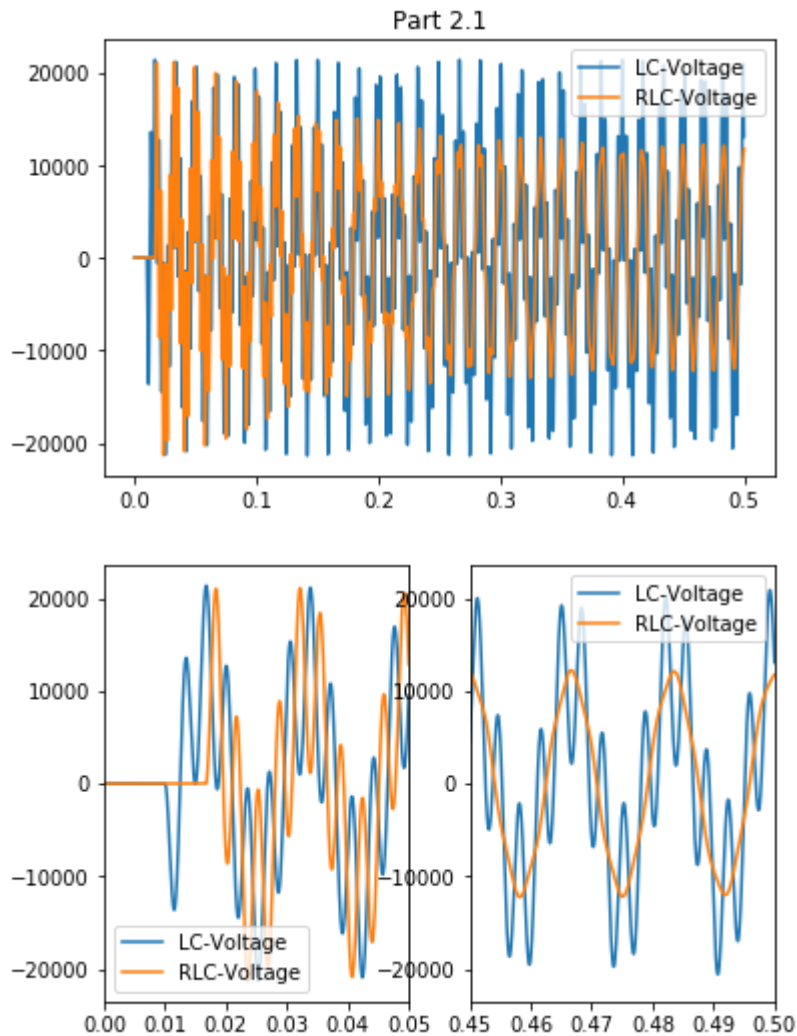


**Remarks**

Note here that there is only a slight difference from the view shown earlier where the breaker was closed. This is just due to a change in the equivalent Thevenin circuit which has caused a difference in the system impedance (and thus the available fault current).

In [16]:

```
1 # Plot Data From Previous
2 plt.plot(t_d,VCAP_d,label="Breaker Closed")
3
4 # Load New Data from File
5 data = np.genfromtxt("PartDD_data.ADF",delimiter='\t',skip_header=2,usecols=
6 t_arr, VCAP= data
7
8 # Plot Data
9 plt.plot(t_arr,VCAP,label="Breaker Open")
10 plt.legend()
11 plt.title("Part 2.2 Cap. Voltage")
12 plt.show()
13
14 # Plot Data
15 plt.subplot(1,2,1)
16 plt.plot(t_d,VCAP_d,label="Breaker Closed")
17 plt.plot(t_arr,VCAP,label="Breaker Open")
18 plt.legend()
19 plt.xlim(0,0.05)
20 plt.subplot(1,2,2)
21 plt.plot(t_d,VCAP_d,label="Breaker Closed")
22 plt.plot(t_arr,VCAP,label="Breaker Open")
23 plt.legend()
24 plt.xlim(0.175,0.2)
25 plt.show()
```

 



## Remarks

Note here that there are some subtle differences between the breaker-open and breaker-closed systems. Of course, this is due to the fact that the thevenen circuit will be vastly different based upon the state of the breaker. It is worth noting that although both circuits show some differences in the transient state, they both converge to a like steady state.

In [ ]:

1	
---	--