

# Joe Stanley

## ECE 524 - HWK 7

```
In [1]: 1  # Import Libraries
        2  import numpy as np
        3  import matplotlib.pyplot as plt
        4  import eepower as eep
        5  from eepower import p,n,u,m,k,M
```

## Problem 1

In [55]:

```
1  # Define givens
2  Vsrc = 345*k #transformer is Y-G
3  N = 345/69
4  Srat = 100*M
5  Xleak = 10/100
6  XoR = 12
7  Cphsgrnd = 7.5*n # HV side
8
9  # A)
10 Rloss = Xleak / XoR
11 leak = Rloss+1j*Xleak * eep.zpu(S=Srat,VLN=Vsrc)
12 print("Leakage:",leak,"Ω")
13 Imax = Vsrc / leak
14 print("Worst Case Peak Fault Current:",abs(Imax),"A (High-Side)")
15 print("Worst Case Peak Fault Current:",abs(Imax/k)*N,"kA (Low-Side)")
16 print("Angle of Inception:",np.degrees(np.angle(Imax)),"°\n")
17
18 # B)
19 Lleak = eep.reactance(Xleak * eep.zpu(S=Srat,VLN=Vsrc))
20 print("Leakage Inductance:",Lleak/m,"mH")
21 oscfreq = eep.fault.natfreq(C=Cphsgrnd,L=Lleak)
22 print("Oscillation Frequency:",oscfreq,"Hz")
23 print("Oscillation T-cycle:",(1/oscfreq)/m,"msec")
24 pkV = eep.fault.pktransrecvolt(Cphsgrnd,Lleak,VLN=Vsrc)[0]
25 print("Peak Voltage:",pkV/k,"kV\n")
26
27 print("7.5nF",Cphsgrnd*u/n,"uF")
```

Leakage: (0.008333333333333333+357.07500000000005j) Ω  
Worst Case Peak Fault Current: 966.1835746161103 A (High-Side)  
Worst Case Peak Fault Current: 4.830917873080551 kA (Low-Side)  
Angle of Inception: -89.9986628444 °

Leakage Inductance: 947.170855076 mH  
Oscillation Frequency: 1888.31888658 Hz  
Oscillation T-cycle: 0.529571571362 msec  
Peak Voltage: 975.809971318 kV

7.5nF 7.500000000000001e-06 uF

## Problem 2

In [50]:

```
1  # Define givens
2  Srat = 300*M
3  ZHX = 9.46j/100 # 300 MVA
4  ZHY = 4.236j/100 # 30 MVA
5  ZXY = 3.184j/100 # 30 MVA
6  ExLoss = 918.75*k
7  ExI = 2.56
8
9  # Convert to common base
10 ZHX *= Srat/(300*M)
11 ZHY *= Srat/(30*M)
12 ZXY *= Srat/(30*M)
13
14 # Find supportive components
15 ZH = 0.5*(ZHX+ZHY-ZXY)
16 ZX = 0.5*(ZHX+ZXY-ZHY)
17 ZY = 0.5*(ZHY+ZXY-ZHX)
18 print("ZH:",ZH,"Ω-pu")
19 print("ZX:",ZX,"Ω-pu")
20 print("ZY:",ZY,"Ω-pu")
21
22 # Evaluate PU-Bases and Inductances
23 ZH *= eep.zpu(S=Srat,VLN=525*k)
24 ZX *= eep.zpu(S=Srat,VLN=241.5*k)
25 ZY *= eep.zpu(S=Srat,VLL=34.5*k)
26 LH = eep.reactance(ZH)
27 LX = eep.reactance(ZX)
28 LY = eep.reactance(ZY)
29 print("H-Winding Inductance:",LH/m,"mH")
30 print("X-Winding Inductance:",LX/m,"mH")
31 print("Y-Winding Inductance:",LY/m,"mH")
32
33 # Evaluate Rm
34 Rm = ((525*k)**2/ExLoss)
35 print("Magnetizing Resistance:",Rm,"Ω")
```

ZH: 0.09989999999999999j Ω-pu

ZX: -0.0052999999999999971j Ω-pu

ZY: 0.3237j Ω-pu

H-Winding Inductance: 730.3869018085658 mH

X-Winding Inductance: 0.8581411766990243 mH

Y-Winding Inductance: 3.406657842088726 mH

Magnetizing Resistance: 300000.0 Ω

In [ ]:

1

In [ ]:

1