

## ECE 525

## Exam 1

July 2019

### EXAMINATION RULES

1. This is an open-book/open-note take-home exam.
2. I can e-mail a MathCAD or Mathcad Prime file with the exam problems to you if you would like a copy.
3. Do your own work on this examination. You are on your honor. Therefore, you will neither give nor receive aid on this examination, except from the *course* instructor. If you violate this trust, you will receive the grade of zero for this examination.
4. Show all of your work! Make it neat. *No* partial credit will be given if I can not easily follow your work.
5. ***You have 3 days to complete the exam the exam from the time you receive it from your proctor.***
6. Please read and sign the following statement when you finish the exam:

I certify that I have neither given nor have I received any help on this examination, except from the course instructor.

SIGNED: \_\_\_\_\_

PRINTED NAME: \_\_\_\_\_

DATE: \_\_\_\_\_

1. \_\_\_\_\_/25 pts

2. \_\_\_\_\_/20 pts

3. \_\_\_\_\_/25 pts

4. \_\_\_\_\_/30 pts

Total: \_\_\_\_\_/100 pts

**1. (25 pts) Overcurrent Protection**

- (a) How does one determine the coordinating time between a protective device and a downstream device? Explain how this is implemented in a protection scheme if inverse time overcurrent elements are used? How might you implement it if you are only using instantaneous overcurrent elements?
- (b) Why would an inverse time overcurrent could be combined with instantaneous overcurrent element? Sketch a combined characteristic for such an implementation and describe how it works. Describe an application where this would be used.
- (c) How could symmetrical component based overcurrent elements improve the performance of overcurrent elements? What are the advantages? Is any special equipment needed to implement zero sequence or negative sequence based elements?
- (d) As you begin setting inverse time overcurrent relays for a radial distribution system, the short circuit MVA looking into the transmission system is given as a range from 66 MVA to 90 MVA. Which value do you use when determining minimum pick up levels for the relays and reclosers in the circuit? Which do you use for determining time dial settings?
- (e) Due to power quality problems arising from voltage sags, an inductive reactance is added in the neutral to ground path of a transformer supplying several distribution feeders. Assuming the overcurrent protection uses phase elements and ground elements, will any settings need to be changed as a result? If so, which ones and how are they changed?

2. (20 pts) Current Transformers:

- A. Describe what causes a CT to saturate. Comment on how this differs if the current is only at fundamental frequency versus a combination of fundamental frequency and a decaying dc offset.
- B. How would CT saturation impact the performance of an overcurrent relay? If this causes a misoperation, in what way will it misoperate? Will it eventually give a correct output? Support your answer for each.
- C. Do CTs work better with a small burden impedance or a large burden impedance? Explain
- D. Explain why it is a bad idea for an unused CT to be open circuited? Does an open circuited CT impact the primary side power system? What should you do with a CT when the output is not needed (possibly temporarily)?
- E. Is it sufficient to delay the onset of saturation or must it be avoided altogether? If so, how do you decide how much delay is acceptable? Explain


**3. (25 pts) Voltage Transformers:**

- A. Would you be concerned about using a wound VT to measure voltage harmonics or other high frequency disturbances? How about if you only want to detect a transient event has occurs rather than accurate magnitude and angle? Explain your answer.
- B. Repeat part A for a CVT. Explain your answer.
- C. What options can be chosen to improve CVT performance when choosing a CVT? What are the trade-offs with these options?
- D. Is saturation normally a concern for VTs or CVTs? Are there circumstances where it could arise? Explain your answer and describe any circumstances.
- E. How might a CVT transient impact the performance of a protective relay response? Out of the types of elements discussed so far, which are more likely to be effected?

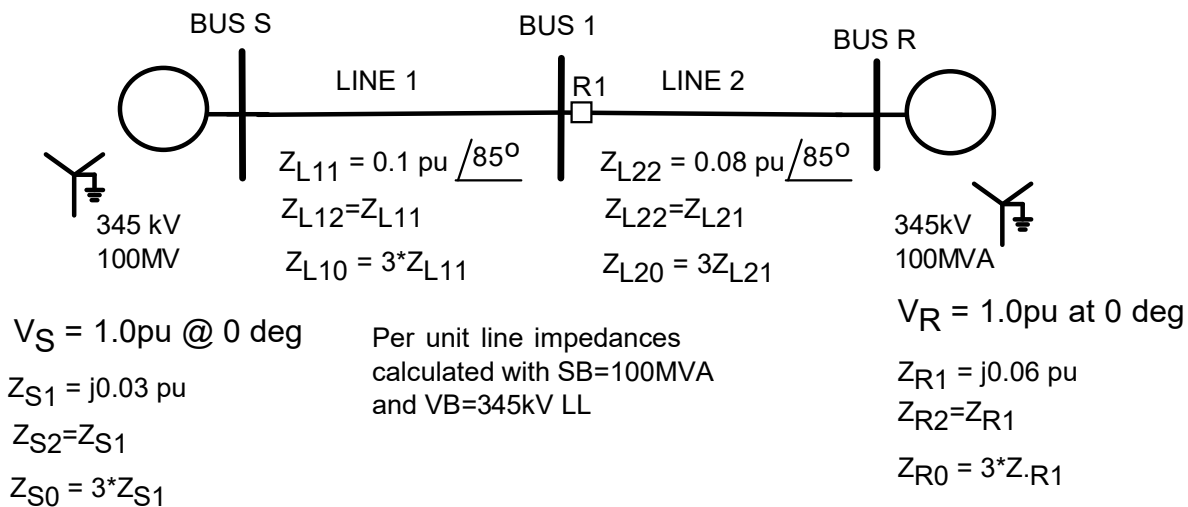4. (30 pts) The voltage and current magnitudes and angles provided below the figure are the results as seen by a relay located at R1 on a simulated power system. Assume the primary side MVA base of 100MVA, and a voltage base of 345kV and a CTR of 1500/5 and PTR of 345kV/120V for the power system shown below. Assume that you have a relay with a directional element located at R1 with the forward direction set to look into LINE 2. The relay have multiple directional elements available to operate in parallel.

Do the following:

- [4 pts] Determine the value for the maximum torque angle (explain your reasoning behind this selection). Also explain why you need a maximum torque angle.
- [20 pts] Determine the direction to fault relative to the relay location using at least two significantly different methods for each fault and also try to identify the fault type. Explain how you made this determination and why you selected the methods you used (this reasoning may differ by case)
- [6 pts] List the settings you used for the directional elements in part (b). Note that you should not have different settings for each of the 4 cases, just a single set of settings. Also include any elements to qualify the elements to ensure security against misoperation.



CASEA:

$$|I_{abcFA}| = \begin{pmatrix} 5.2658 \\ 5.2658 \\ 5.2658 \end{pmatrix} \text{ pu} \quad \arg(I_{abcFA}) = \begin{pmatrix} -85.7889 \\ -205.7889 \\ 34.2111 \end{pmatrix} \text{ deg}$$

$$|V_{abcFA}| = \begin{pmatrix} 0.3159 \\ 0.3159 \\ 0.3159 \end{pmatrix} \text{ pu} \quad \arg(V_{abcFA}) = \begin{pmatrix} -0.7889 \\ -120.7889 \\ 119.2111 \end{pmatrix} \text{ deg}$$

CASE B:

$$|I_{abcB}| = \begin{pmatrix} 0 \\ 4.3201 \\ 4.3201 \end{pmatrix} \text{pu}$$

$$\arg(I_{abcB}) = \begin{pmatrix} 0 \\ -10.3489 \\ -162.5532 \end{pmatrix} \text{deg}$$

$$|V_{abcB}| = \begin{pmatrix} 1.1935 \\ 0.3228 \\ 0.3228 \end{pmatrix} \text{pu}$$

$$\arg(V_{abcB}) = \begin{pmatrix} 0.1121 \\ -121.451 \\ 118.549 \end{pmatrix} \text{deg}$$

CASE C:

$$|I_{abcC}| = \begin{pmatrix} 3.2957 \\ 1.2874 \\ 1.2874 \end{pmatrix} \text{pu}$$

$$\arg(I_{abcC}) = \begin{pmatrix} -76.9625 \\ -126.6662 \\ 113.3338 \end{pmatrix} \text{deg}$$

$$|V_{abcC}| = \begin{pmatrix} 0.3159 \\ 1.1271 \\ 1.156 \end{pmatrix} \text{pu}$$

$$\arg(V_{abcC}) = \begin{pmatrix} -0.7889 \\ -142.0355 \\ 121.4844 \end{pmatrix} \text{deg}$$

CASE D:

$$|I_{abcD}| = \begin{pmatrix} 1.2874 \\ 1.2452 \\ 2.2247 \end{pmatrix} \text{pu}$$

$$\arg(I_{abcD}) = \begin{pmatrix} -6.6662 \\ 50.4357 \\ -158.6344 \end{pmatrix} \text{deg}$$

$$|V_{abcD}| = \begin{pmatrix} 0.9833 \\ 1.0374 \\ 0.6938 \end{pmatrix} \text{pu}$$

$$\arg(V_{abcD}) = \begin{pmatrix} -9.6265 \\ -149.5794 \\ 96.1953 \end{pmatrix} \text{deg}$$

# Joe Stanley

## ECE 525 - Midterm Exam (EX 1)

In [8]:

```
1  # Import Libraries
2  import numpy as np
3  import matplotlib.pyplot as plt
4  import eepower as eep
5  from eepower import u,m,k,M
6
7  # Define Maximum Torque Angle Formula
8  def torqueangle(Vbc,Ia,k=1,beta=None):
9      """
10     torqueangle Function
11
12     Calculates the torque angle from the
13     respective voltage and current.
14
15     Parameters
16     -----
17     Vbc:          complex
18                  The voltage between phases B and C, may
19                  be a float (not complex) if beta is specified
20                  as value other than None.
21     Ia:           complex
22                  The current in phase A, may be a float (not
23                  complex) if beta is specified as value other
24                  than None.
25     k:            float, optional
26                  The specified design constant.
27     beta:         float, optional
28                  The angle difference between Vbc and Ia. Must
29                  be specified if Vbc and/or Ia are specified as
30                  floats. default=None
31
32     Returns
33     -----
34     TA:           float
35                  Calculated Maximum Torque Angle.
36     """
37     # Test if beta must be calculated
38     if beta==None:
39         # Calculate beta from angles
40         beta = np.angle(Vbc) - np.angle(Ia)
41     else:
42         # Convert beta to radians
43         beta = np.radians(beta)
44     # Evaluate MTA
45     TA = k*abs(Vbc)*abs(Ia)*np.cos(beta-np.radians(90))
46     return(MTA)
```


# Problem 1:

a) How does one determine the coordinating time between a protective device and a downstream device? Explain how this is implemented in a protection scheme if inverse time overcurrent elements are used? How might you implement it if you are only using instantaneous overcurrent elements?

- Coordination between protective devices (upstream and downstream) relies primarily on a time delay commonly referred to as a time-dial. The term "Time-Dial" refers to the mechanical setting that must be applied in electro-mechanical relays. However, the setting still applies in modern microprocessor based relays. When using inverse-time-over-current elements, this can be applied based on a formula that takes into account the pickup settings for both upstream/downstream devices and the coordinating time interval to evaluate a constant time-dial setting based on the TOC curve of choice (ie U1, U2, C1, etc.). When applying solely instantaneous OC elements instead of the more adaptive inverse TOC elements, a constant pickup delay may be applied in conjunction with the OC element, thus the OC must be sustained for a certain delay period (regardless of current amplitude) before the element asserts. With multiple OC elements, this can be applied in a step fashion, creating a trip characteristic that begins to better resemble a TOC element.

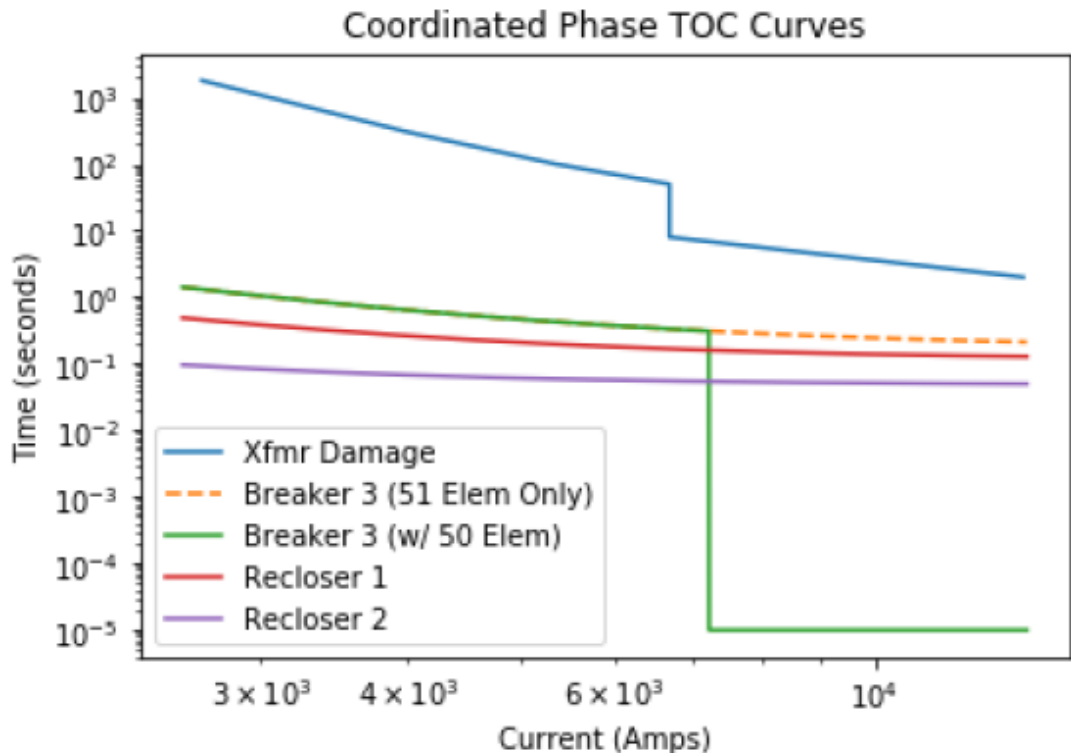b) Why would an inverse time overcurrent be combined with instantaneous overcurrent element? Sketch a combined characteristic for such an implementation and describe how it works. Describe an application where this would be used.

- Such combinations might be used to act on high-current, close-in faults, thus reducing the time required before tripping. The figure below (taken from Homework 4) illustrates how the combination might appear in terms of tripping characteristics. Notice that the green and dashed orange lines both carry the same curve characteristic, but because of the combined instantaneous element, the green line drops to (essentially) zero when the current level surpasses the pickup threshold.





**c) How could symmetrical component based overcurrent elements improve the performance of overcurrent elements? What are the advantages? Is any special equipment needed to implement zero sequence or negative sequence based elements?**

- Symmetrical components can aid protection in their effective pickup of smaller faults; faults that may not surpass the threshold for standard over-current elements, but surpass the characteristics set for imbalance tripping. Additionally, seq-comp based protection can help determine the direction of the fault. Typically, "special" equipment is not required to use seq-comp protection, but microprocessor-based relays typically are required as they can perform the calculations internally to determine tripping characteristics.

**d) As you begin setting inverse time overcurrent relays for a radial distribution system, the short circuit MVA looking into the transmission system is given as a range from 66 MVA to 90 MVA. Which value do you use when determining minimum pick up levels for the relays and reclosers in the circuit? Which do you use for determining time dial settings?**

- Determining minimum pickup levels for relays and reclosers would require the minimum fault current, thus the minimum short-circuit-MVA (66-MVA). Determining the time-dial settings requires the maximum fault current, thus the maximum SCMVA (90-MVA).

**e) Due to power quality problems arising from voltage sags, an inductive reactance is added in the neutral to ground path of a transformer supplying several distribution feeders. Assuming the overcurrent protection uses phase elements and ground elements, will any settings need to be changed as a result? If so, which ones and how are they changed?**

- Yes, some settings will likely require alteration. The settings that should be altered should be the ground-element settings, they should be changed to account for the additional reactance.

## **Problem 2:**

**a) Describe what causes a CT to saturate. Comment on how this differs if the current is only at fundamental frequency versus a combination of fundamental frequency and a decaying dc offset.**

- CTs can saturate for a variety of reasons, however, the largest reasons are because of being over-burdened or because of having too much current travel through their primary. CTs, like all transformers, carry a B-H curve characteristic. The characteristic is largely non-linear, but we use the linear portions of the CT's characteristic to evaluate the current levels. If the current is too great, or the burden is too high, the CT will leave the linear portion, falling into what we call saturation.
- Adding a decaying DC offset to a standard fundamental frequency further complicates the CT B-H relationship. The offset will further press the operation out of a linear region, making the CT's characteristics increasingly complex.

**b) How would CT saturation impact the performance of an overcurrent relay? If this causes a misoperation, in what way will it misoperate? Will it eventually give a correct output? Support your answer for each.**

- CT saturation often causes a relay to underperceive the current on a line, thus they will often misoperate by missing characteristics which require tripping. The CT's saturation often is a

passing characteristic, thus it will often correct itself shortly after it causes problems, so the relay will eventually operate correctly (given enough time).

**c) Do CT's work better with a small burden impedance or a large burden impedance?**

**Explain**

- CTs work better with smaller burden impedances (just as the word burden so implies). The larger the burden impedance, the further the CT strays from its linear region (and thus closer to saturation).

**d) Explain why it is a bad idea for an unused CT to be open circuited? Does an open circuited CT impact the primary side power system? What should you do with a CT when the output is not needed (possibly temporarily)?**

- CTs are treated as if they are current sources, and an open circuit can be represented by a resistor with an infinite (or nearly infinite) resistance. From the perspective of burden impedance, an infinite resistance is very bad, and will cause saturation issues; worse yet, from the perspective of the CT acting as a current source, with an infinite resistance, a current source must generate an equally infinite voltage to overcome the resistance. Such performance will enable arcing and thus can be dangerous and damaging.
- When removing equipment from service and pulling it from connected CTs, the CTs should be shorted. In fact, in most cases, CT connections are made with a CT shorting bar or shorting switch that make this process quite easy.
- CT open-circuits will inevitably impact the primary power system, although they may or may not have significant impact based on the system parameters.

**e) Is it sufficient to delay the onset of saturation or must it be avoided altogether? If so, how do you decide how much delay is acceptable? Explain**

- Undoubtedly, it is far better to avoid CT saturation altogether, but in certain situations, delaying such performance may be accepted. The acceptable delay is determined by identifying how much time is required between fault inception, and fault detection. In other words, the delay is based on how long it takes for the relay to identify the characteristics that justify tripping.

### **Problem 3:**

**a) Would you be concerned about using a wound VT to measure voltage harmonics or other high frequency disturbances? How about if you only want to detect a transient event has occurs rather than accurate magnitude and angle? Explain your answer.**

- Traditional (wound) VTs (or, equally, PTs) are able to measure harmonics quite well as they do not inherently apply any frequency filtering due to capacitive reactance, since they are simply wound transformers, they transfer harmonic content quite well.
- Traditional VTs would not be my primary choice for detecting transient events (regardless of mag/ang) because they would be subject to saturation and likely not provide useful data.

**b) Repeat part A for a CVT. Explain your answer.**

- CVTs are not able to accurately measure harmonic content since they apply inherent filtering due to their capacitive nature. As such, the data would be filtered and provide inaccurate

harmonic levels.

- CVTs would be a primary choice for identifying transient information since their response would be (largely) unimpeded by saturation characteristics due to their capacitive construction. As suggested, their magnitudes and angles may be largely incorrect, but they would likely provide enough useful information to correctly identify transients.

**c) What options can be chosen to improve CVT performance when choosing a CVT? What are the trade-offs with these options?**

- Choosing an active or passive CVT and the C-rating of the CVT are both considerations for choosing a CVT. Changing the C-rating will affect the sensitivity, and the range of the CVT. Choosing active/passive will affect the frequency response of the CVT.

**d) Is saturation normally a concern for VTs or CVTs? Are there circumstances where it could arise? Explain your answer and describe any circumstances.**

- Saturation is primarily a concern for VTs, but it can also affect CVTs. Over-burdening the VTs can cause saturation, as well as certain transient characteristics.

**e) How might a CVT transient impact the performance of a protective relay response? Out of the types of elements discussed so far, which are more likely to be effected?**

- CVT transients impact the performance of protective relays by increasing the time to accurately evaluate fault characteristics. These transients increase the number of time-steps it takes to evaluate the fault impedance. In many situations, this delay causes inaccurate fault impedance encroachment curves. These curves may fall into the operate zone of a relay element (typically instantaneous -50- elements).

## **Problem 4:**

**a) Determine the value for the maximum torque angle (explain your reasoning behind this selection). Also explain why you need a maximum torque angle.**

- According to the formula:  $MTA = k * |V_{BC}| * |I_A| * \cos(\beta - 90^\circ)$  and the circuit parameters (which dictate zero power flow) the maximum torque angle is zero; this is because the phase-A current ( $I_A$ ) is zero. The maximum torque angle was a term coined for use in electro-mechanical relays, but it is still used frequently with modern microprocessor relays. It is used to determine the direction of the fault.

**b) Determine the direction to fault relative to the relay location using at least two significantly different methods for each fault and also try to identify the fault type. Explain how you made this determination and why you selected the methods you used (this reasoning may differ by case)**

In [30]:

```
1  # Define Case Components
2  # CASE A:
3  IabcFA = [eep.phasor(5.2658,-85.7889),
4            eep.phasor(5.2658,-205.7889),
5            eep.phasor(5.2658,34.2111)]
6  VabcFA = [eep.phasor(0.3159,-0.7889),
7            eep.phasor(0.3159,-120.7889),
8            eep.phasor(0.3159,119.2111)]
9  # CASE B:
10 IabcFB = [eep.phasor(0,0),
11           eep.phasor(4.3201,-10.3489),
12           eep.phasor(4.3201,-162.5532)]
13 VabcFB = [eep.phasor(1.1935,0.1121),
14           eep.phasor(0.3228,-121.451),
15           eep.phasor(0.3228,118.549)]
16 # CASE C:
17 IabcFC = [eep.phasor(3.2957,-76.9625),
18           eep.phasor(1.2874,-126.6662),
19           eep.phasor(1.2874,113.3338)]
20 VabcFC = [eep.phasor(0.3159,-0.7889),
21           eep.phasor(1.1271,-142.0355),
22           eep.phasor(1.156,121.4844)]
23 # CASE D:
24 IabcFD = [eep.phasor(1.2874,-6.6662),
25           eep.phasor(1.2452,50.4357),
26           eep.phasor(2.2247,-158.6344)]
27 VabcFD = [eep.phasor(0.9833,-9.6265),
28           eep.phasor(1.0374,-149.5794),
29           eep.phasor(0.6938,96.1953)]
30
31 # Determine Fault Location
32 def faultloc(V,I):
33     print("Sequence Component Analysis")
34     V012 = eep.Aabc.dot(V)
35     I012 = eep.Aabc.dot(I)
36     Z012 = V012/I012
37     Z1 = Z012[1]
38     if(abs(np.degrees(np.angle(Z1))) < 90):
39         print("Fault Occurred Downstream (between Bus-1 and Bus-R)")
40     else:
41         print("Fault Occurred Upstream (between Bus-1 and Bus-S)")
42     eep.cprint(Z1,label="Pos-Seq-Z")
43 def loadflow(V):
44     print("Load Flow Analysis")
45     P = 0
46     for i in range(3):
47         Vs = eep.phasor(1,0)
48         Zx = eep.phasor(0.1,85)+0.03j
49         P += eep.powerflow(Vs,V[i],Zx)
50     if(abs(np.degrees(np.angle(P))) < 90):
51         print("Fault Occurred Downstream (between Bus-1 and Bus-R)")
52     else:
53         print("Fault Occurred Upstream (between Bus-1 and Bus-S)")
54     eep.cprint(P,label="Total Power Flow")
55
56
```

```

57 # CASE A:
58 faultloc(VabcFA,IabcFA)
59 loadflow(VabcFA)
60 print()
61 # CASE B:
62 faultloc(VabcFB,IabcFB)
63 eep.cprint(eep.Aabc.dot(VabcFB),"V")
64 eep.cprint(eep.Aabc.dot(IabcFB),"I")
65 print()
66 # CASE C:
67 faultloc(VabcFC,IabcFC)
68 eep.cprint(eep.Aabc.dot(VabcFC),"V")
69 eep.cprint(eep.Aabc.dot(IabcFC),"I")
70 print()
71 # CASE D:
72 faultloc(VabcFD,IabcFD)
73 loadflow(VabcFD)
74 eep.cprint(eep.Aabc.dot(IabcFD),"I")

```

Sequence Component Analysis

Fault Occurred Downstream (between Bus-1 and Bus-R)

Pos-Seq-Z  $0.06 \angle 85.0^\circ$

Load Flow Analysis

Fault Occurred Downstream (between Bus-1 and Bus-R)

Total Power Flow  $0.0 \angle -82.875^\circ$

Sequence Component Analysis

Fault Occurred Upstream (between Bus-1 and Bus-S)

Pos-Seq-Z  $0.222 \angle -93.986^\circ$

[['  $0.29 \angle 0.691^\circ$  V']

['  $0.613 \angle -0.437^\circ$  V']

['  $0.29 \angle 0.691^\circ$  V']]

[['  $0.692 \angle -86.451^\circ$  I']

['  $2.767 \angle 93.549^\circ$  I']

['  $2.075 \angle -86.451^\circ$  I']]

Sequence Component Analysis

Fault Occurred Downstream (between Bus-1 and Bus-R)

Pos-Seq-Z  $0.529 \angle 37.784^\circ$

[['  $0.404 \angle 166.24^\circ$  V']

['  $0.849 \angle -8.972^\circ$  V']

['  $0.135 \angle 166.229^\circ$  V']]

[['  $1.036 \angle -99.917^\circ$  I']

['  $1.606 \angle -46.756^\circ$  I']

['  $1.036 \angle -99.917^\circ$  I']]

Sequence Component Analysis

Fault Occurred Upstream (between Bus-1 and Bus-S)

Pos-Seq-Z  $1.172 \angle -101.213^\circ$

Load Flow Analysis

Fault Occurred Upstream (between Bus-1 and Bus-S)

Total Power Flow  $0.0 \angle 93.847^\circ$

[['  $0.0 \angle -33.381^\circ$  I']

['  $0.763 \angle 80.324^\circ$  I']

['  $1.462 \angle -38.091^\circ$  I']]

*From analysis of the faults characterized above, the following can be found:*

**Case A:**

- Downstream, 3-Phase Fault
- Direction Determined by Sequence Impedance
- Fault type characterized by equal voltage/current magnitudes

**Case B:**

- Upstream, line-to-line-to-ground
- Direction Determined by Sequence Impedance
- Fault type characterized by Sequence Components

**Case C:**

- Downstream, single-line-to-ground
- Direction Determined by Sequence Impedance
- Fault type characterized by Sequence Currents

**Case D:**

- Upstream fault (Unidentified)
- Direction Determined by Sequence Impedance

In [ ]:

|   |  |
|---|--|
| 1 |  |
|---|--|